



Indicating meter

order: 2nd order

$$G(s) = \frac{km^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$0 < \zeta < 1$  underdamped case

$\zeta = 1$  Critical

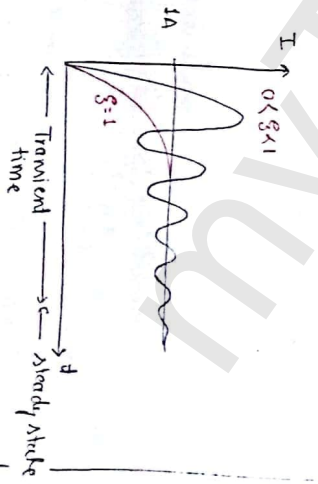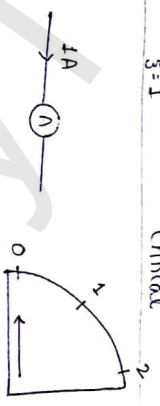

For practical indicating meter

$$\zeta = 0.6 \text{ to } 0.8$$

Torque

Damping Torque: To stop/damp oscillations at final steady state position so that accurate time is achieved.

Instrument	Damping
M.I, Emmc	Air friction
Electrostatic	fluid friction
PMMC	Eddy current
Galvanometer	Electromagnetic

Controlling torque ( $T_c$ ):

Spring control :  $T_c = K\theta \Rightarrow$  linear response

Gravity :  $T_c \propto \sin\theta \Rightarrow$  non-linear response

$T_c = N-m$

$K = N-m/rad \text{ or } N-m/degree$

$\theta = Rad \text{ or degree}$

Deflecting torque.

$T_d \propto$  (Quantity to be measured)

At balance :

$T_d = T_c$

Electromagnetic Instrument	$T_d$	$T_c$	$T_d = T_c$	Application
PMMC	$NBI A$	$K\theta$	$NBI A = K\theta$ $\theta \propto I$	Measures DC, AC Rectifier meter, Thermal meter
M.I	$\frac{1}{2} I^2 \frac{dL}{d\theta}$	$K\theta$	$K\theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$ $\theta \propto I^2$	Measure AC & DC current voltage AC-99MS
Emmc/ED (Electrodynamic)	$I^2 \frac{dM}{d\theta}$	$K\theta$	$K\theta = I^2 \frac{dM}{d\theta}$ $\theta \propto I^2$	Measure AC & DC <u>(Transformer instrument)</u> can be used for measurement of AC without standardisation

Q1 A PMMC instrument has a coil of dimensions  $10mm \times 8mm$  the flux density is in the air gap is  $0.15 \text{ wT/m}^2$  if the coil is wound for 100 turns carrying a current of  $5mA$  calc  
 ① Deflecting torque  
 ② Deflection of the spring coil in  $0.2 \times 10^{-6} \text{ N-m/degree}$

Soln

①  $T_d = NBI A$

$= 100 \times 0.15 \times 5 \times 10^{-3} \times 10 \times 8 \times 10^{-6}$

$= \frac{106 \times 15 \times 5 \times 10 \times 8 \times 10^{-9}}{100}$

$750 \times 8 \times 10^{-9} = 6000 \times 10^{-9} = 6 \times 10^{-6} \text{ N-m}$

②  $T_d = T_c = K\theta$

$6 \times 10^{-6} = 0.2 \times 10^{-6} \times \theta$

$\theta = 30 \text{ degree}$

Solc

- If pure AC signal is send to PMMC like  $I = I_m \sin \omega t$  and the pointer vibrates near to zero because of inertia of the instrument. The avg value of  $\sin \omega t$  is 0.

- If spring is broken or unattached then the pointer will come to zero in that position in case of PMMC bcz current is passing through the spring. If in all other case pointer move to max<sup>m</sup> posn?

Instrument	Damping
MI, Emmc	Air friction
Electrostatic	fluid friction
pmmc	Eddy current
Galvanometer	Electromagnetic

Controlling torque ( $T_c$ ):

Spring control:  $T_c = K\theta \Rightarrow$  Linear response

Control:  $T_c \propto \sin\theta \Rightarrow$  Non-linear response

$T_c = N \cdot m$

$K = N \cdot m / \text{rad or } N \cdot m / \text{degree}$

$\theta = \text{Rad or degree}$

Deflecting torque.

$T_d \propto$  (Quantity to be measured)

At balance:

$T_d = T_c$

Electromagnetic instrument's	$T_d$	$T_c$	$T_d = T_c$	Applications
pmmc	$NBI A$	$K\theta$	$NBI A = K\theta$ $\theta \propto I$	Measure DC, Vdc Rectifier meter, Thermometer
MI	$\frac{1}{2} I^2 \frac{dL}{d\theta}$	$K\theta$	$K\theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$ $\theta \propto I^2$	Measure AC & DC current voltage AC $\rightarrow$ sinus
Emmc/ED	$I^2 \frac{dM}{d\theta}$	$K\theta$	$K\theta = I^2 \frac{dM}{d\theta}$ $\theta \propto I^2$	Measure AC & DC [Transformer instrument] radiated for dc Same is used for measurements of ac without calibration

Q1 A pmmc instrument has a coil of dimensions  $10\text{mm} \times 8\text{mm}$  the flux density is  $0.15 \text{ Wb/m}^2$  if the coil is wound for 100 turns carrying a current of  $5\text{mA}$  calc.  $\theta$  Deflecting torque.

$\theta$  Deflection of the spring will be  $0.2 \times 10^{-6} \text{ N-m/degree}$

soln  $\theta T_d = NBI A$

$= 100 \times 0.15 \times 5 \times 10^{-3} \times 10 \times 8 \times 10^{-6}$

$= \frac{100 \times 15 \times 5 \times 10 \times 8 \times 10^{-9}}{100}$

$750 \times 8 \times 10^{-9} = 6000 \times 10^{-9} = 6 \times 10^{-6} \text{ N-m}$

$\theta T_d = T_c = K\theta$

$6 \times 10^{-6} = 0.2 \times 10^{-6} \times \theta$

$\theta = 30 \text{ degree}$

Note:

If pure AC signal is send to pmmc &  $I = I_m \sin \omega t$  and the pointer vibrates near to zero because of smooth of the instrument. The avg value of  $\sin \omega t$  is 0.

If spring is broken or damaged then the pointer will come to zero in that position in case of pmmc big current is passing through the spring. If in all other case pointer move to max<sup>m</sup> pos<sup>n</sup>.

Measurement	Damping
MJ, Emmc	Air friction
Electrostatic	fluid friction
PMMC	Eddy current
Galvanometer	Electromagnetic

Controlling torque (T<sub>c</sub>):

Spring control : T<sub>c</sub> = Kθ ⇒ Linear scale

Gravity : T<sub>c</sub> ∝ Sinθ ⇒ Non-linear scale

T<sub>c</sub> = N-m

K = N-m/rad or N-m/degree

θ = Rad or degree

Deflecting torque:

T<sub>d</sub> ∝ (Quantity to be measured)

At balance :

T<sub>d</sub> = T<sub>c</sub>

Electromagnetic instrument	T <sub>d</sub>	T <sub>c</sub>	T <sub>d</sub> = T <sub>c</sub>	Application
PMMC	NBIA	Kθ	NBIA = Kθ θ ∝ I	Measure DC, AC, Voltage Rectifier meter, Thermal meter
MI	$\frac{1}{2} I^2 \frac{dL}{d\theta}$	Kθ	$K\theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$ θ ∝ I <sup>2</sup>	Measure AC & DC current voltage AC → SImS
Emmc/ED (Electrodynamometer)	$I^2 \frac{dM}{d\theta}$	Kθ	$K\theta = I^2 \frac{dM}{d\theta}$ θ ∝ I <sup>2</sup>	Measure AC & DC Transfer instrument radi standard grade Some is used for measurement of ac without saturation

Q1 A pmmc instrument has a coil of dimensions 10mm x 8mm the flux density B in the air gap is 0.15 wb/m<sup>2</sup> if the coil is wound for 100 turns carrying a current of 5mA calculate  
 ① Deflecting torque  
 ② Deflection if the spring coil is 0.2 x 10<sup>-6</sup> N-m/degree

Sol<sup>n</sup>  
 ① T<sub>d</sub> = NBIA

= 100 x 0.15 x 5 x 10<sup>-3</sup> x 10 x 8 x 10<sup>-6</sup>

=  $\frac{100 \times 15 \times 5 \times 10 \times 8 \times 10^{-9}}{1000}$

750 x 8 x 10<sup>-9</sup> = 6000 x 10<sup>-9</sup> = 6 x 10<sup>-6</sup> N-m

② T<sub>d</sub> = T<sub>c</sub> = Kθ

6 x 10<sup>-6</sup> = 0.2 x 10<sup>-6</sup> x θ

θ = 30 degree

Sol<sup>n</sup>:

• If pure AC signal is send to pmmc like I = I<sub>m</sub> sin ωt and the pointer vibrates near to zero because of smooth of the instrument. The avg value of Sin ωt is 0.

• If spring is broken or damaged then the pointer will come to zero in that position in case of pmmc bcz current is passing through the spring. In all other case pointer move to max<sup>m</sup> point.

Q2 Due to Temp. Variation from 20°C Spring tension is reduced by 20% and magnetic field is reduced by


- ① 20%
- ② 10%

then the error in the instrument is

Sol<sup>n</sup> ①  $H \rightarrow 0.99K \cdot 0.8K$  &  $B \rightarrow 0.8B$   
 $\% \text{ error} = N \cdot \% B \cdot I \cdot A$   
 Isothermal


②  $H \rightarrow 0.8H$  &  $B \rightarrow 0.9B$   
 $0.8K \cdot 0 \rightarrow 140.9B \cdot I \cdot A$   
 $K \cdot \theta \text{ error} = T_A - T_c = 0.9 - 0.8 = 0.1 = 10\%$

error in the instrument is 10%

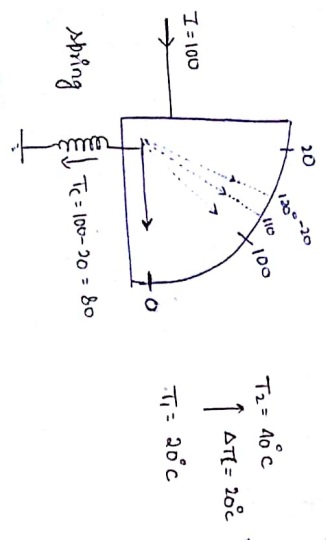

Enhancement of meters

① Ammeter 100mA

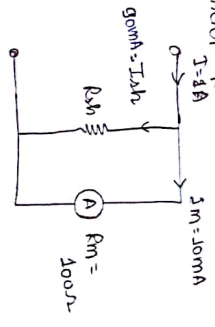


$$I_m = I \times \frac{R_{sh}}{R_{sh} + R_m}$$

$$R_{sh} = \frac{R_m}{\left(\frac{I}{I_m} - 1\right)}$$

$$R_{sh} = \frac{R_m}{m - 1}$$

$$V_m = I_m R_m = I_{sh} \cdot R_{sh}$$
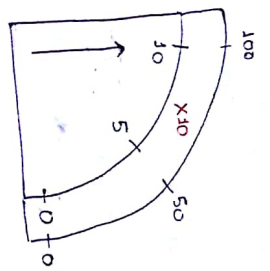
$$m = \frac{I}{I_m} = \text{multiplication factor}$$




Q3 A 100mA ammeter has meter resistance of 100Ω measures max. current of 10mA. Calc voltage drop across the meter and shunt resistance required.

- ① 100mA
- ② 1A

Sol<sup>n</sup> 3


①  $100 \times 10 \text{ mA} = R_{sh} \times 100 \text{ mA}$   
 $R_{sh} = \frac{1000 \text{ V} = 100 \text{ V}}{10} = 11.111 \Omega$

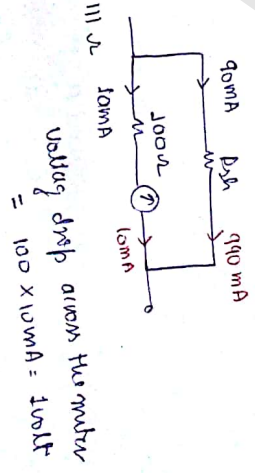②  $100 \times 10 \text{ mA} = R_{sh} \times 1000 \text{ mA}$   
 $R_{sh} = \frac{1000}{990} = \frac{100}{99} \Omega = 1.0101 \Omega$



Q2. D.C. meter has meter resistance of  $50\Omega$  measures F.S. current  $10\text{ mA}$ .  
 Shunt resistance is required for measurement of  $1\text{ amp}$ .  
 Another ammeter having meter resistance of  $100\Omega$  carrying F.S. current of  $10\text{ mA}$ . Find the shunt resistance required for measuring  $1\text{ amp}$  of current.  
 If these two meters are connected in parallel what is the max. in current able to measure through the combination.

Soln

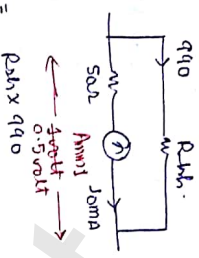


Amm 1 can bear  $0.5\text{ volt}$ , more than  $0.5\text{ volt}$  will damage the insulation

$$R_{sh} = \frac{500}{990} = 0.505\Omega$$

$$50 \times 10 = R_{sh} \times 990$$

$$V = 1\text{ volt}$$

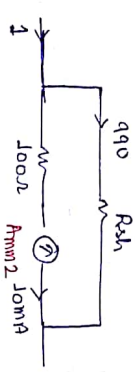


Ammeter 2 can bear max.  $1\text{ volt}$

$$100 \times 10 = 990 \times R_{sh}$$

$$R_{sh} = 1.01\Omega$$


For  $A_2$

$$0.5 = I \times 100$$

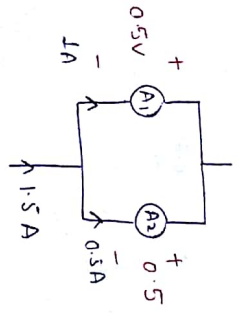

Note: If the ammeters are to be connected in parallel then the min. voltage among all the meters is applicable to set the parallel meters. So that withstanding the insulation level of the meter.

Asynton shunt :-

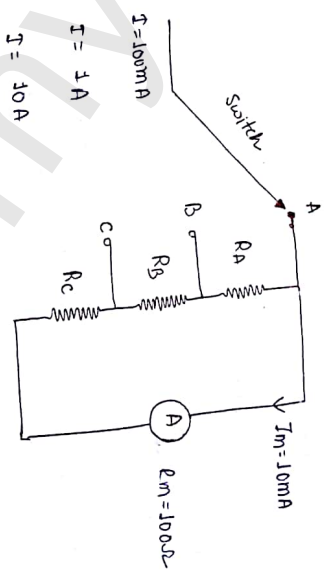

$I = 100\text{ mA}$   
 $I = 1\text{ A}$   
 $I = 10\text{ A}$

when current measured is high shunt resistance should low.

Shunt A:

$$m = \frac{I}{I_m} = \frac{100}{10} = 10$$

$$(R_m + R_s + R_p) = \frac{R_m}{m-1} = \frac{100}{9} \text{--- ①}$$

Switch at B:

$$m = \frac{I}{I_m} = \frac{1000}{10} = 100$$

$$R_B + R_C = \frac{R_A + R_m}{m-1} = \frac{R_A + 100}{100-1} \quad \text{--- (2)}$$

Switch at C:

$$m = \frac{I}{I_m} = \frac{10000}{10} = 1000$$

$$R_C = \frac{R_A + R_B + R_m}{m-1} = \frac{R_A + R_B + 100}{1000-1} \quad \text{--- (3)}$$

$$\text{eq}^n \quad (R_A + R_B + R_C) = \frac{100}{9} \quad \text{--- (1)}$$

$$(1) \quad R_A = \frac{11 \times 100}{11 \times 9} - \frac{R_A + 100}{9}$$

$$99 R_A = 1100 - (R_A + 100)$$

$$99 R_A + R_A = 1000$$

$$100 R_A = 1000$$

$$\boxed{R_A = 100 \Omega}$$

$$(1) \quad R_A + R_B = \frac{100}{9} - \frac{(110 + R_B)}{99}$$

$$10 + R_B = \frac{1100 - 110 - R_B}{99}$$

$$990 + 99 R_B + R_B = 10990$$

$$1000 R_B = 10990$$

$$R_B = \frac{1.1 \times 10^{-3}}{999} = 1.1 \text{ mA}$$


Put in (1)

$$10 + 11 \times 10^{-3} + R_C = \frac{100}{9}$$

$$R_C = 1.11 \text{ A}$$

Q6. Design a Ayrton shunt to provide an ammeter with current range of 1A, 5A, 10A with basic meter resistance of 50Ω and Full scale deflection current of 1mA

Sol<sup>n</sup>

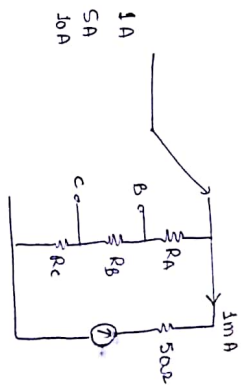

$$(1) \quad m = \frac{I}{I_m} = \frac{1000}{1} = 1000$$

$$R_{sh} = \frac{R_m}{m-1}$$

$$R_A + R_B + R_C = \frac{50}{1000-1} \quad \text{--- (1)}$$

$$(2) \quad m = \frac{5000}{1} = 5000$$

$$R_B + R_C = \frac{R_A + 50}{5000-1} \quad \text{--- (2)}$$

$$(3) \quad m = \frac{10000}{1}$$

$$R_C = \frac{R_A + R_B + 50}{10000-1} \quad \text{--- (3)}$$

$$R_A = \frac{50}{999} - \frac{(R_A + 50)}{9999}$$

$$R_A = 0.01 \text{ A}$$

$$R_B = 5 \text{ mA}$$


$$R_C = 5 \text{ mA}$$

Effect of Temperature on ammeter

By the addition of Swamp resistance in series with the meter Effect of temp is reduced.

Q → An ammeter has meter Resistance of 75Ω measures current up to 10mA the a meter is made of copper  $\alpha = 0.004/^\circ\text{C}$

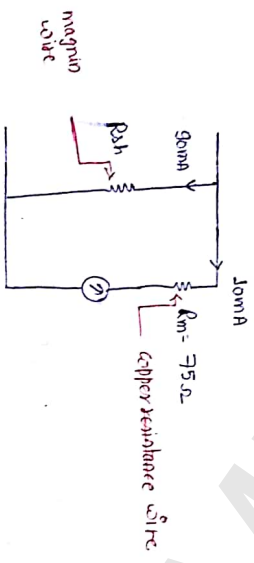
- ① How much of shunt is required for measurement of 100mA.
- ② Find the error in the meter if the temp' rise of  $1^\circ\text{C}$  the  $\alpha$  for magnet shunt is  $0.0015/^\circ\text{C}$
- ③ If a swamp resistance of 85Ω is connected in series to the meter find the error for temp' range of  $25^\circ\text{C}$  Swamp is made of magnet.



①  $90 \times R_{sh} = 10 \times 75$   
 $R_{sh} = \frac{750}{90} = \frac{25}{3} = 8.3 \Omega$

②  $\Delta T = 25$   
 $R_{m2} = R_{m1} [1 + \alpha \Delta T]$   
 $= 75 [1 + 0.004 \times 25]$   
 $R_{m2} = 82.5 \Omega$

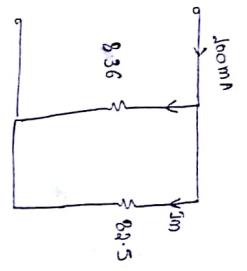
$R_{sh2} = \frac{10 \times 82.5}{90} = \frac{12.5}{9}$   
 $R_{sh2} = 8.3 [1 + 0.0015 \times 25] = 8.36$



$I_m = \frac{100 \times 8.36}{8.36 + 75}$   
 $= 9.295 \text{ mA}$  [measured value]

$\% \text{ error} = \frac{\text{MV} - \text{TV}}{\text{TV}} \times 100$

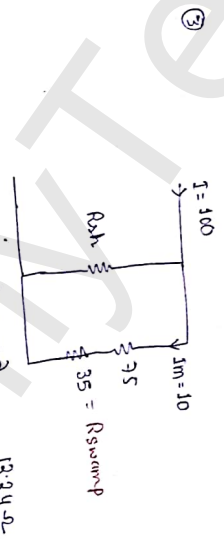
$= \frac{9.295 - 10}{10} \times 100$   
 $\% \text{ error} = -7.98 \%$



$R_{sh} = \frac{R_m}{(m-1)} = \frac{75 + 75}{(10 - 1)} = 12.24 \Omega$

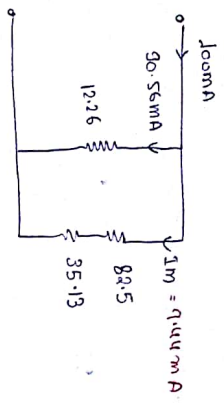$\Delta T = 25^\circ\text{C}$   
 $R_{sh2} = 12.24 [1 + 0.0015 \times 25] = 12.26 \Omega$   
 $R_{sw2} = 75 [1 + 0.0015 \times 25] = 82.5 \Omega$





$$I_m = \frac{100 \times 12.26}{82.5 + 35.13 + 12.26}$$

$$= 9.44 \text{ mA} = \text{measured}$$

$$\% \text{ error} = \frac{9.44 - 10}{10} \times 100$$

$$= -5.5\%$$

Note: ammeter which has minimum full scale value has higher sensitivity

Ex: these amm. A, B, & C are having a full scale value of 5A, 2A, & 1A then when the sensitivity of the meter is in mg order.

Soln: A B C

Note: In case of AC ammeter like MI, EMMC etc the shunt time constant and meter frame constant are to be maintained equal for making the instrument independent of frequency.

A MI ammeter has meter resistance of 1000 and inductance of 20 mH so designed to work independent of freq then the time const of shunt is \_\_\_\_\_ sec.



$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{20} = 0.2 \text{ msec}$$

Enhancement of voltmeters

$$m = \frac{V}{V_m}$$

$$R_s = R_m [m-1]$$
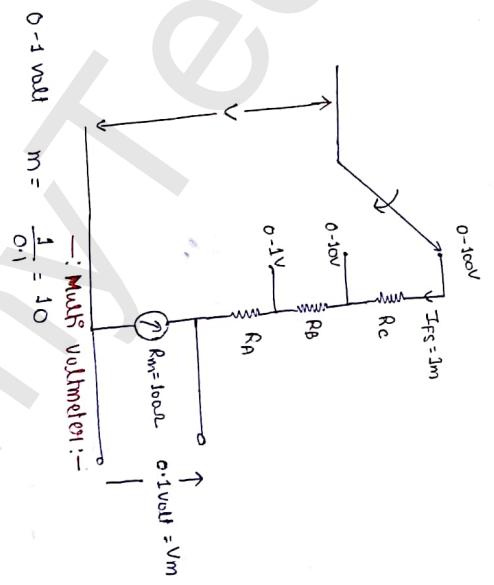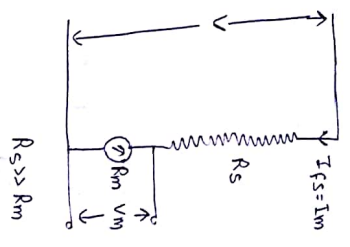
$$S_u = \frac{1}{I_{FS}} = \frac{(R_s + R_m)}{V}$$



0-1 volt  $m = \frac{1}{0.1} = 10$

RA =  $R_m [m-1] = 100 [10-1] = 900 \Omega = 0.9 \text{ K}\Omega$

RA + RB =  $100 \left[ \frac{10}{0.1} - 1 \right]$

$100 [99] = 9900 \Omega = 9.9 \text{ K}\Omega$

RA + RB + RC =  $100 [1000-1] = 99900 \Omega$

RC =  $99900 - 9900 = 90000 = 90 \text{ K}\Omega$



$R_B = 9900 - 900 = 9 \text{ K}\Omega$

$Q = HV$

am =

Q8. Two voltmeter A and B having sensitivities of  $1k\Omega/V$  and  $2k\Omega/V$  and each has a range of 0-100 volts are connected in series. What is the maximum voltage is able to measure by this series combination.

Soln:

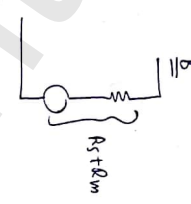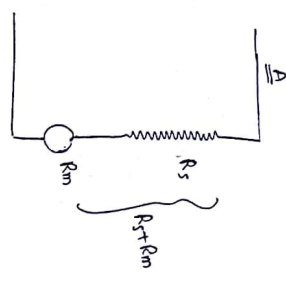

$S_v = 1k\Omega/V$

$I_{FS} = 1mA$

$V = 0-100V$

$(R_s + R_m) = \frac{100}{1} = 100k\Omega$


$S_v = 2k\Omega/V$

$I_{FS} = 0.5mA$

$V = 0-100V$


$(R_s + R_m) = \frac{100}{0.5} = 200k\Omega$

Minimum  $I = 0.5mA$

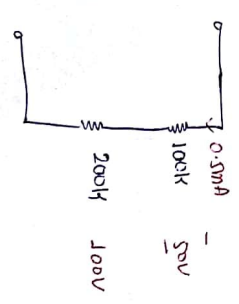


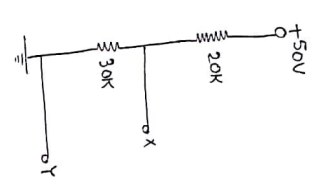Q9

Two voltmeters having a range of 30V and sensitivities of  $1k\Omega/V$  and  $1m\Omega/V$  are used to measure voltage across  $30k\Omega$ . Shown in fig find the reading of each meter and error in each meter.




$I_{FS1} = 1mA$

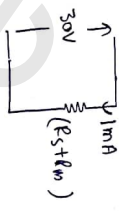


$30 = 1mA (R_s + R_m)$

$R_s + R_m = 30k\Omega$

$I_{FS2} = 1\mu A$

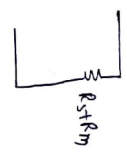

$R_s + R_m = 30M\Omega$

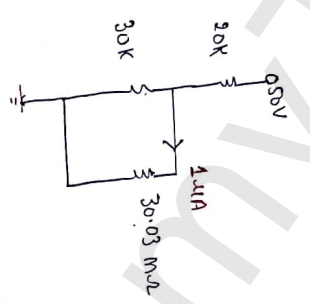

$$TV = \frac{50 \times 30}{50} = 30V$$


$$MV = \frac{30 \times 0.3}{30} = 0.3V$$

$$\therefore \text{error} = \frac{0.3}{30} = 0.1\%$$

$V_{T_{max}} = TV = \frac{50 \times 30}{30+20} = 30V$


(1) A:  $S_V = 1k\Omega/V$ ,  $I_T = 1mA$   
 $0-30V$   
 $R_S + R_m = V \cdot S_V = 30k\Omega$

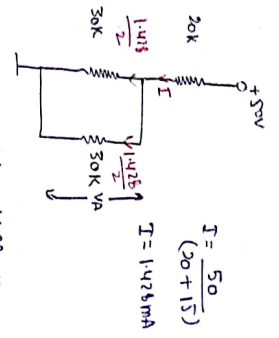(2) B:  $S_V = 1mA/V$   
 $0-30V$   
 $R_S + R_m = 30mA$



$I = \frac{50}{(20+15)}$   
 $I = 1.428mA$   
 $V_A = \frac{1.428 \times 30}{2}$   
 $= 21.428V$   
 $= \text{Measured}$


$\% \text{ error} = -0.856\%$

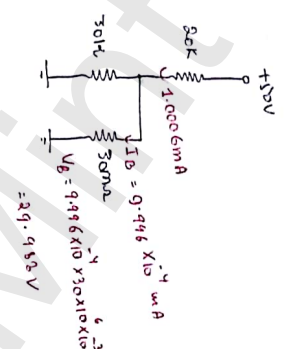

$R_S + R_m = 30k\Omega$   
 $\% \text{ error} = \frac{29.988 - 30}{30} \times 100$   
 $= -0.04\%$

$\% \text{ error} = -0.04\%$

- voltmeter having high resistance, have high sensitivity
- Ammeter must have high resistance, ideal cond<sup>n</sup> is  $\infty$  and low op resistance
- voltmeter with higher sensitivity has high resistance so that loading effect is less and accuracy is higher.
- If any connecting channel is used to transfer the voltage sig want have high i/p resistance and low op resistance so that loading effect is less
- A buffer's amp<sup>r</sup> (CC), op amp has  $R_i = \infty$  and,  $R_o = 0$  so that there is no attenuation of sampled signal i.e gain = 1 (in CC)

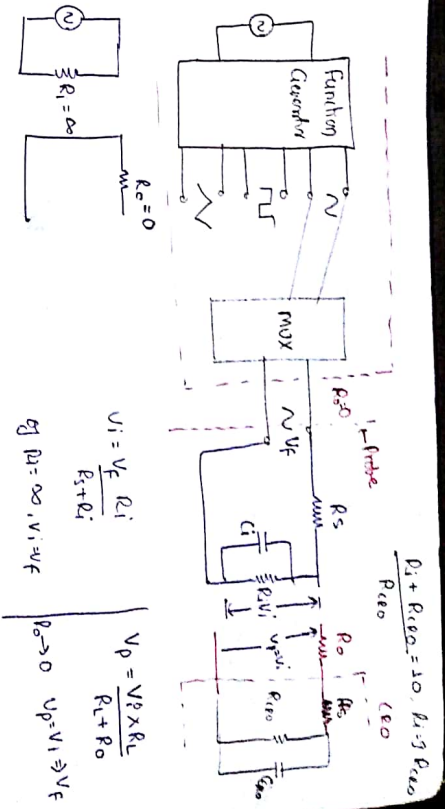

$V_i = V_c \frac{R_i}{R_S + R_i}$   
 eq (2)  $\rightarrow \infty, V_i = V_c$   
 $V_p = \frac{V_i \times R_L}{R_L + R_o}$   
 $V_p \rightarrow V_i \rightarrow V_c$

Note: Probe is used to transfer function generator op signal to the CRO. The op resistance of the probe must be of low value (practical value: 50 $\Omega$ ). To avoid loading effect the resist<sup>n</sup> is used i.e  $\frac{R_{probe} + R_{CRO}}{R_{CRO}}$

Function gen<sup>r</sup> is delivering different signal with wide range of freq<sup>s</sup> from Hz to MHz. These signals must pass through the probe i.e probe must be independent of freq<sup>s</sup> by maintaining time const<sup>t</sup> of the probe and CRO are to be equal.

$R_{probe} \text{ (meter)} = R_{CRO} \cdot C_{CRO}$

A CRO has i/p resistance of 1M $\Omega$  and i/p capacitance of 25 pF parallel to the resistance.

Q Design a 10V probe which is connected via function Gen<sup>r</sup> and CRO  
 If it has tip resistance of 1mA and capacitance impedance of 55 pF  
 parallel to the resistance


sol<sup>n</sup>  
 $9X \text{ Probe} = 25pF \times 1 \text{mA}$   
 $\text{Capacitor} = 2.77pF$   
 $R_{probe} = 9R_{tip}$

Note\* Digital multimeter uses operational amplifiers, buffer amp<sup>r</sup> which  
 has higher tip resistance. As that loading effect is very less  
 bcz sensitivity is higher, compared to analog multimeter

an AC voltmeter is made independent of supply frequency by connecting  
 capacitance in parallel to the series multiplier resistance

$$C \approx 0.41 \frac{L_m}{R_s^2}$$

$$R_s C \approx 0.41 \frac{L_m}{R_s}$$

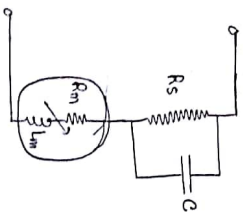


Q An AC voltmeter has meter resistance of 100Ω and inductance of  
 10mH is connected with series multiplier resistance of 10kΩ  
 how much of compensating capacitance is required for making  
 meter independent of freq

$$C = \frac{0.41 \times (10 \times 10^3)}{100 \times 10^6}$$


$$C = \frac{41 \times 10^3 \times 10^{-6}}{10^8} = 41 \times 10^{-16} \text{ F}$$

Q How voltmeters having ABC are specified

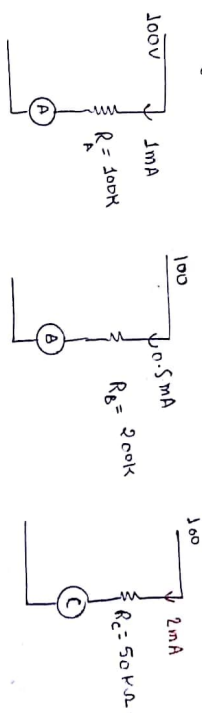- A: 0-100V, 1mA/V
  - B: 0.5mA, 0-100V
  - C: 50kΩ, 0-100V
- asked in the working of meters A, B, C of tip voltage is 250V  
 if they are connected in series.



We can't send more than 0.5mA.

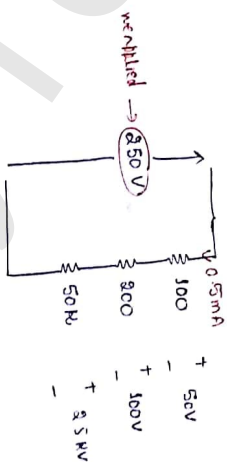

but  $50 + 100 + 80 = 135V$  so we can't apply more than  
 $135V$   
 $V_{max} = 135V$

Maximum measurable voltage is 135V

MI meters

Q Inductance of moving iron instrument is given by  $L = (12 + 6\theta - \theta^2) \mu H$  where  $\theta$  (deflection in radian) From zero position. Spring constant is  $12 \times 10^{-6} \frac{N \cdot m}{rad}$ . Calculate deflection in radian and degree for a current of 8 amps.

Sol<sup>n</sup>  $K\theta = \frac{I^2}{2} \frac{dL}{d\theta}$

$12 \times 10^{-6} \times \theta = \frac{(8)^2}{2} [6 - 2\theta] \times 10^{-6}$

$\frac{24}{6} \theta = 6 - 2\theta$

$\theta \left( \frac{24}{6} + 2 \right) = 6$




$\theta \frac{12}{3} = \frac{6}{3} \Rightarrow \theta = 2$

$\theta = \frac{19}{6} = 3.16$

$\theta = \frac{8 \times 6}{19} = \frac{48}{19} = 2.53 \text{ rad}^n$

$\theta = 144.24^\circ$

Electrostatic motor

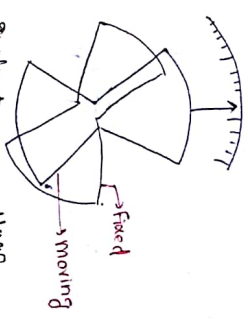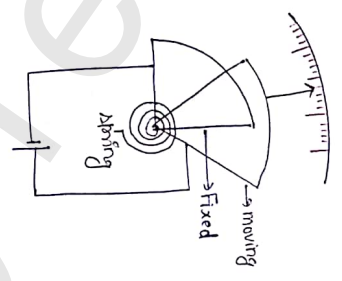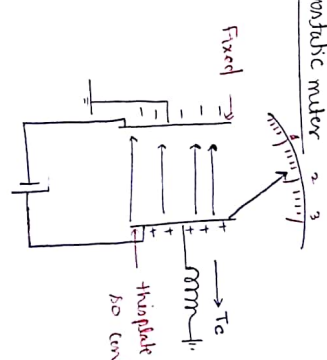

Substant + ES voltage  $T_d = \frac{1}{2} I^2 \frac{dL}{d\theta} \Rightarrow mI$


$T_c = K\theta$   
 $T_d = T_c$

$V_m = \frac{V \cdot C_s}{(C_s + C_m)}$

$\frac{C_s + C_m}{C_s} = \frac{V}{V_m} = m$

$1 + \frac{C_m}{C_s} = m$

$C_s = \frac{Q_m}{(m-1)}$

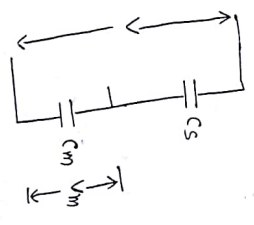


Condition for Linearity

$M \propto \theta \frac{dI}{d\theta} = \text{constant}$

Emmic  $\Rightarrow \theta \frac{dM}{d\theta} = \text{constant}$

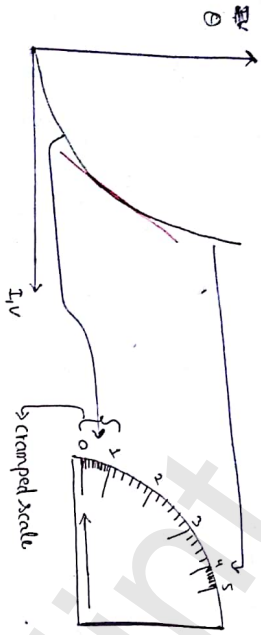Es  $\Rightarrow \theta \cdot \frac{dC}{d\theta} = \text{const}$



$\theta \propto I^2, \theta \propto V^2$

Q In Electrostatic voltmeter controlled by a spring a spring ckt of  $4 \times 10^{-6}$  Nm and has a full scale deflection of  $90^\circ$  when voltage of 1500 volts is applied to it, the capacitance at zero voltage is 10 pf. find the capacitance when the pointer indicates 1500 volts

Soln  $\theta = \frac{\pi}{2} V^2 \frac{dC}{d\theta}$

$4 \times 10^{-6} \theta = \frac{1}{2} \times 1500^2 \times$

$4 \times 10^{-6} \times \frac{\pi}{2} = \frac{1}{2} \times 1500^2 \times \frac{dC}{d\theta}$

$\frac{4 \times 10^{-6} \times \pi}{(1500)^2 \times 2} = \frac{dC}{d\theta} = 5.585 \times 10^{-12}$

$0V \rightarrow 10 \text{ pf}$

$\theta = \frac{\pi}{2} \rightarrow 1500$

$dC = 5.585 d\theta$

$C = 5.585 \theta + \text{const}$   
at  $\theta = 0$


$C = 5.585 \theta + 10$

$C = 5.585 \times \frac{\pi}{2} + 10$

$= 18.79 \text{ pf}$

Q capacitance of 0-1000V, electrostatic voltmeter is uniformly from 36 to 42 pf. from 0 to full scale deflection. It is required to extend the range of voltmeter to 10kV by using an external series capacitor. calculate the value of series capacitor.

$m = \frac{10000}{1000} = 10$

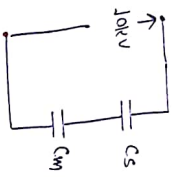

before we could measure 1000V by adding  $C_s = 4.66 \text{ pf}$  we can measure 10kV.

$C_s = \frac{C_m}{(m-1)} = \frac{36}{9} = 4 \text{ pf}$

$C_s = \frac{C_m}{m-1} = \frac{42}{9} = 4.667 \text{ pf}$  Answer

bcz we need to take higher value



capacitive voltage divider [CVT]

so working on the principle of electrostatic

voltmeter used for measurement of large bus bars or feeder voltages.

like the 11, 33, 132 kV substation etc

Wattmeter

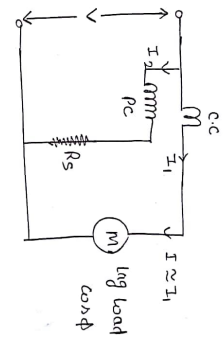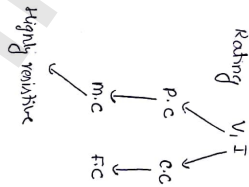



$$T_d = I_1 I_2 \cos \alpha = k \theta$$

$$= I_1 \cdot V \cos \phi \frac{dM}{d\theta}$$

$$T_d = \frac{P_{avg}}{R_s} \cdot \frac{dM}{d\theta} = k \theta$$

$$\theta \propto P_{avg}$$

P.C containing inductance (Lp):

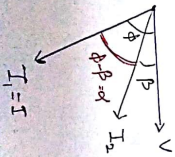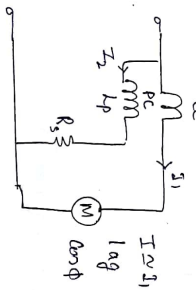

$$P_T = VI \cos \phi$$

$$P_m = VI \cos \beta \cos (\phi - \beta)$$

$$\text{Correction Factor } [C_F] = \frac{\cos \phi}{\cos \beta \cos (\phi - \beta)} = \frac{P_T}{P_m}$$

$$\% \text{ error} = \frac{P_m - P_T}{P_T} \times 100 \approx \tan \phi \tan \beta \times 100$$

$$\text{percentage error} = P_m - P_T = \tan \phi \tan \beta \times P_T$$

$$C_F = \frac{1}{1 + \tan \phi \tan \beta}$$

$\phi = \text{P.F. angle of load}$

Error in watts:

① Lag Load:  $\phi = +ve$

$$P_e = P_m - P_T = VI \sin \phi \tan \beta$$

$$P_m = (P_T + VI \sin \phi \tan \beta)$$

$$P_m > P_T$$

$\therefore r = +ve$

② Lead load  $\phi = -ve$

$$P_e = P_m - P_T = -VI \sin \phi \tan \beta$$

$$P_m = P_T - (VI \sin \phi \tan \beta)$$


$$P_m < P_T$$

$\therefore r = -ve$


error in watts due to  $L_p$

Errors due to potential coil inductance

① P.C. on source side

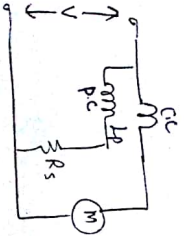

② P.C. on load side

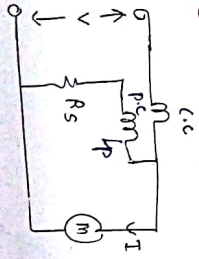

$$P_m = P_T + I_m^2 R_s$$

$$\therefore r = \frac{I_m^2 R_s}{P_T} \times 100$$

$r_c = \text{C.C. inductance}$

\* \* \*  
sketch total error on source side = error due to  $L_p$  + error due to current coil

$$VI \sin \phi \tan \beta + I_m^2 R_s$$

$$P_m = P_T + \frac{V^2}{R_s} \sin^2 \phi$$

$$\therefore r = \frac{V^2}{R_s} \sin^2 \phi \times 100$$


sketch total error on load side = error due to  $L_p$  + error due to P.C.

Q. An electrodynamometer is used for measurement of power in a single phase d.c.t. the load voltage is 100 volts and the load current is 10 amperes. at a p.f. of 0.2. wattmeter voltage d.c.t. has a resistance of 3 kΩ and inductance of 30 mH calculate the % error in the wattmeter reading when pressure coil is connected

① on the supply side

② on the load side

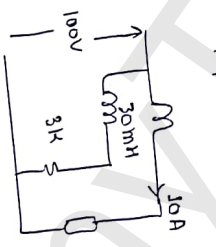The current coil has a resistance of 0.1 Ω and negligible inductance. The  $\cos \phi$  is 0.2.



$$\cos \phi = 0.2$$

$$\phi = 98.116^\circ$$

$$P = \text{true} = \frac{10 \times 10 \times 0.2}{1000 \times 3000}$$

$$\beta = 0.179^\circ$$

① error when P.C. on supply side

$$= (50)^2 \times (10)^2 \times r_c = 100 \times 0.1 + VI \tan \phi \sin \phi$$

$$V_L = 10 + 100 \times 10 \times 3.14 \times 10^{-3} \times 0.9799$$

$$= \frac{11113.079}{100 \times 10 \times 6.2} = 180.540 \quad 6.5380\%$$




on load side

$$= \frac{V^2}{R_S} + V I \sin \phi \tan \phi$$

$$= \frac{(100)^2}{8000} + 3.076$$

$$= \frac{6.355 \times 100}{V I \cos \phi} \therefore \frac{635.5 \times 100 \times \cos \phi}{100 \times 10 \times 0.2} = 3.166 \angle 10^\circ$$

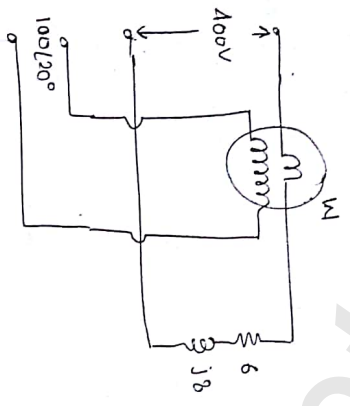Q for a following krt calculate reading of wattmeter




$$P = VI \cos \phi$$


$$I = \frac{400}{(6+j8)} = \frac{400}{\sqrt{64+36} \angle \tan^{-1} \frac{8}{6}} = 40 \angle -53.13^\circ$$

$$P = 100 \times 40 \times \cos(93.13^\circ)$$

$$= 1160.80 \text{ watt}$$

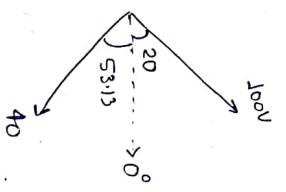

Q find out wattmeter reading

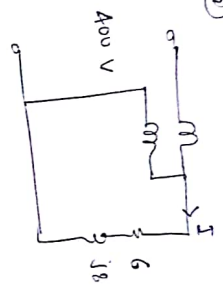

$$V_{WT} = 100 \times$$


$$I = \frac{400}{6+j8} = 40 \angle -53.10^\circ$$

$$P = 400 \times 40 \times \cos 53.10^\circ$$

$$P = 48240.168 \text{ W}$$

$$= 9600 \text{ watt}$$

(3)

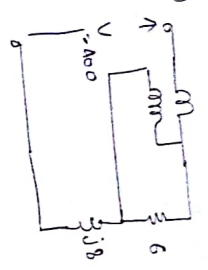


$$I = \frac{400}{6+j8} = 40 \angle -53.10^\circ$$

$$V = 6 \times 40 \angle -53.10^\circ$$

$$= 240 \angle -53.10^\circ$$

$$P = 240 \times 40 \times \cos 0^\circ$$

$$P = 9600 \text{ W}$$

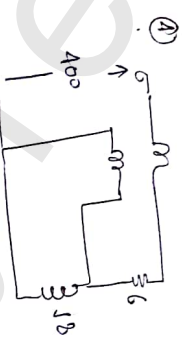

$$I = 40 \angle -53.10^\circ$$

$$V = 40 \angle -53.10^\circ \times 2 \angle 90^\circ$$

$$V = 80 \angle 36.9^\circ$$

$$P = 40 \times 80 \times \cos 90^\circ$$

$$P = 0 \text{ watt}$$

PC  $\Rightarrow V = V_0 + V_{m1} \sin(\omega t + \alpha_1) + V_{m2} \sin(2\omega t + \alpha_2) + \dots$

CC  $\Rightarrow I = I_0 + I_{m1} \sin(\omega t + \beta_1) + I_{m2} \sin(2\omega t + \beta_2) + \dots$

wattmeter reading =  $P_{avg}$

$$= V_0 I_0 + \frac{1}{2} [V_{m1} I_{m1} \cos(\alpha_1 - \beta_1) + V_{m2} I_{m2} \cos(\alpha_2 - \beta_2) + \dots]$$

Ex:  $V = 10 + 5 \sin(\omega t + 45^\circ) + 2 \sin(\omega t + 130^\circ)$


$I = 8 + 4 \sin(\omega t - 15^\circ)$

$P = 10 \times 8 + \frac{5 \times 2 \times 4}{\sqrt{2} \sqrt{2}} \cos 45^\circ$


$80 + 4 \times \frac{1}{\sqrt{2}}$

$P = 82.828W$

3 φ wattmeters




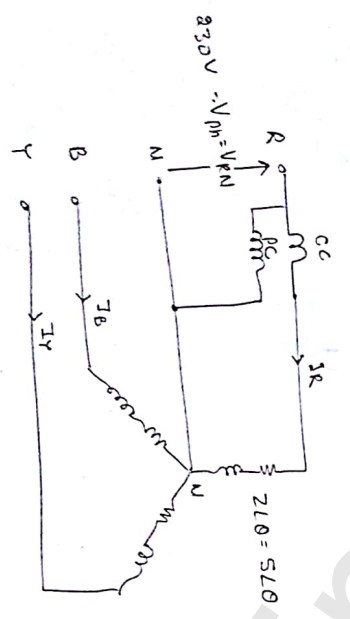


$W_1 = V_{RN} I_{CC} \cos(\angle V_{RN} - I_{CC})$   
 $= |V_{RN}| |I_{CC}| \cos L\theta$   
 $= 330 \times \frac{230}{5} \cos 30^\circ$   
 $= 4162.55 \text{ watt}$

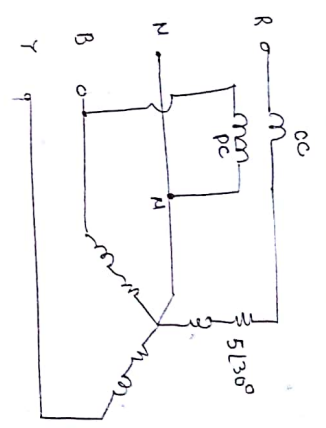


$W_1 = 330 \times \frac{230}{5} \cos(120 + 30^\circ)$   
 $= -916W$

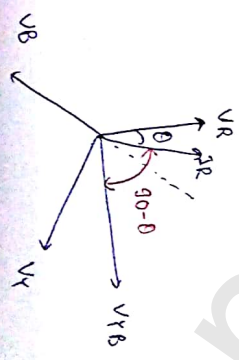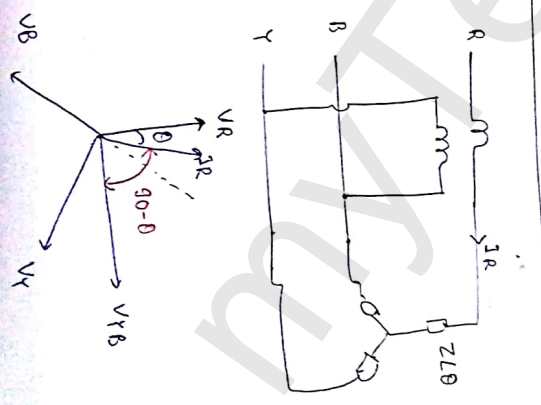
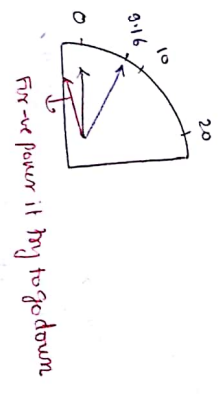
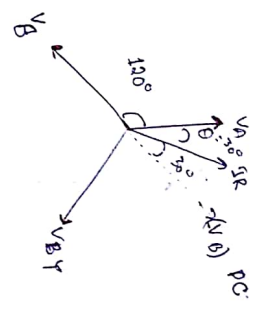
3 φ wattmeter reads -ve value. Suggests either the cc or cc terminals interchanged of the power A. Correct with -ve sign.



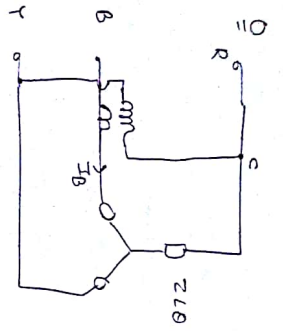$W_1 = V_{RB} I_{CC} \cos(90 - \theta)$   
 $W = V_L I_L \sin \phi$   
 → wattmeter measuring reactive power.




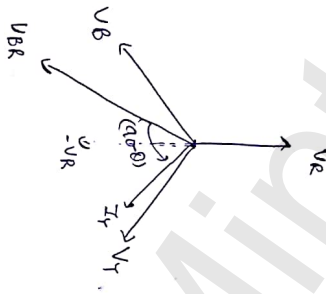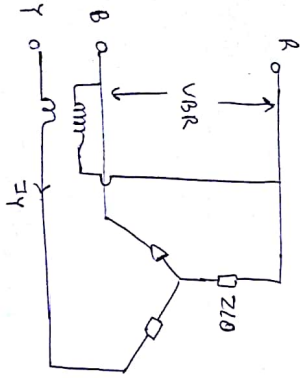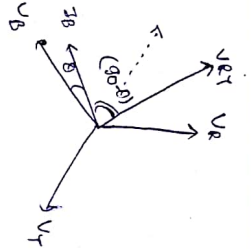
$$W = I_B \times V_{RY} \times \cos(90^\circ - \theta)$$





if current coil is connected to one phase or phase coil is connected to remaining two phases then the wattmeter measures active power

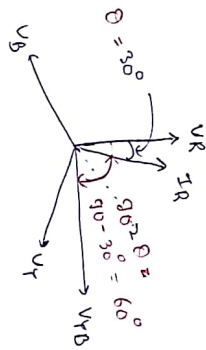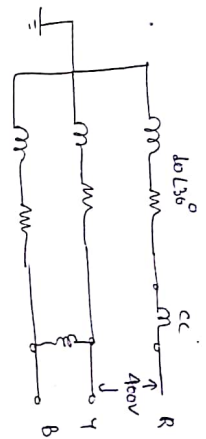2) For the ckt shown in the figure find the wattmeter reading



$$I = \frac{400}{\sqrt{3} \cdot 10 \angle 30^\circ} = \frac{40 \angle -30^\circ}{\sqrt{3}} = 23.1 \angle -30^\circ$$

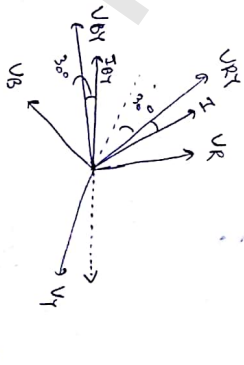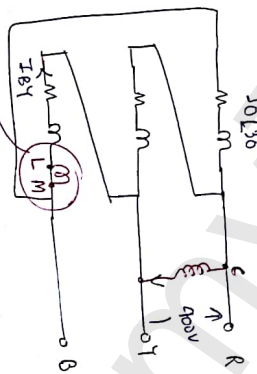
$$W = V_{RY} \times I_R \times \cos(90^\circ - \theta) = 400 \times \frac{40}{\sqrt{3}} \times \sin 30^\circ = \frac{400 \times 40 \times \frac{1}{2}}{\sqrt{3}} \text{ watt}$$



Final Ans  
of given L problem


$$W = 400 \times 40 \times \cos 30^\circ = 400 \times 40 \times \frac{\sqrt{3}}{2} = 13856.4 \text{ watt}$$

Q

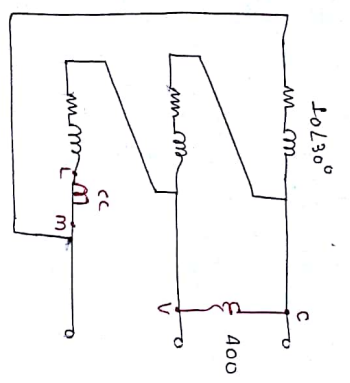


Find loading of each motor

Sol<sup>n</sup>

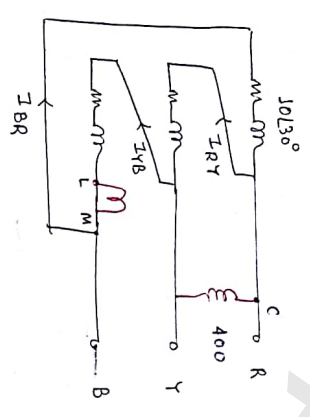



$$|I_{RY}| = \frac{400}{10} = 40$$

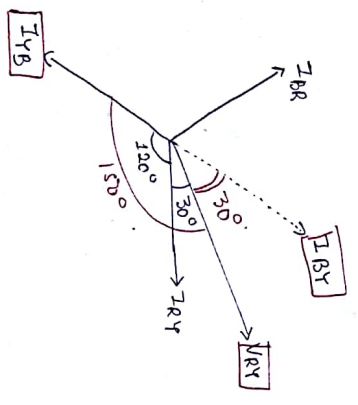


$P = V_{RY} I_{RY} \cos 150^\circ = \text{-ve power.}$   
 $P = 400 \times 40 \times (-0.866) = -13.85 \text{ kW}$   
 $P = 400 \times 40 \times \cos 30^\circ = 13.85 \text{ kW}$

-ve power, so total loading by either winding is external CC terminal or PC terminal.

Q

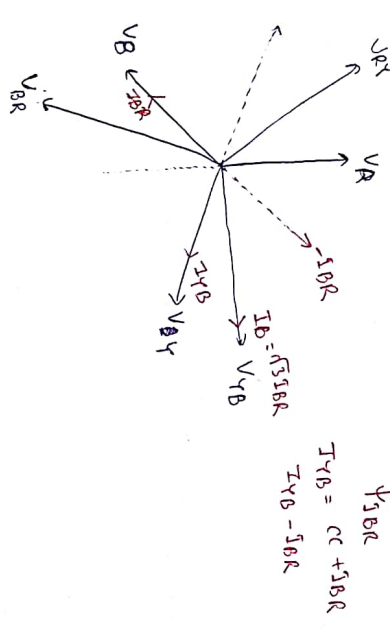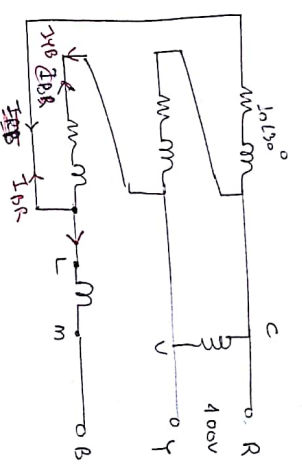

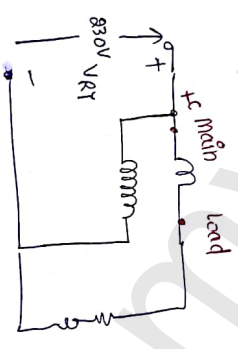
$$= V_{RY} \cdot \sqrt{3} I_{BR} \times \cos 120^\circ$$



In external coil main = +ve terminal lead = -ve terminal  
 In pressure coil C = +ve terminal V = -ve terminal


Q

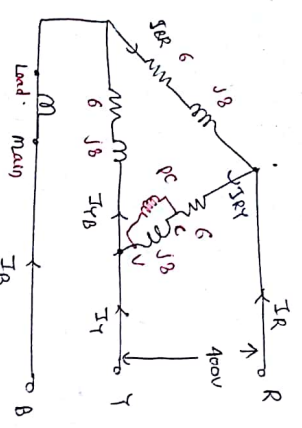

Soln

$6 + j8$

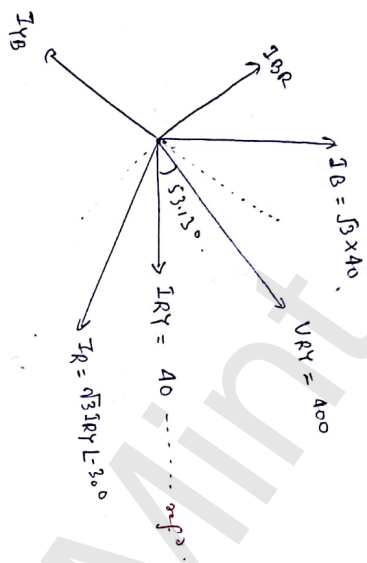$\phi = \tan^{-1} \frac{8}{6} = 53.13^\circ$



$I_{RY} = \frac{400}{10\sqrt{3} \times 13} = 40 \angle -53.13^\circ$

$V_{p.c} = \sqrt{3} \times 40 = 320 \angle 90^\circ$


$W = 3 \times 320 \times 40 \times \cos 0^\circ$   
 $W = 390 \times 40 \times \sqrt{3}$

$W = 22.17 \text{ kW}$

Instrument Transformer

- CT  $E_1$  in phase with  $I_{20}$
- PT  $I_{20}$

$I_2$  lag  $E_2$  by  $\phi$

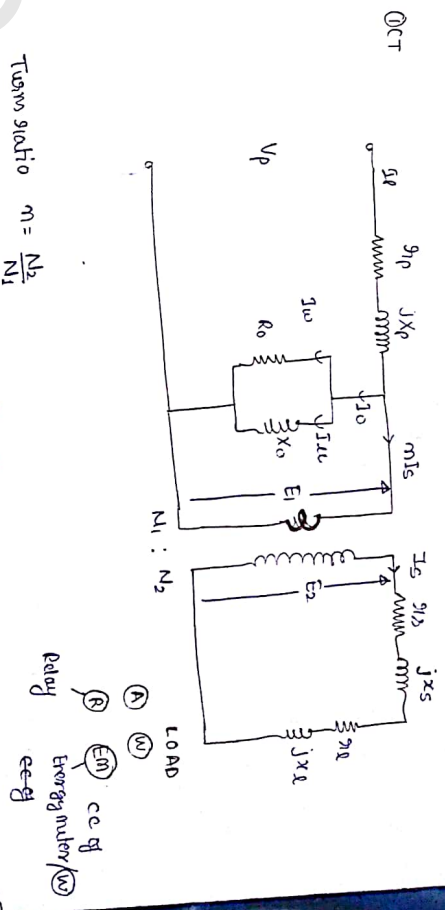


LOAD  
 (R) (L)  
 Error meter (W)  
 cc of  
 relay

Turns ratio  $m = \frac{N_2}{N_1}$

Nominal ratio  $= k_n = \frac{I_p}{I_s} = \frac{I_0 + m I_s}{I_s}$

Actual / Transformation ratio  $= R = \frac{I_p}{I_s}$

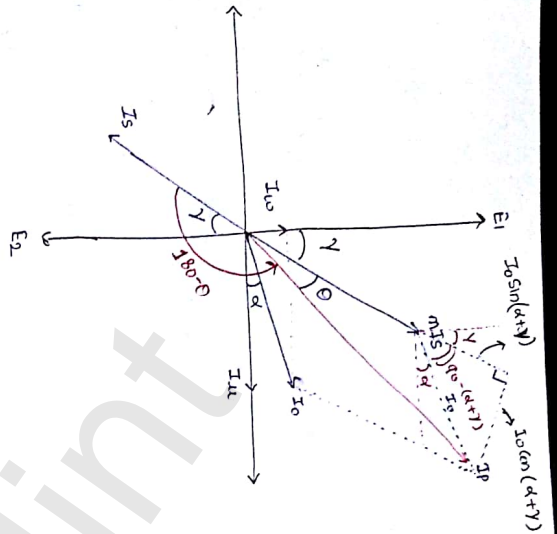$\phi = \text{secondary burden angle}$   
 $= \tan^{-1} \left( \frac{X_2 + X_s}{R_2 + R_s} \right)$



Transformation ratio (R)

Q If  $\gamma \neq 0$

$$R = \frac{I_1}{I_2} = \frac{n + \frac{I_0 \sin(\alpha + \gamma)}{I_S}}{n + \frac{I_0 \cos(\alpha + \gamma)}{I_S}}$$

$$= \frac{n + \frac{I_0 \sin \alpha \cos \gamma + I_0 \cos \alpha \sin \gamma}{I_S}}{n + \frac{I_0 \cos(\alpha + \gamma)}{I_S}}$$


$$R = \frac{n + \frac{I_0 \cos \alpha \sin \gamma + I_0 \sin \alpha \cos \gamma}{I_S}}{n + \frac{I_0 \cos(\alpha + \gamma)}{I_S}}$$

← valid for all  $\gamma$  except  $\gamma = 0$

Q If  $\gamma = 0$   
(purely resistive burden)

Assume  $I_0 \ll n I_S$
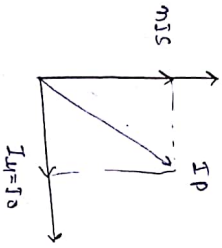
$$R = \frac{I_1}{I_2} = \frac{\sqrt{(n I_S)^2 + I_0^2}}{I_S}$$



Q3) phase angle error ( $\theta$ )

assuming  $I_0 \sin(\alpha + \gamma)$  is very small

$$\tan \theta \approx \theta \approx \frac{I_0 \cos(\alpha + \gamma)}{n I_S} \dots \text{Radian}$$

$$\theta \approx \frac{I_0 \cos \alpha \cos \gamma - I_0 \sin \alpha \sin \gamma}{n I_S}$$

$$\theta \approx \frac{I_0 \cos \alpha \cos \gamma - I_0 \sin \alpha \sin \gamma}{n I_S} \dots \text{Radian}$$

← valid for all values of  $\gamma$

Phase angle b/w  $I_1$  &  $I_2 \Rightarrow (180 - \theta) \times \frac{180}{\pi}$  degree





Q4) Ratio error ( $\sigma$ ):

$$\sigma = \frac{k_n - R}{R} \times 100$$

Q5) Ratio correction factor

$$RCF = \frac{R}{k_n} \rightarrow \text{Actual ratio}$$

← Nominal ratio

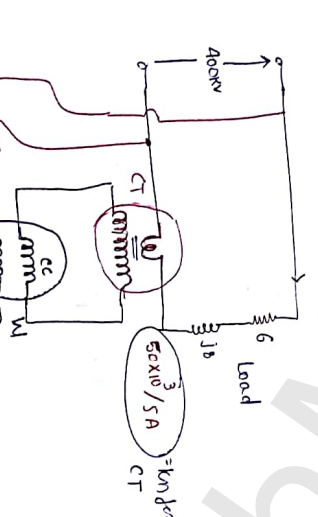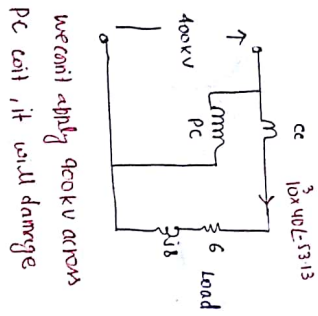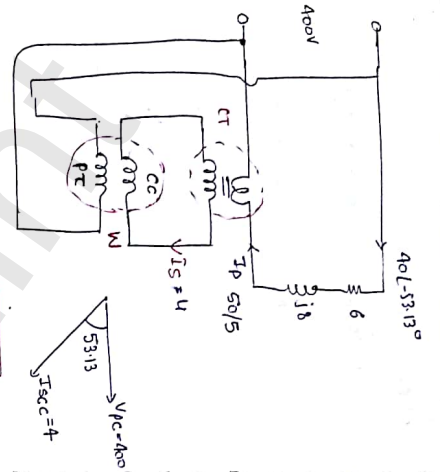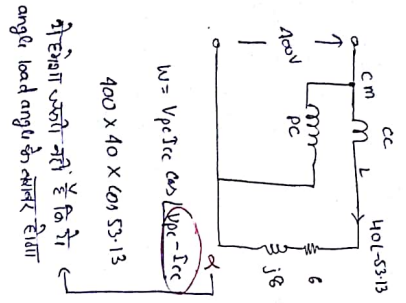

W = 100 x 4 x cos 53.13 x CT stick

400 kv/100v = Km for PT

adding errors (Ducto error)

For CT (-) ratio error

$K_m = \frac{I_p}{I_s}$

$R = \frac{I_p}{I_s}$

$RCF = \frac{R}{K_m}$

$R = (RCF) \times K_m$

$\frac{I_p}{I_s} = (RCF) \times \left(\frac{I_p}{I_s}\right)$


True cos phi measured

For PT (-)


$\frac{V_p}{V_s} = R = RCF \times \frac{V_p}{V_s} = K_m$

Power measurement using wattmeter including errors in CT and PT and Potential coil inductance

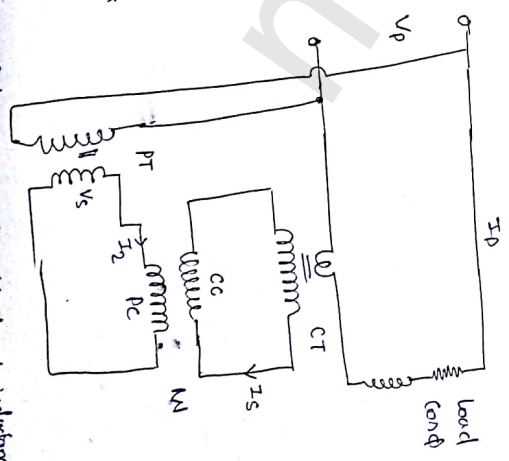- $V_p$  = Voltage across the load
- $I_p$  = load current
- $\phi$  = pf angle of load
- $V_s$  = voltage across secondary of PT
- $I_s$  = current in the secondary of CT
- $I_2$  = current in the primary coil of wattmeter
- $\alpha$  = phase angle b/w CT current & PC voltage of wattmeter
- $\theta$  = phase angle error of CT




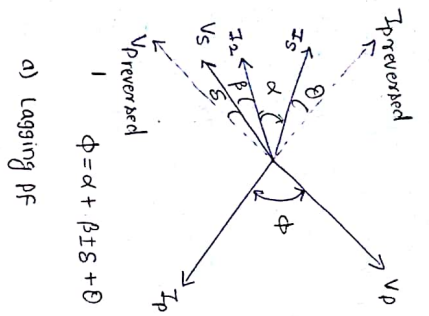$\theta$  = angle by which  $I_2$  lags  $V_s$  due to inductance of PC



a) Lagging PF

$$\phi = \alpha + \beta + \theta$$

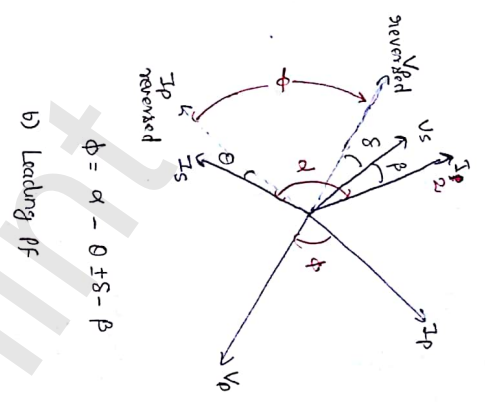

b) Leading PF

$$\phi = \alpha - \theta + \beta$$

$$\phi = \alpha + \beta + \theta + \theta$$

$$\phi = \alpha + \beta - \theta + \theta$$

$$\phi = \alpha - \beta - \theta - \theta$$

$$\phi = \alpha - \beta + \theta - \theta$$

S (+ve) } Lagging PF

S (-ve) } Leading PF

$$C_f = \text{Correction factor} = K = \frac{\cos \phi}{\cos \beta \cos \alpha}$$

$$\alpha = \phi - \beta - \theta - \theta$$

$$\alpha = \phi + \beta + \theta + \theta$$

Lagging PF (with S (+ve))  
 Leading PF (with S (-ve))

True Power =  $K \times$  actual ratio  $\times$  actual ratio  $\times$  wattmeter reading

$$\text{True Power} = K \times \left[ \frac{R_{CT}}{g_{CT}} \right] \times \left[ \frac{R_{CT}}{g_{PT}} \right] \times \left[ \frac{\text{nominal ratio}}{g_{CT}} \right] \times \left[ \frac{\text{nominal ratio}}{g_{PT}} \right] \times \left[ \text{wattmeter reading} \right]$$

$$\left[ \text{True Power} \right] = K \times \left[ \frac{R_{CT}}{g_{PT}} \right] \times \left[ \frac{R_{CT}}{g_{CT}} \right] \times \left[ \frac{\text{kn of } g_{CT}}{C_T} \right] \times \left[ \frac{\text{kn of } g_{PT}}{C_{PT}} \right] \times \left[ \text{wattmeter reading} \right]$$

Reading of 400 watts is indicated on a 100 volt, 5 amp wattmeter used in connection with PT and CT of nominal ratio 100 and 20 respectively. If primary pressure coil has ratio of 400 and induction of 20 mV the ratio and phase angle errors of PT is +1% and 50' (50/60) degrees and CT is -0.5% and 100' (100/60) degrees respectively calculate true value of the power measured the load phase angle is 60 degrees lagging and f is 50 Hz.

Given Wattmeter reading = 400 W

$$K_n = g_{CT} = 20$$

$$K_n \text{ of PT} = 100$$

$$\sigma = \pm \text{kr PT} = 1\%$$

$$R = 99.0099$$

$$R \cdot 0.01 = 99 - R$$

$$R \cdot 100 = 20$$

$$R = 20/100$$

$$R_{CT} \text{ for PT} = \frac{R}{K_n} = \frac{99.0099}{100} = 0.990099$$



For PT = 1%

$$\sigma = \frac{kn-R}{R} \Rightarrow \cos \phi = \frac{(100-R)}{R} \quad R = 99.0999$$

$$(RCF)_{PT} = \frac{A}{km} = \frac{99.0999}{100} = 0.99099$$

$$\sigma_{PT} = -\frac{15}{100} = -\frac{20-R}{R}$$

$$-15R = 2000 - 400R$$

$$2000 = 150R \quad R = 13.33$$

$$\tan \beta = \frac{R \tan \phi}{R_s}$$

$$K = C_f = \frac{\cos \phi}{\cos \alpha \cdot \cos \beta} = 0.9506$$

$$\phi = 60^\circ$$

$$\beta = 0.89^\circ$$

$$S = 0.83^\circ$$

$$\theta = 1.563^\circ$$

$$\Phi = \alpha + \beta - S + \theta$$

$$\alpha = 58.226^\circ$$

$$(RCF)_{CF} = 0.99$$

$$W_m = W_T \times (km)_{PT} \times (km)_{PT} \times (RCF)_{CF} \times (RCF)_{PT} \times C_f$$

$$= 400 \times \frac{20}{100} \times \frac{100}{100} \times 0.99099 \times 1.005 \times 0.9506$$

$$W_m = 356.879 \text{ Kw}$$

there are errors

if error not present

$$W_T = 400 \times 20 \times 100 = 800 \text{ Kw}$$

$$\therefore \epsilon_r = \frac{356.879 - 800}{800} = -5.41\%$$

Q A PT Nominal ratio of  $\frac{2000}{100}$  volts, ratio correction factor of 0.995

Phase angle error of  $-22'$  (27 minutes) =  $\left(-\frac{22'}{60}\right)^\circ$  is used with a CT

of nominal ratio 100 and ratio correction factor of 1.005 and a phase

angle error of  $10^\circ$ . If we measure the power (2s leads I p) to a

single phase inductive load, a wattmeter connected lead correct

readings of 402 V, 4 A and 535 watts determine the power consumed by the load.

Soln  $\beta = 0^\circ$  (there)

$$RCF_{PT} = 0.995$$

$$\tan \theta_{PT} = \frac{2000}{100} = 20$$

$$S = -22 \text{ minutes} = \left(-\frac{22'}{60}\right)^\circ = -0.366^\circ$$

$$\theta = 10^\circ$$

$$\tan \theta_{CT} = \frac{100}{5} = 20$$

$$\phi = \alpha + \beta + S + \theta \quad \dots \text{Solve } \} \text{loggin pf}$$

$$W = V_{RC} \times I_{CC} \times \cos \alpha \quad ] \text{ take care}$$

$$335 = 102 \times 4 \times \cos \alpha$$

$$\frac{335}{408} = \cos \alpha$$

$$\alpha = 33.20^\circ$$


$$\phi = \alpha + \beta + S + \theta$$

$$\phi = 23.20 + 0 + 0.366 + 10^\circ$$

$$\phi = 33.566^\circ$$

$$CF = \frac{\cos \phi}{\cos \beta \cdot \cos \alpha}$$
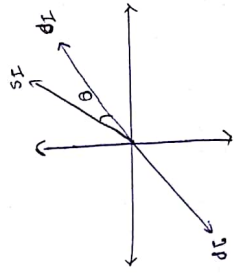
$$K = CF = \frac{\cos 33.566^\circ}{\cos 0^\circ \cdot \cos 23.20^\circ} = 0.9065$$



$$W_m = 395 \times 20 \times 20 \times 0.955 \times 1.005 \times 0.9065 = 125.99 \text{ kW}$$

### Digital Multimeter & [DMM] Digital Voltmeter [DVM]

Advantages:

- No parallel or series
- Single meter used for multiple applications
- High accuracy
- High resolution
- Higher sensitivity
- Easily compatible with computers
- Easily adjustable scale
- Less affected by dielectric and electrostatic effect
- Less maintenance.
- Low power consumption
- Higher speed
- compact in size

Disadvantages:

- Affected by surrounding temp due to electronic equipment (m) temp dependency.
- External battery source is required.
- If the battery is discharged then errors are produced.


CKT of DVM:

→ The basic measurable quantity of DVM is DC voltage, i.e any quantity to be measured like devolage, AC voltage, DC AC currents and unknown resistances are initially converted in terms of DC voltage which is of analog sig.


→ During measurement the ip is assumed constant for this purpose a sample & hold sig CKT is used for sampling of ip data and holding this data until it is measured.

→ This analog sampled data is converted into digital using ADC and this digital data is processed through the BCD converter and displayed on a 7 segment display unit.

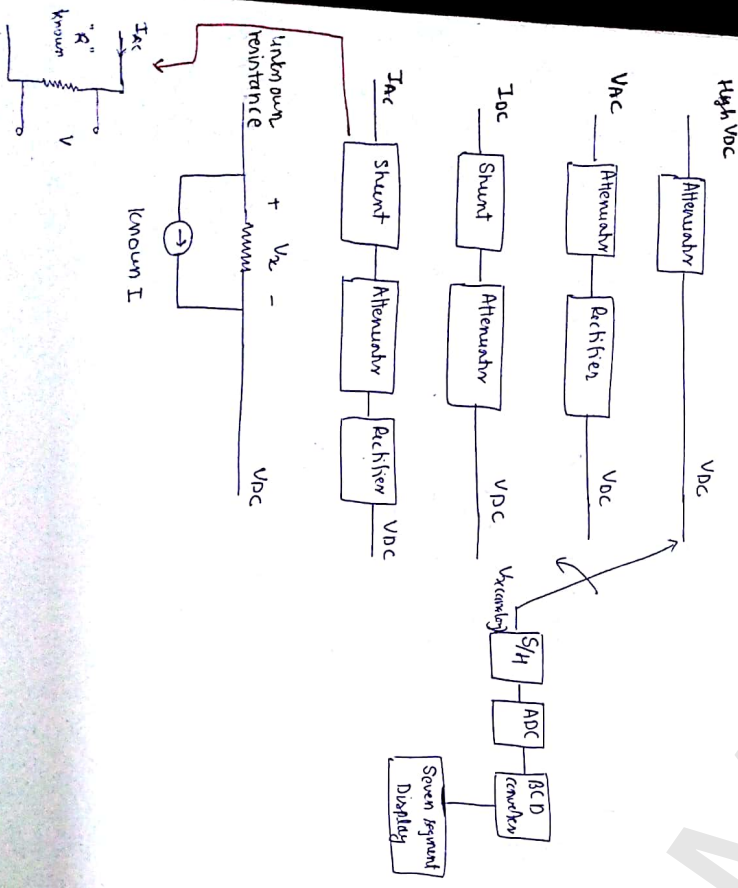
→ Dual slope ADC is practically used method in DVM bcz accuracy is higher and less affected by external noise.



→ S/H CKT

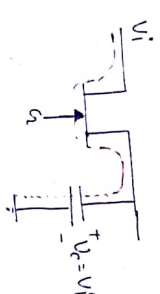

→ Attenuator

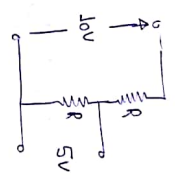

→ ADC

Types

- 1) Flash
- 2) SAR
- 3) Counter

Data conversion time

- 1 clock cycle.
- n x Tclk
- (2<sup>n</sup> - 1) Tclk

(4) Dual slope (DVM uses) → 2<sup>n+1</sup> Tclk

Tclk = Time period of clock sig  
n = no. of digital bits of ADC

Significance of DVM

① Resolution : Smallest change in input able to be detected by the instrument is called resolution.

→ In DVM by fixing the no. of digits resolution is fixed.

$$R = \frac{1}{10^n}$$


$n$  = no. of full digit  
↳ which can display all no. from 0 to 9.

Seven segment display :-



$$n = 3$$

$$R = \frac{1}{10^3} = 0.001$$

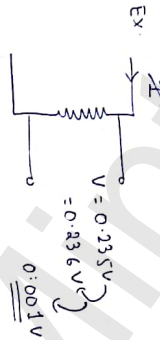

② Sensitivity  
Smallest value of the i/p that can be displayed by the meter in the given range is called sensitivity.


$$\text{Sensitivity} = S = \frac{\text{min}^m \text{ full scale value}}{(f.s)_{\text{min}} \times R}$$

$$S = \text{Range} \times \text{Resolution}$$


Ex:

Range	$R = \frac{1}{10^n}$	$S$	$\text{max}^m$	$\text{min}^m$	$\text{max}^m$ Display
0-1V	0.001	0.001 x 1 = 0.001	9.99	0.000	9.99
0-10V	0.001	0.001 x 10 = 0.01	99.9	00.0	99.9
0-100V	0.001	0.001 x 100 = 0.1	999.9	000.0	999.9

Ex: .236

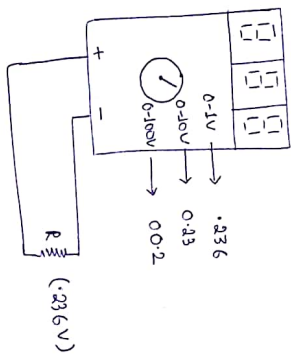

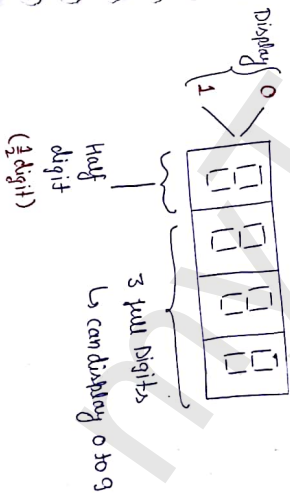③ Over Ranging :-  
→ If extra 1/2 digit is switch on is called over ranging.



3 1/2 Digit Display :  $R = \frac{1}{10^3} = 0.001$   
 $n \frac{1}{2}$  Digit Display  $\Rightarrow R = \frac{1}{10^n}$   
 1/2 sensitivity will change.

Ex

Range	$R = \frac{1}{10^n}$	S	mm	Max. Display
0-1 V	0.001	0.001 × 1 = 0.001	0.000	1.999
0-10 V	0.01	0.001 × 10 = 0.01	00.00	19.99
0-100 V	0.001	0.001 × 100 = 0.1	000.0	199.9

Here in averaging, range is doubled

0000  
1999

④ % Total Error (% CV)

$$\% CV = \pm \left[ \frac{\text{Error of reading value} \times \text{Reading value}}{\text{No. of counts}} + \frac{\text{No. of counts}}{\text{(max. scale range)}} \times \text{full scale reading} \right]$$

$$+ \frac{\text{No. of counts}}{\text{(max. scale range)}} \times \text{full scale reading}$$


(max<sup>m</sup> over ranging)

$$\text{Error} = (\% \text{ error in reading}) \times \text{reading} + (\text{No. of counts}) \times \frac{\text{Full scale range of meter}}{\text{Range of meter}}$$

23<sup>rd</sup> September

Q-meter (Quality factor meter or voltage magnifier) :-

{ Principle is Series Resonance }

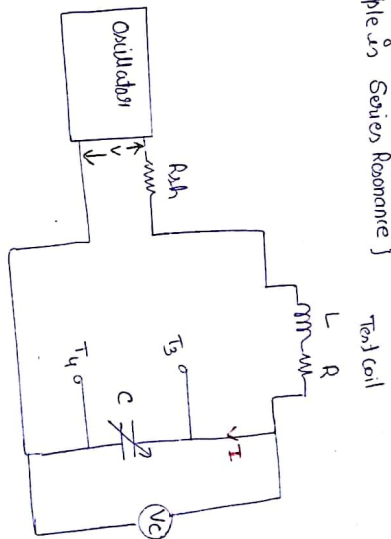

$$Q_T = \frac{\omega L}{R} = \frac{X_L}{R} = \text{True value}$$

$$V_C = I \cdot X_C$$

Series resonance  $X_C = X_L$

$$I = \frac{V}{(R + R_{sh})}$$

$$V_C = \frac{V X_C}{(R + R_{sh})} = \frac{V \cdot X_L}{(R + R_{sh})}$$

$$V_C = \frac{V \cdot X_L}{R \left[ 1 + \frac{R_{sh}}{R} \right]}$$

$$= \frac{V \cdot Q_T}{\left( 1 + \frac{R_{sh}}{R} \right)}$$

$$V_C = V \cdot Q_m$$

$$V_C \propto Q_m$$

$$Q_m = \frac{Q_T}{\left( 1 + \frac{R_{sh}}{R} \right)}$$


$$\% CV = \frac{Q_m - Q_T}{Q_T} \times 100$$

$$\% CV = - \left( \frac{R_{sh}}{R_{sh} + R} \right)$$

∴ in case of  $R_{sh}$  is low value


so  $R_{sh} = m\Omega$

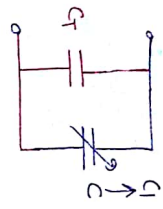Application ① If we want to measure Test capacitance.



$$f_1 = \frac{1}{2\pi\sqrt{L(C_1+C_2)}}$$

we arrange we will make  $f_1 = f_2$

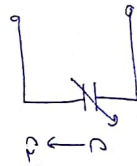

$$f_2 = \frac{1}{2\pi\sqrt{LC_2}}$$

$$f_1 = f_2$$

$$C_T = C_2 - C_1$$

How to measure self-capacitance of the coil.



$$f_1 = \frac{1}{2\pi\sqrt{L(C_1+C_d)}}$$

$$C \rightarrow C_2 \quad f = f_2$$

then  $f_1$  such that  $f_2 = n f_1$

$$f_2 = \frac{1}{2\pi\sqrt{L(C_1+C_d)}} = n f_1 = \frac{1}{2\pi\sqrt{L(C_1+C_d)}}$$

$$C_d = \frac{C_1 - n^2 C_2}{(n^2 - 1)}$$

eg / distributed capacitance of coil = Cd

Q Given cap is set to 400uf with oscillator fm of 2kHz now by varying the oscillator fm to 4kHz. the new value of capacitance is 20uf. Find the self or distributed capacitance of the test coil


$$C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$$

$$f_1 = 2 \text{ kHz} \quad f_2 = 4 \text{ kHz}$$

$$f_2 = n f_1 \Rightarrow n = 2$$

$$C_d = \frac{400 - (2)^2 \times 20}{2^2 - 1} = \frac{400 - 80}{4 - 1} = \frac{320 \mu\text{F}}{3}$$

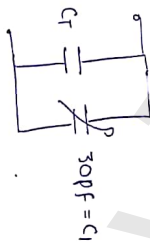
Q An unknown cap is measured using a Q meter by connecting a test capacitance across cap of Q meter. the Q is suspended with a cap of 30 pf and the reading of 50 observed across the unknown capacitor connected. By removing the capacitance the Q is resonated at a freq of 80 pf. find the unknown capacitance.



$$C_T = C_2 - C_1 = 80 - 30 = 50 \text{ pf}$$

Note: S meter is also used for the measurement of L from known S and R and measure R from known S and L  
 \* In the measurement of loss impedance S meter is connected in series and for the measurement of high impedance S meter is connected in parallel to the coil

Q.12) Find the circuit for

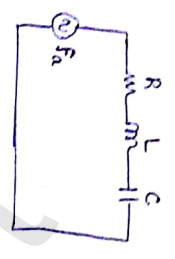


$$f = \frac{1}{2\pi\sqrt{LC}}$$


$f_a$  applied freq,  $f_n$  natural freq

If  $f_a = f_n$  then  $X_L = X_C$  and system will behave as a Resonance circuit.


Q.13) 2

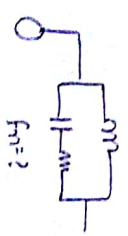


$f_n = ?$

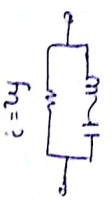

$f_n = ?$

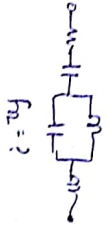

$f_n = ?$

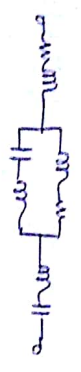

$f_n = ?$

Cathode Ray Oscilloscope [CRO]:

110 cycles visible on the screen

$$\eta = \frac{\text{Time period of Screen}}{\text{Time period of signal}} = \frac{T_{\text{Screen}}}{T_{\text{Signal}}}$$

Q1 A CRO has 10cm x 8cm in the x ray scale. The time per division is 20ms. In set a sig of  $V = V_m \sin 2\pi 100t$  is applied. Calc no. of cycle visible on the screen.

So 20ms x 10 = 200ms =  $T_{\text{Screen}}$

$$2\pi 100 = \omega \quad f = T = \frac{1}{200} = 5 \text{ Hz}$$

$$\frac{T_{\text{Screen}}}{T_{\text{Signal}}} = \frac{200 \text{ ms}}{10 \text{ ms}} = 20 \text{ cycles are visible.}$$

Q2 In the above CRO 2 volts/div is set to the y scale. If a sig of

①  $2 \sin 2\pi 50t$

② a ac rms voltage of 10V magnitude & freq of 200Hz is applied. Find no. of cycles and visibility of waveform on the screen. i.e. draw or undistorted

sol<sup>n</sup> peaks peak to peak = 16 volts k2 & div in y scale.

①  $f = 50 \text{ Hz} \quad T = \frac{1}{50} = 20 \text{ ms}$

$n = \frac{T_{\text{Screen}}}{T_{\text{Signal}}} = \frac{200 \text{ ms}}{20} = 10 \text{ cycle.}$

1st 0 of sig = 8 volt so undistorted

②  $f = 200 \text{ Hz} \Rightarrow T = \frac{1}{200} = 5 \text{ ms}$

$n = \frac{200 \text{ ms}}{5 \text{ ms}} = 40 \text{ cycle.}$

$V_{\text{rms}} = 10 \text{ V}$

$V_{\text{pk}} = 10 \times \sqrt{2} = 14.14 \text{ V}$   
 so clipped sig.

Preaccelerating and Accelerating Anode potential are used to ↑ the speed of the e<sup>-</sup>.

$$K.E = p.E$$

$$\frac{1}{2} m v^2 = q.V_a$$

$$v = \sqrt{\frac{2q.V_a}{m}}$$

$$V_a = \text{anode potential}$$

$$v = \sqrt{\frac{2 \times 1.6 \times 10^{-19}}{9.1 \times 10^{-31}}} \sqrt{V_a}$$

$$= 0.59 \times 10^6 \sqrt{V_a}$$

$$V \approx 0.6 \times 10^6 \sqrt{V_a}$$

if  $V_a$  doubles,  $v$  becomes twice.

Q The anode potential applied to the CRT is 2500V find the velocity of the electron beam


$$v \approx 0.6 \times 10^6 \sqrt{25}$$

$$v \approx 3 \times 10^6 \text{ m/sec}$$

Stability :-

Note: By changing the control grid potential, intensity or brightness of the beam is changed.

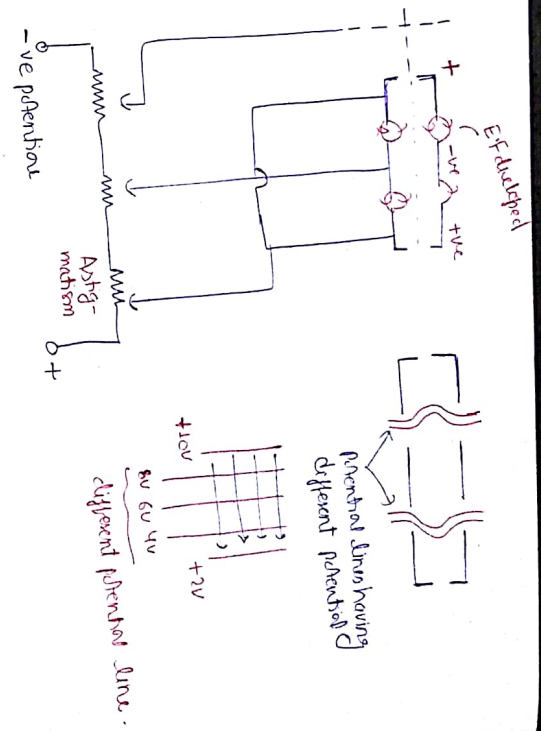
if 1 only -ve potential at control grid no. of e<sup>-</sup> will be stopped





Focus control :

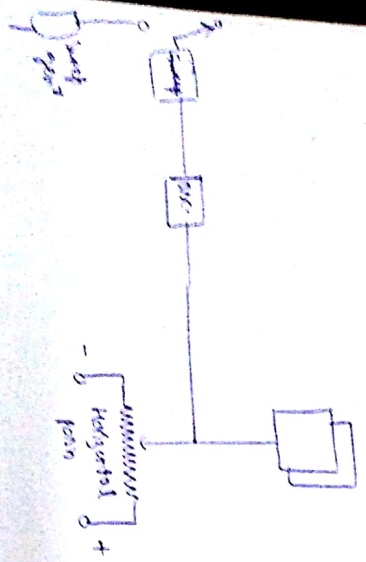Electrostatic Focus control is used in laboratory CRT's which is working on the principle of Double convex electron lens. For Fine Focus control Astigmatism is used by applying a potential to pre and accelerating anode.








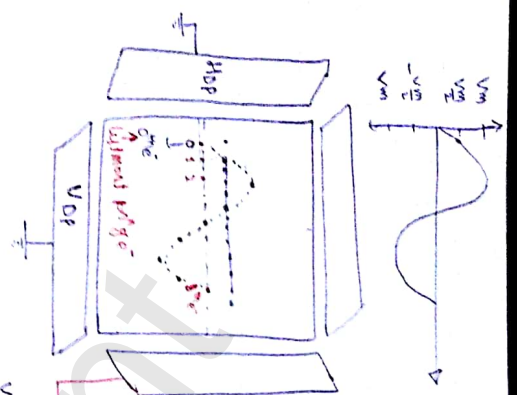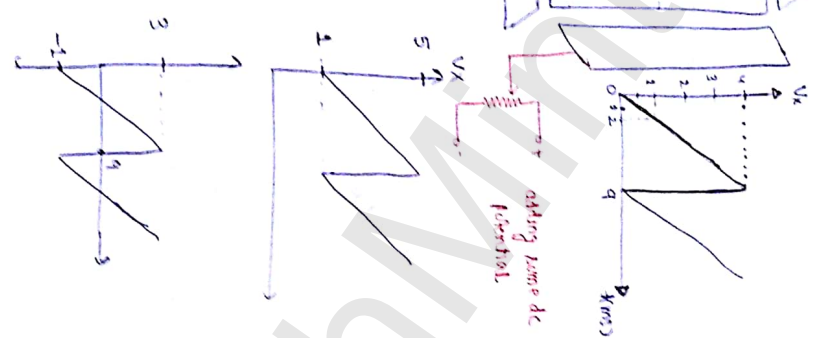If i want to pull the horizontal wave toward right or left dc potential is required.  
 apply + dc  $\rightarrow$  right side  
 " - dc  $\rightarrow$  left side




- \* Horizontal deflection plate stop applied with a constant current to move the beam along horizontal axis.
- \* Vertical deflecting plate is applied with a def signal to move the beam up and down in vertical path.
- \* This dc potential +ve or -ve is applied to both Hg or Vg for horizontal and vertical path of the beam.
- Some time we used to zero the wave form. wave reads adjust on level. call possible.

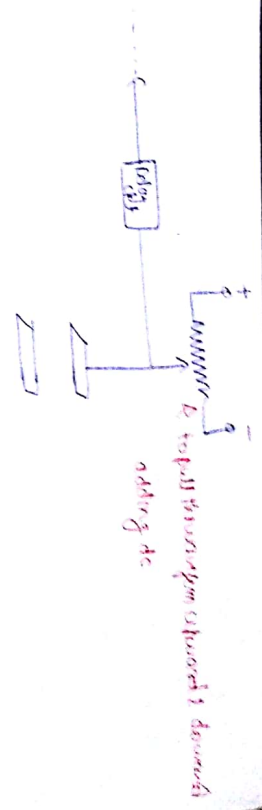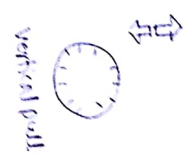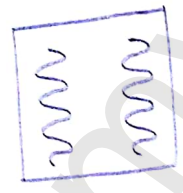


Q Vpp is applied with 10 volt DC produces a displacement of 1cm on a screen if a 10 sig having same value of 10v is applied what is the max distance occupied on the screen.

10V = 1 cm  
 1V = 0.1 cm

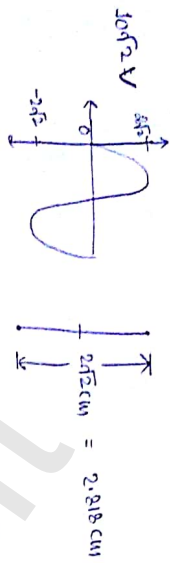

\*\*\*  
 Concept :-

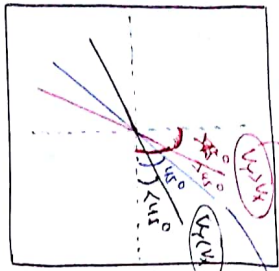


$V_y = V_m \sin w t = V_x$   
 $V_x = 2 V_m \sin w t$

LP  
 $\phi = 0$  or  $360^\circ$


$0^\circ < \phi < 90^\circ$   
 or  
 $270^\circ < \phi < 360^\circ$

$\phi = 90^\circ$  or  
 $270^\circ$

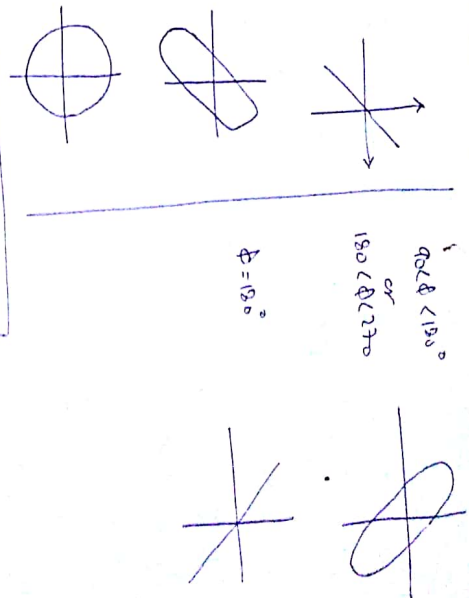

$V_x = V_m \sin w t$   
 $V_y = V_m \sin(w t + \phi)$   
 $\phi = \text{phase angle b/w } V_x \text{ \& } V_y$

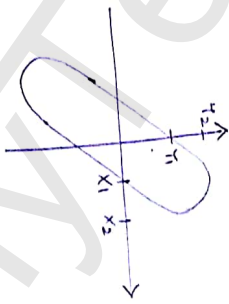
QLP in I<sup>st</sup> & III<sup>rd</sup> Quadrant



$\phi = \sin^{-1} \left( \frac{y_1}{x_1} \right)$  or  
 $= \sin^{-1} \left( \frac{y_2}{x_2} \right)$


Second probability =  $(360 - \phi)$

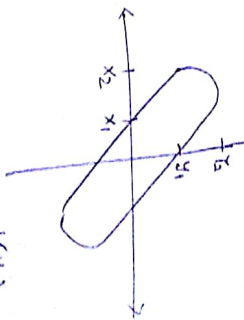QLP in II<sup>nd</sup> & IV<sup>th</sup> Quad




$\phi = 180^\circ - \sin^{-1} \left( \frac{y_1}{x_1} \right)$   
 $= 180^\circ - \sin^{-1} \left( \frac{y_2}{x_2} \right)$

Second prob =  $(360 - \phi)$


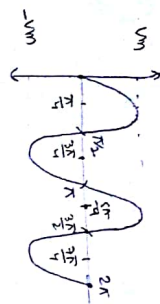


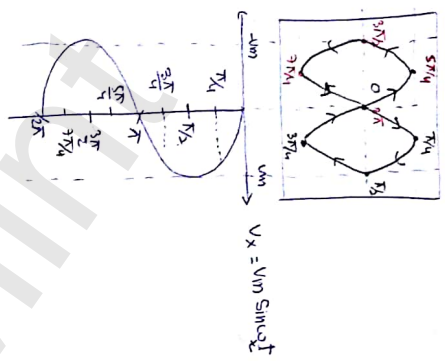$V_y = V_m \sin \omega t$   
 $V_x = V_m \sin \omega t$



$\frac{f_y}{f_x} = \frac{\text{No. of horizontal touch}}{\text{No. of vertical touch}} = \frac{2}{2} = 1$


$f_x = 2f_c$

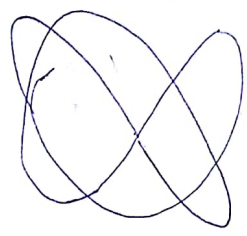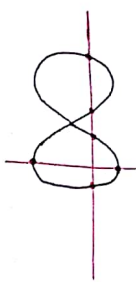


$x = \sin 3t$

$y = \sin 2t$

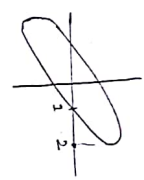Q. From the following Lissajous pattern find phase angle difference between horizontal and vertical deflection as voltage.



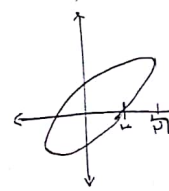
$\phi = \sin^{-1}(\frac{1}{2})$   
 $\phi = 30^\circ$   
 or  $(360 - \phi) = 330^\circ$



$\phi = \sin^{-1}(\frac{1/2}{1})$   
 $\phi = \sin^{-1}(\frac{1}{2})$   
 $\phi = 30^\circ$   
 $(360 - 135^\circ) = 225^\circ$




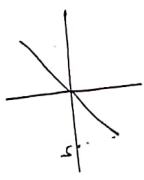$\phi = \sin^{-1}(\frac{1}{1}) = 90^\circ$   
 or  $270^\circ$



$\phi = \sin^{-1}(\frac{0}{1}) = 0^\circ$   
 or  $360^\circ$

Conc. Q. 1

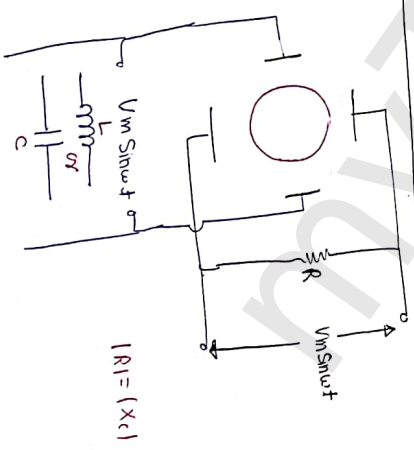

Q CRO Vpp Applied with  $V = V_m \sin 2\pi \times 1000 t$  with threshold & resistance of  $1k\Omega$ . How much of capacitance required if  $V = V_m \sin 2\pi \times 1000 t$  is applied to the CRO so that circle is formed on the screen.

Sol<sup>n</sup> =

$$|R| = |X_c|$$

$$1000 = \frac{1}{2\pi \times 1000 C}$$


$$C = \frac{1}{2\pi} \mu F$$

$$|R| = |X_L|$$

$$1000 = 2\pi \times 1000 L$$

$$L = \frac{1}{2\pi} \text{ Henry}$$

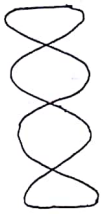Q Voltage  $V_x = V_m \sin 1000t$  is applied to the CRO on with  $V_y = V_m \sin 4000t$  to the Vpp produces Liss pattern shown in the figure find the fms of  $V_{pp}$ .



$$\frac{f_y}{f_x} = \frac{8}{2}$$

$$f_y = 4f_x$$




$$f_y = 4 \times f_x$$

$$\omega_y = 4\omega_x$$



$$\omega_y = 4000$$

$$f_y = \frac{4000}{2\pi} = \frac{2000}{\pi} \text{ Hz}$$


Problems with Sawtooth wave

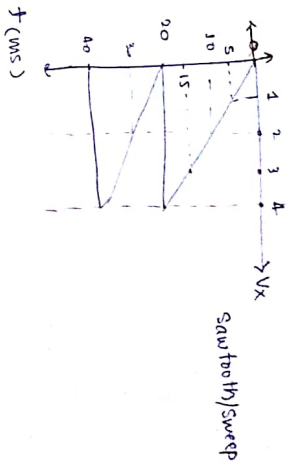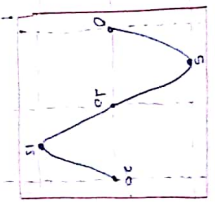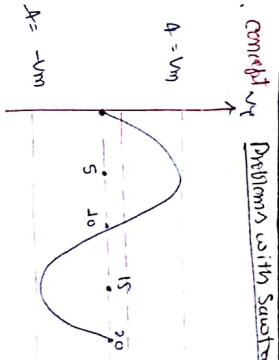

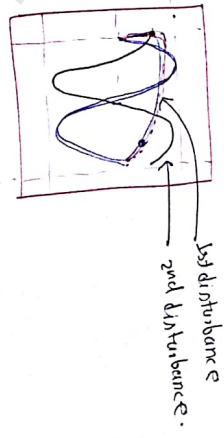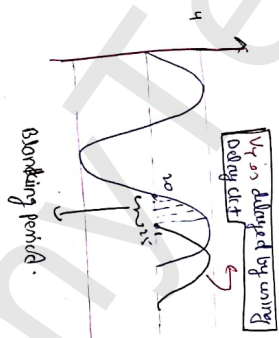Switches don't have a falling time practically. UT contain RC time so some time delay is there.



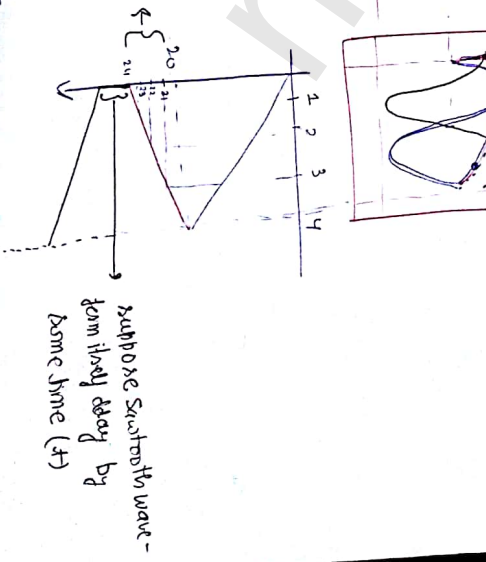Extrace time of Sawtooth  
Time delay  
Falling time



\* Blanking CRT is used to stop the e-<sup>-</sup>s entering into the CRT during starting or advance time, of the sawtooth signal applied to the HOP.

Time delay line circuit is connected to the VOP for delaying the test sig for synchronising the sawtooth and test sig.

Total time Delay  $V_{op} =$  Falling time of Sweep gun + Initial starting time delay of the sweep sig.

Blanking dlt connected to control grid, makes control grid more -ve so we e-<sup>-</sup> flow for falling time.


\* Concept  
VST is inbuilt inside CRT  
V<sub>r</sub> we need to apply from outside for gun

Trigger input is used in the CRT to bring the initial starting point of the test sig which is suppressed to be synchronize with the horizontal deflecting plate initial sawtooth signal depending on the initial magnitude.

from the to -ve of the test sig corresponding compensation is added using the trigger and bring the waveform to the initial position so that smooth dip is available superimposed displaying similar waveform of test sig.

Edge triggering is the most basic type used in all the digital and analog oscilloscope both the +ve and -ve slope are added depending on slope of the incoming sig.

Deflection of CRT :-

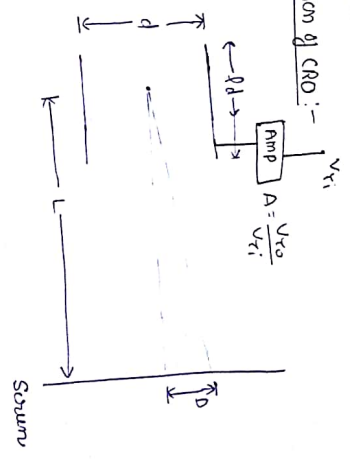

$$D = \frac{LdV_r}{2dV_a}$$

V<sub>a</sub> = anode voltage

Deflection Sensitivity  $S = \frac{D}{V_r} = \frac{Ld}{2dV_a} \dots \frac{\text{mm}}{V}$

Deflection factor  $G = \frac{1}{S} \dots \dots \dots \frac{V}{\text{mm}}$

Q. An electron beam having a velocity of  $6 \times 10^6$  m/sec is passing through the vertical deflecting plate separated by 10mm and a length of 20mm and L = 25mm produces a D = 10mm. Find the voltage applied to the VOP if the gain of the amp is 100.


Soln.  
 $D = \frac{LdV_r}{2dV_a}$   
 $\frac{1}{2} m v^2 = q V_a$   
 $\frac{1}{2} \times 91 \times 10^3 \times 6 \times 10^6 = 1.6 \times 10^{-19} \times V_a$   
 $V_a \approx 102.325$

$10 \text{ mm} = \frac{25 \text{ mm} \times 20 \text{ mm} \times V_r}{2 \times 10 \text{ mm} \times 102.325}$


$V_r = 40.95$

$V_i = \frac{40.95}{100} = .40 \text{ volt}$

Continuous Ramp type DVM

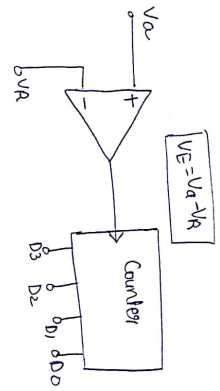

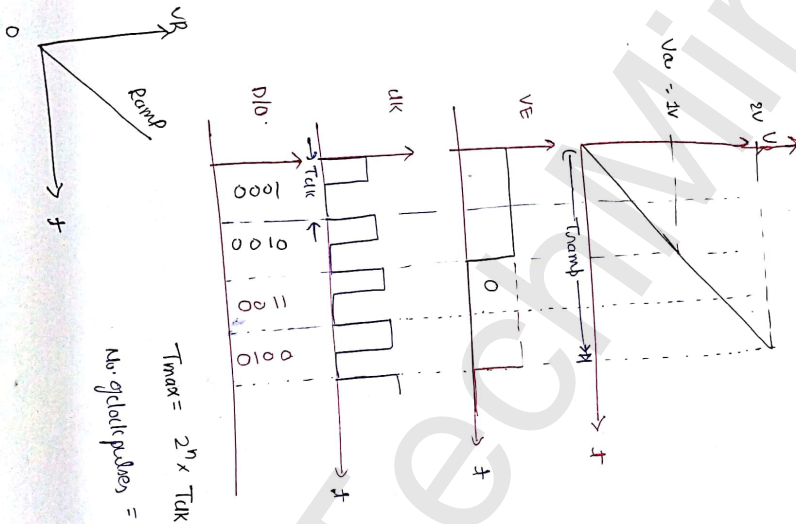Data conversion time is a high order in a problem.



$$T_{max} = 2^n \times T_{clk}$$


$$\text{No. of clock pulses} = P = \frac{T_{ramp}}{T_{clk}} = \frac{f_{clk}}{f_{ramp}}$$

Q A continuous ramp DVM has a ramp slope with a  $-10$  slope drops voltage from  $6V$  to  $0V$ , in  $10$  msec. calculate the no of pulses required for this ramp type.

Talk =  $1 \mu\text{sec}$   
 $T_{\text{ramp}} = 10 \text{ msec}$

$$P = \frac{10 \text{ msec}}{1 \mu\text{sec}} = \frac{10 \times 10^{-3}}{1 \times 10^{-6}} = 10000 \text{ pulses required}$$

Stair case Ramp

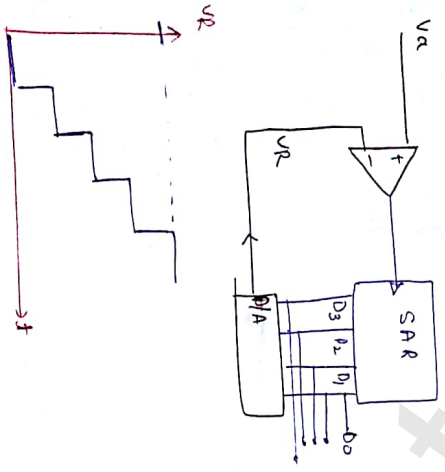

Successive Approximation

Advantages


- Capable of high speed and flexible
- Medium accuracy ~~accuracy~~ compared to other ADC types
- Good trade-off between speed and cost
- Capable of outputting the binary no. in serial (one bit at a time) format.

Disadvantages

- Higher resolution Successive approximation ADC's will be slower.
- Speed limited to  $\sim 1 \text{ Msps}$

$$T_{\text{max}} = n \times T_{\text{clk}}$$
  
 max<sup>m</sup> conversion time  
 $n = \text{no. of digital output bits}$

Dual slope Approximation:

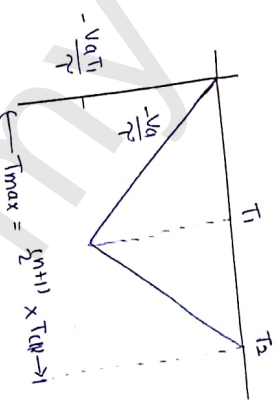

Data conversion occur at  $t = T_2$

$$V_{\text{ATI}} = V_R \left( \frac{T_2 - T_1}{T} \right)$$
  
 Discharging time.

Advantage


- o Slip sig is averaged
- o greater noise immunity than other ADC type
- o High accuracy

Disadvantage

- o slow
- o High precision external components required to achieve accuracy.

Speed	Data conversion time	Accuracy
Flash	1 clock	↓
SAR	n "	↓
Single slope/ramp	2 <sup>n</sup> "	↓
Dual slope	2 <sup>(n+1)</sup> "	most accurate

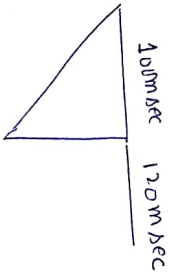Q. A Dual slope ADC DVM has charging time of 100msec and discharging in period of 120msec with reference voltage of 2V. Find the analog input voltage.



$$V_R = 2V$$

$$V_a \cdot T_1 = V_R (T_2 - T_1)$$

$$V_a \cdot 100 = 2 \cdot 120$$

$$V_a = \frac{240}{100} = 2.4 \text{ Volt}$$

Q. A Dual slope DVM consisting of an integrator of gain time = 100ms & full scale balance the voltage applied to the integrator in 1V. Now if a reference voltage is applied to integrator at  $T_1$  to SV in amplitude when time interval of  $T_2$ .

$$T^2 = RC = 100 \times 10^{-3} \times 10^{-6} = \frac{1}{10} = 0.1$$

$$V_a = 1V ; V_R = 5V$$


$$\frac{V_a}{V_R} T_1 = (T_2 - T_1)$$

$$\frac{1}{5} T_1 + T_1 = T_2$$

$$T_1 \left(1 + \frac{1}{5}\right) = T_2$$

$$\frac{6}{5} T_1 = T_2 \quad \text{--- (1)}$$


$$T_2 = 1.2 T_1 \quad \text{--- (2)}$$

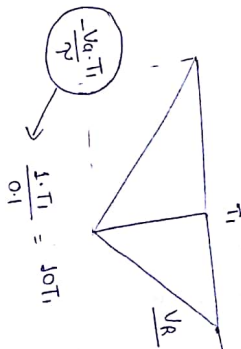

Specifications :- of DVM

$$\text{(1) } R = \frac{1}{10^6} = \text{Resolution}$$

m = no. of full digit

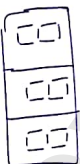

Ex n=3

$$R = \frac{1}{10^3} = 0.001$$


(1) Read sensitivity.



Prblm:- A  $3\frac{1}{2}$  voltmeter used for voltage measurement

- ① Find its resolution
- ② How would 1152 counts will be displayed on the 10 V range.
- ③ " " 0.2345 volts " " " 1V-50 and 10V range.

Soln:- ①  $R = \frac{1}{10^3} = 0.001$

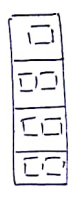

② 0-10V

$S = 0.001 \times 10 = 0.001$

display = 11.52

③ (i) ~~S = 0.001~~

0-1V Range  
 $S = 0.001 \times 1 = 0.001$

display = 0.234

(ii) 0-10V

$S = 0.001 \times 10 = 0.001$

display = 00.23


Transducer

- ① Potentiometer T/D
- ② LVDT T/D
- ③ Hall Effect T/D


Q1 A potentiometer has a stroke of 20 cm applied with voltage of 1V.

- Find ① sensitivity  
 ② Displacement in the 0p voltage in 0.25V  
 ③ if the 0p voltmeter has 20 divisions. Also 0 to 1 volt range and scale can be used upto  $\frac{1}{5}$ th of division find the resolution of the potentiometer

Soln

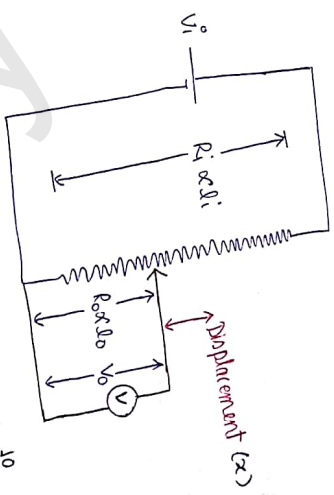

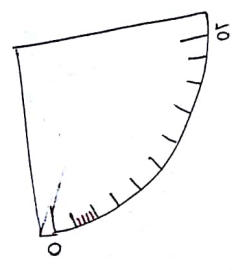$S = \frac{\Delta Vo}{\Delta x}$   
 = max Displacement measured by POT



$V_o = V_i \frac{R_o}{R_i}$   
 $= V_i \frac{10}{2} = \frac{V_i x}{2}$   
 $S = \frac{V_o}{x} = \frac{V_i}{2}$   
 $S = \text{sensitivity}$   
 $\frac{V}{mm}$

$$① S = \frac{V_i}{U} = \frac{1}{20} = 0.05 \text{ V/cm} \quad \text{Sensitivity} = \frac{dV}{dx}$$

$$② \frac{V_o}{V_e} = S \Rightarrow x = \frac{V_o}{S} = \frac{0.25}{0.05} = 5 \text{ cm}$$

$$③ 20 \text{ divisions} = 1 \text{ V}$$

$$1 \text{ division} = \frac{1}{20} \text{ V} = 0.05 \text{ V}$$



$$\text{Read upto } \frac{1}{5} \text{ division} = \frac{0.05}{5} = 0.01 \text{ V}$$

$$\text{Resolution} = \frac{\text{min}^m \text{ Read value}}{S} = \frac{0.01}{0.05 \text{ V/cm}} = 0.2 \text{ cm}$$

$$R = 0.2 \text{ cm}$$

5 An LVDT has opp of 5 volts across its terminals when the core moves through a distance of 2mm the tip of LVDT is connected through a low voltmeter through an amp of gain 200. if the multi voltmeter scale has 100 divisions and scale can be read up to  $\frac{1}{5}$ th of the divisions find the overall inductance in mm.
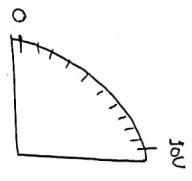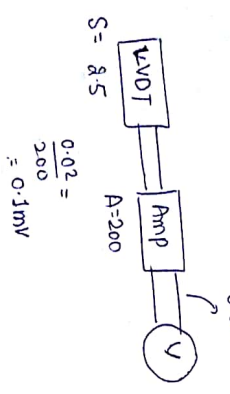
$$\text{Sensitivity} = \frac{5 \text{ mV}}{2 \text{ mm}} = 2.5 \text{ mV/mm}$$



$$S = 2.5$$

$$\frac{0.02}{200} = 0.1 \text{ mV}$$

$$R \approx \frac{0.1 \text{ mV}}{2.5 \frac{\text{mV}}{\text{mm}}} = 0.04 \text{ mm}$$


$$= 40 \mu\text{m}$$

$$\text{100 div} = 10 \text{ V}$$

$$1 \text{ div} = 0.1 \text{ V}$$

$$\text{Readability} = \frac{0.1}{5} = 0.02 \text{ V}$$

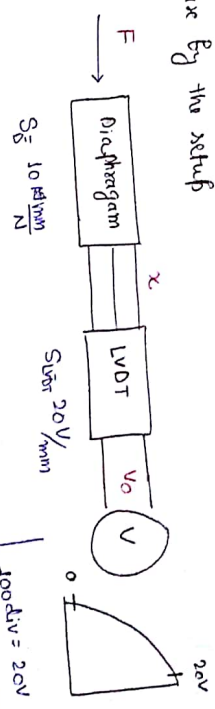9 A diaphragm and LVDT combination are used to measure force. In terms of voltage diaphragm has sensitivity of  $10 \frac{\text{mV}}{\text{N}}$  LVDT has sensitivity of  $20 \frac{\text{mV}}{\text{mm}}$  the opp of LVDT voltmeter has 100 divisions measures upto  $\frac{1}{10}$ th of divisions find the min force able to measure by the setup



$$\text{Overall sensitivity} = S_D = \frac{V_o}{F} = \frac{V_o}{F} \times \frac{X}{X}$$

$$= S_D \times S_{LVDT} = 10 \times 20 = 200 \text{ V/N}$$

$$\text{min Force} = \text{Resolution} \Rightarrow \frac{0.02 \text{ V}}{200 \text{ V/N}} = 0.1 \text{ mN}$$

$$100 \text{ div} = 20 \text{ V}$$


$$1 \text{ div} = 0.2 \text{ V}$$

$$\frac{1}{10} \text{ div} \Rightarrow \text{Readability} = 0.02$$

Stress / Strain / Pressure / Force :-

- ① Piezo Resistive / Strain Gauge / Load cell
- ② Piezo Electric

Strain Gauge :-

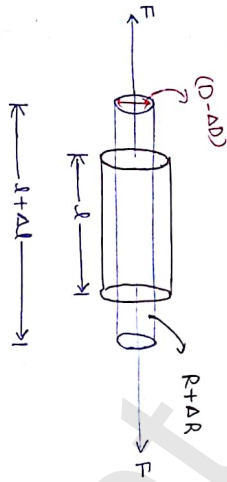


$$G_f = \frac{\frac{\Delta R}{R}}{\frac{\Delta l}{l}} = 1 + 2\gamma + \frac{\partial \rho / \rho}{\partial l / l}$$

*confirm*

$\gamma = \frac{\Delta \rho / \rho}{\Delta l / l} = \text{Young Modulus}$

$-\frac{\Delta D}{D} = \epsilon_D = \text{Lateral strain}$

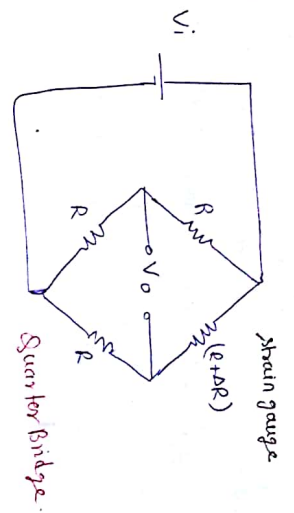$\nu = \frac{\epsilon_D}{\epsilon_l} = \text{Poisson's Ratio}$



$$V_0 = V_i \left[ \frac{R}{2R} - \frac{R}{2R + \Delta R} \right]$$

$$= V_i \left[ \frac{(2R + \Delta R)R - 2R^2}{2R(2R + \Delta R)} \right]$$

$$= \frac{V_i}{2} \left( \frac{\Delta R}{2R + \Delta R} \right)$$

$$= \frac{V_i}{2} \left( \frac{\Delta R / R}{2 + \Delta R / R} \right)$$

$$V_0 = \frac{V_i}{2} \cdot \frac{G_f \cdot \epsilon_l}{(2 + G_f \cdot \epsilon_l)}$$


②  
 Semicond strain gauge has a nominal resistance of 100Ω and Gauge factor of +200 at 25°C calculate the resistance of strain gauge in ohms when subjected to a strain of 10<sup>-4</sup> at the same temp

1020 Ohm

Q a Wheatstone bridge has resistors  $R_1$  in  $R_{AD}$ ,  $R_2$  in  $R_{BC}$ , dummy gauge

$R_{AD}$  and active gauge in arm  $BC$  if a strain of  $1250 \mu\text{m/m}$  is applied find the bridge output voltage across  $BD$ .  
 AC the bridge is supplied with voltage of  $12\text{V}$  across  $BD$   
 assume  $R_1 = R_2 = 350 \Omega$  dummy gauge =  $350 \Omega$  and resistance of active strain gauge =  $350 \Omega$  with gauge factor of 2

Sol<sup>n</sup>

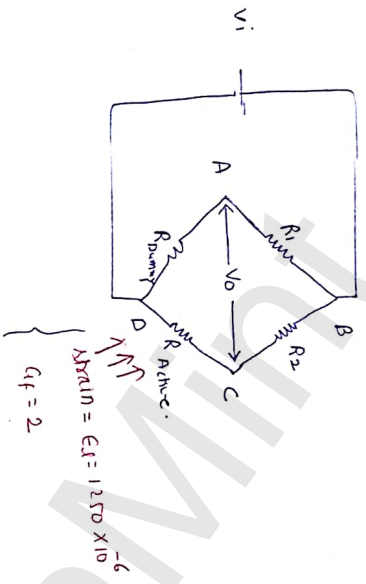

$$V_o = \frac{V_i}{2} \times \frac{G_f \cdot \epsilon \cdot R}{2 + G_f \cdot \epsilon \cdot R}$$


$$V_o = \frac{12}{2} \times \left( \frac{2 \times 1250 \times 10^{-6}}{2 + 1250 \times 10^{-6} \times 2} \right)$$

$$V_o = 7.149 \text{ mV}$$

Q Resistance at temp<sup>n</sup>  $T_0$  value of a thermistor is given by

$$R_T = R_0 e^{p \left( \frac{1}{T} - \frac{1}{T_0} \right)}$$

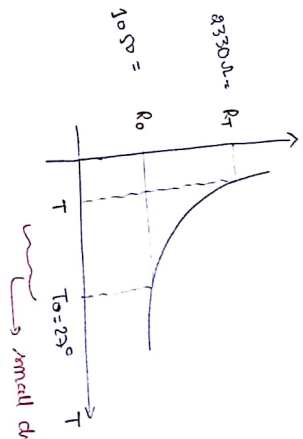where  $R_0 = 1050 \Omega$  at  $25^\circ \text{C}$   $p = 3140$  what is the temp<sup>n</sup> with the thermistor resistance is  $2330 \Omega$



small change in temp<sup>n</sup> leads to large change in resistance  
 Advantages of thermistors  
 1) Temp<sup>n</sup> of resistance.

$$T = 5.33^\circ \text{C}$$