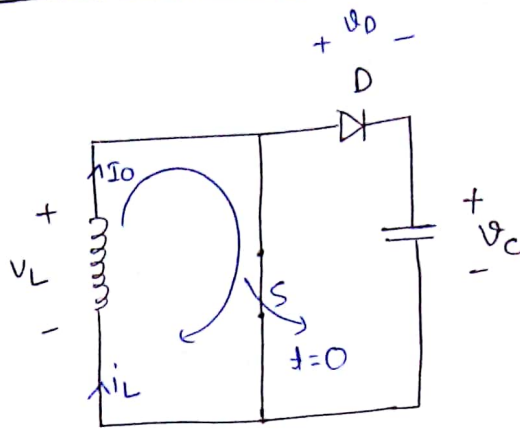


# Power Electronics

NO




Switch opened at  $t=0$ , Find the volt across cap<sup>c</sup> when diode stops conducting  
 and  $V_C[t=0] = 0$   
 $i_L[t=0] = I_0$

Sol<sup>n</sup>

$$-V_L + V_D + V_C = 0$$

$$V_L = V_C$$
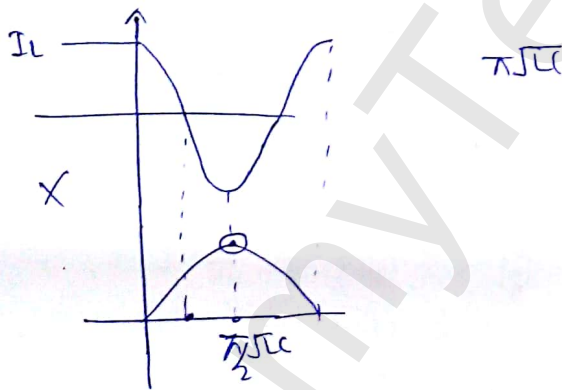
$$L \frac{di_L}{dt} = \frac{1}{C} \int i_L dt$$



By Sir:

Energy relation

At  $t=0$   $\left( \frac{1}{2} L I_0^2 \right)$  Initial energy converted into  $\frac{1}{2} C V_m^2$

At that which cap<sup>c</sup> finally change.

$$\frac{1}{2} L I_0^2 = \frac{1}{2} C V_m^2$$

$$V_m = I_0 \sqrt{\frac{L}{C}}$$


$i_L$  ↓ing so  $i_L = I_0 \cos \omega t$


$V_C$  ↑ing so  $V_C = V_m \sin \omega t$

$$V_C = I_0 \sqrt{\frac{L}{C}} \sin \omega t$$


Diode will conduct for

$$\frac{\pi}{2} \text{ radian}$$

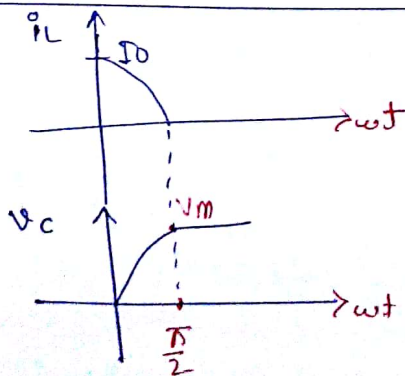

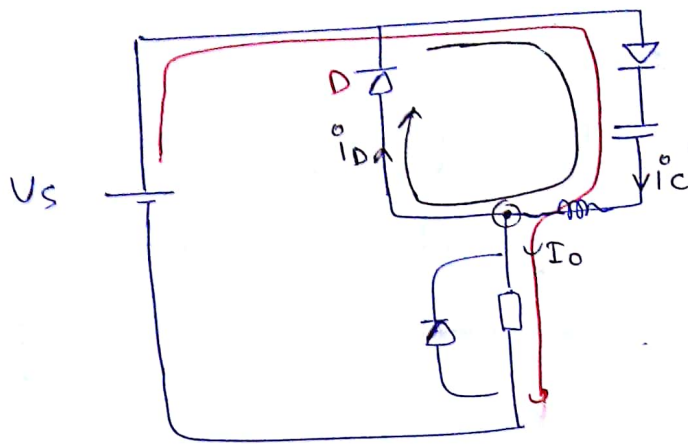

$$i_c = I_o + i_D$$

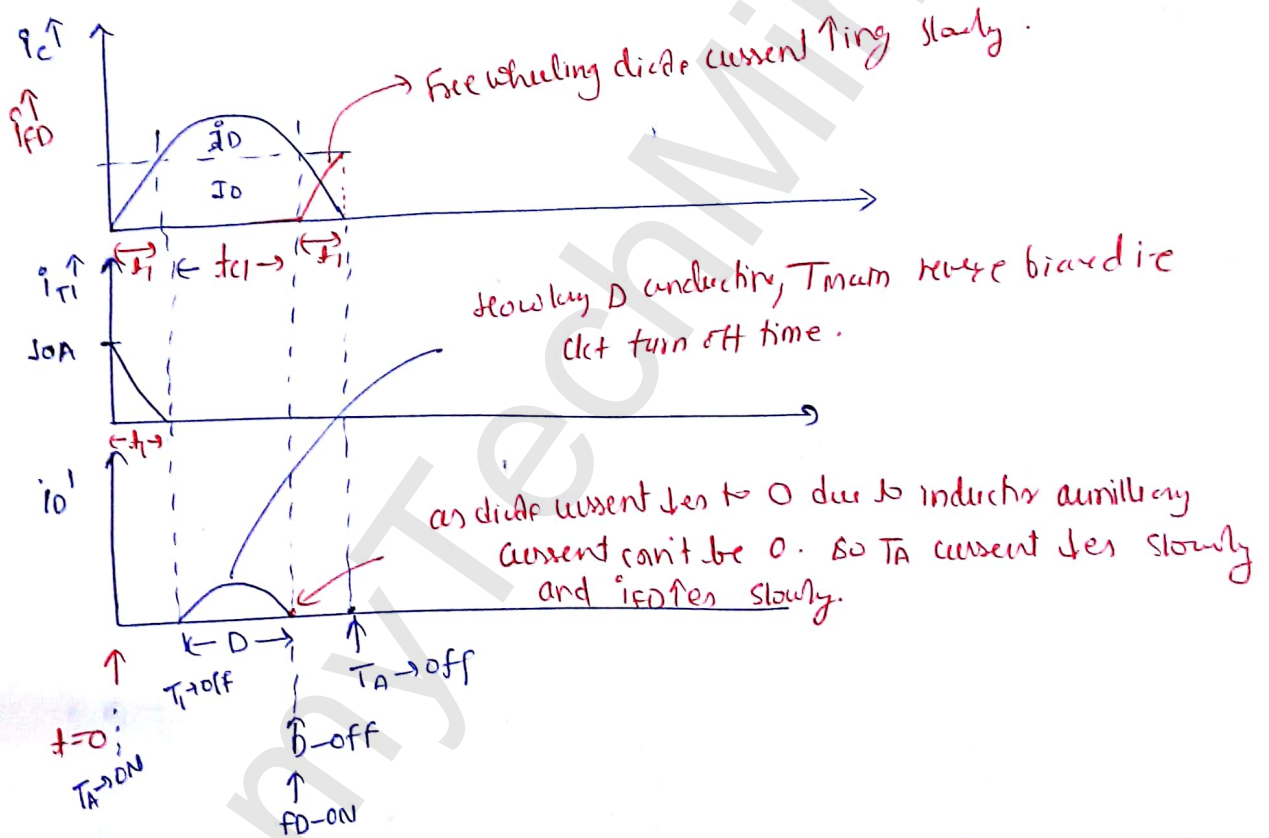

$$t_f = 10 \mu\text{sec}$$


$$t_{cl} = \pi \sqrt{LC} - 2t_f$$

$$= 198.6 \mu\text{s} - 2(10 \mu\text{s})$$

$$= 178.6 \mu\text{sec}$$



Q For a voltage commutated thyr. ckt shown in fig cap<sup>c</sup> is initially charged to  $V_s$  voltage with polarity shown in fig Find the ckt turn off time of main thyristor

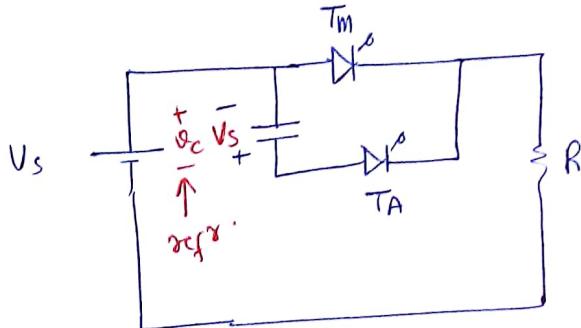$C = 10\mu F$  ,  $R = 5\Omega$  ,  $V_s = 200V$




Soln

at  $t=0$   $T_A \rightarrow ON$

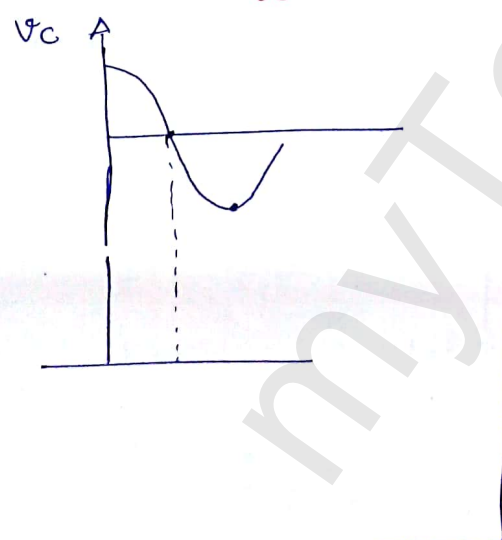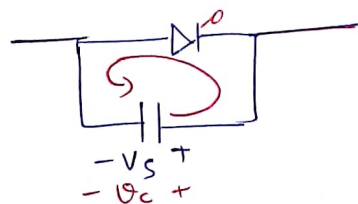


By Sir.

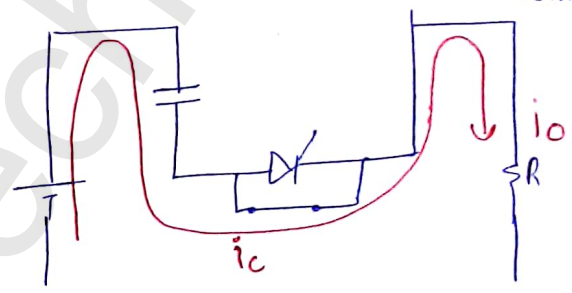at  $t=0$   $T_A \rightarrow ON$   $T_m \rightarrow off$  (Immediately)  
i.e impulse commutation




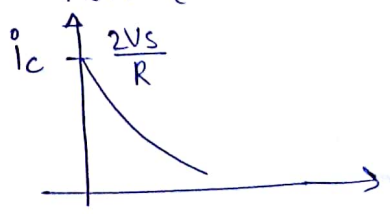RC N/w, exponential decay. *of cap<sup>c</sup> is*  
i.e changing current  $\rightarrow$  exponential decay.  
*so ch volt cap<sup>c</sup> voltage will be exponential*  
here  $i_c$  and  $i_o$  are same



at the end of mode cap<sup>c</sup> voltage opposite

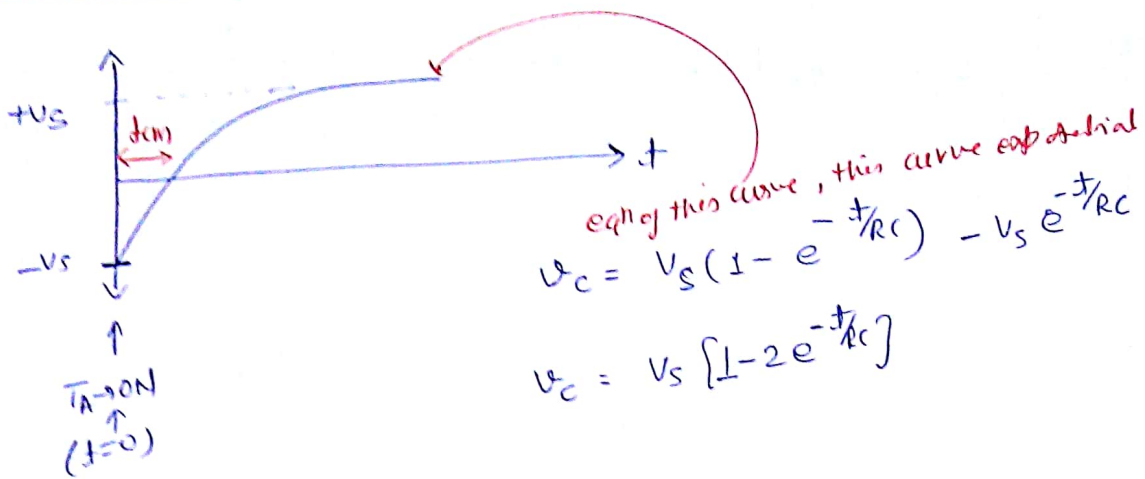$V_c(t=0) = -V_s$   
 $V_c[\text{final value}] = +V_s$



At  $t = t_{cm}$

$V_c = 0$


$0 = V_s(1 - 2e^{-t_{cm}/RC})$

$t_{cm} = RC \ln 2$


$t_{cm} = 34.65 \mu\text{sec}$

Ckt turn off time of main thyristor.

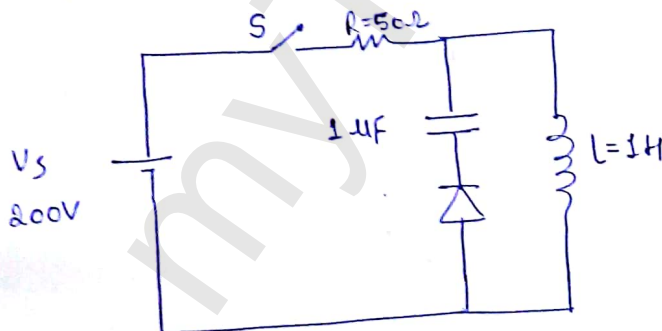Q4 In the ckt in the fig the switch S closed at  $t=0$  and opens after 10ms sec what will be the current in R, L and voltage across the capacitor after 9ms sec when the switch is open. assume diode to be ideal  
 $V_s = 200\text{V}$   $R = 50\Omega$   $C = 1\mu\text{F}$   $L = 1\text{H}$



Soln at  $t=0$

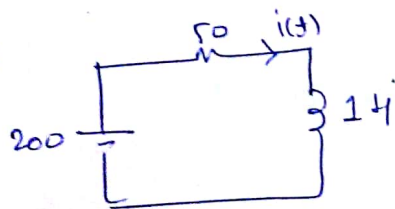

$i_c =$

$v = IR + L \frac{di}{dt}$

$\frac{V_{(0)}}{s} = I_{cm} R + L s I_{cm}$

$\frac{V}{s} = I(R + Ls)$   
 $\frac{V}{s(R+Ls)} = 1 - e$

$$\frac{V}{s(R+L)}$$

$$\frac{V}{R} + \frac{-VL}{R(R+L)}$$

$$\frac{V}{R} \left( 1 - \frac{k e^{-R/L t}}{L(s + \frac{R}{L})} \right)$$


$$\frac{V}{R} (1 - e^{-R/L t})$$

$$i(t) = \frac{V}{R} (1 - e^{-R/L t})$$

$$i(10) = \frac{200}{50} \left( 1 - e^{-\frac{50}{1} \cdot \frac{10}{1000}} \right)$$

$$i(10) = 4 (1 - e^{-0.5})$$


$$i(10) = 1.5738 \text{ A}$$

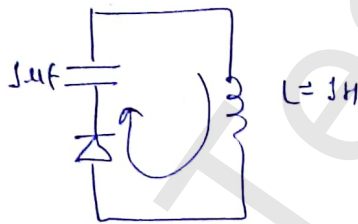

$$I = I_{cp} \cos \omega t$$


$$i(t) = V_s \sqrt{\frac{C}{L}} \cos \frac{1}{\sqrt{LC}} t \approx \frac{X_g}{1000}$$
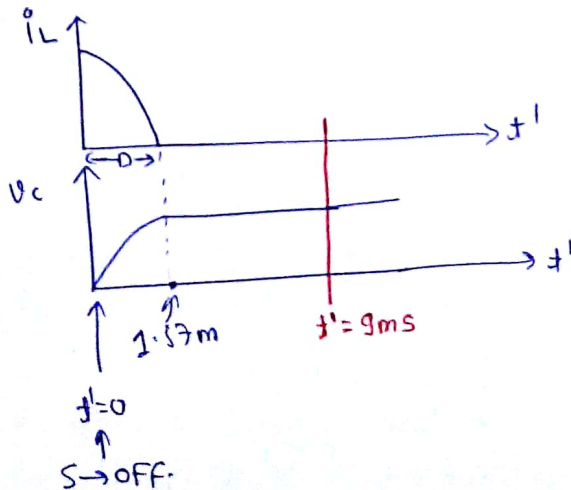
$$V_m = I_0 \sqrt{\frac{L}{C}} = 1.57 \text{ kV}$$



By Sir

S → ON

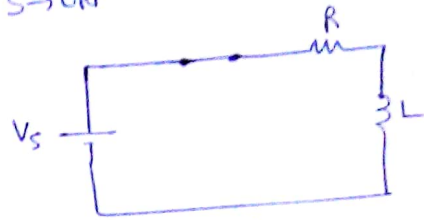


$$i = \frac{V_s}{R} (1 - e^{-t/2})$$

$$i = \frac{200}{50} (1 - e^{-50t})$$

$$(10\text{ms})^c = 4 (1 - e^{-\frac{50 \times 10}{1000}})$$

$$i(10) = 1.574 \text{ A}$$

S → open

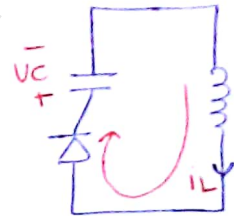

$$i_L(t=0) = 1.574 \text{ A} = I_0$$

$$\frac{1}{2} L I_0^2 = \frac{1}{2} (C V_m^2)$$

$$i_{L \text{ ring}} = I_0 \cos \omega t'$$

$$V_C \text{ ring} = V_m \sin \omega t'$$

diode will conduct for  $\frac{\pi}{2} \sqrt{LC}$

$$= 1.57 \text{ mSec}$$

find the cap<sup>r</sup> voltage in and inductor current after 1ms after switch is open.

$$i_L = I_0 \cos \omega_0 t$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-6}}} = 1000$$

$$i_L = 1.574 \cos 1000 \times 1 \times 10^{-3}$$

$$i_L = 1.574 \cos 1$$

$$i_L = 0.85 \text{ A}$$



$$V = V_m \sin \omega_0 t$$

$$V(1\text{ms}) = 1.57 \times 10^3 \sin \frac{1 \times 180}{\pi}$$


$$V(1\text{ms}) = 1.32 \text{ KV Answer}$$

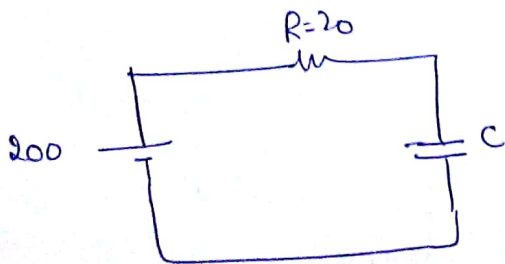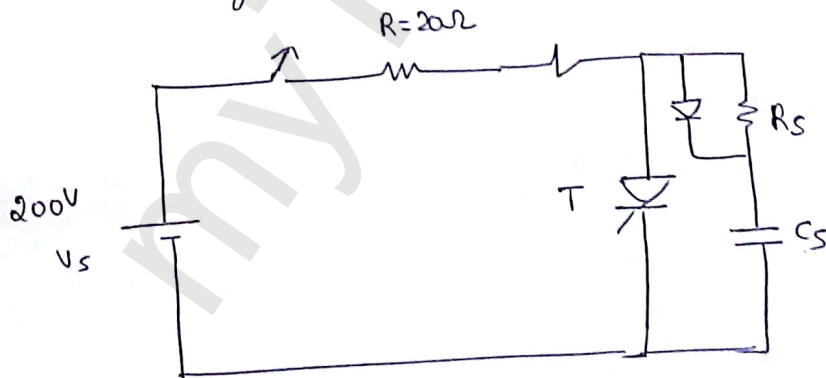Question 5 For the ckt shown in the figure  $\frac{dv}{dt}$  rating of thyristor is 400 V/μsec and its junction cap<sup>r</sup> is 25 pF the switch is closed at  $t=0$  sec @ calc the value of  $C_S$  so that the thyristor is not turned on due to  $\frac{dv}{dt}$ .




⑥ In case the max<sup>m</sup> current through the thy<sup>r</sup> is limited to 40 A determine the value of  $R_S$



$$i = -RC \frac{dv}{dt}$$

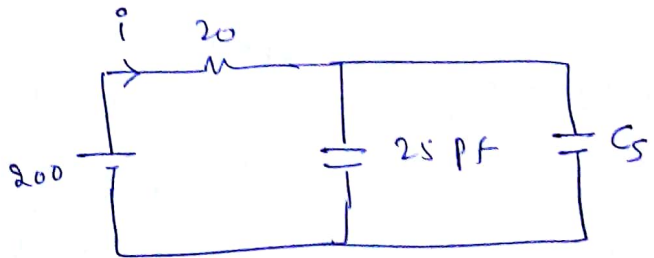

$$i = \frac{20 \phi}{2 \phi} = 10$$

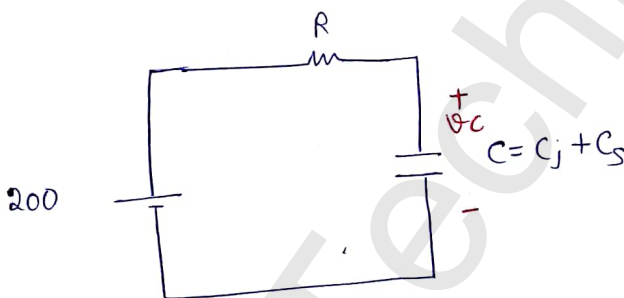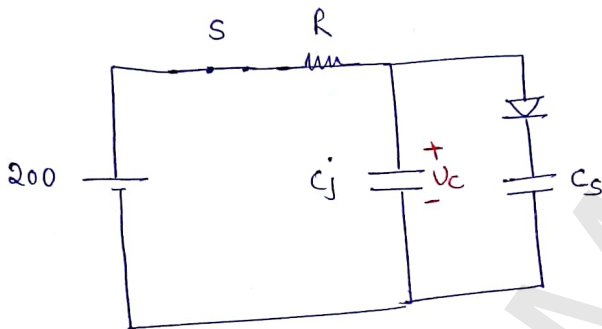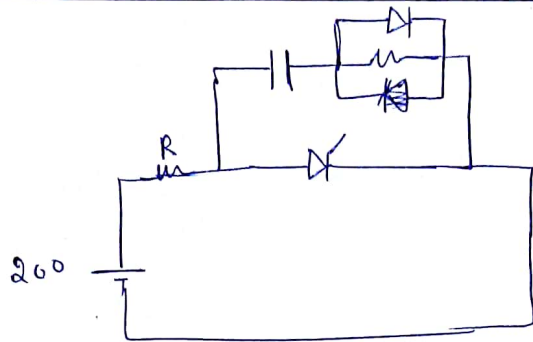


$$V_c = V_s \left[ 1 - e^{-\frac{t}{RC}} \right] + V_i e^{-\frac{t}{\tau}}$$

$\uparrow$  Final value                       $\uparrow$  initial voltage

$$V_c = V_s \left[ 1 - e^{-\frac{t}{RC}} \right]$$

For RC and RL we use exponential func<sup>n</sup>

$\left. \left( \frac{dV_c}{dt} \right) \right|_{t=0}$  —  $t=0$  bcz we are designing snubber cap<sup>r</sup> for worst case i.e. max<sup>m</sup>  $\frac{dV}{dt}$

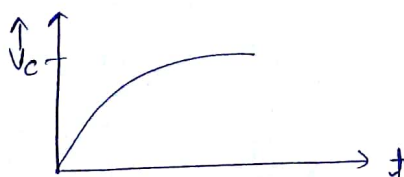

$$\left(\frac{dv_c}{dt}\right)_{t=0} = \left(\frac{dv_c}{dt}\right)_{\max} = \frac{V_s}{RC}$$

$$\left(\frac{dv_c}{dt}\right)_{\text{Rating}} = \frac{V_s}{RC}$$

$$400 \frac{V}{\mu\text{sec}} = \frac{200}{20 \times C}$$

$$C = \frac{200}{20 \times 400} = \frac{1}{40} = 0.025 \mu\text{F}$$



$$C = C_j + C_s$$

$$C \approx C_s$$

bcz  $C_j = 25 \text{ pf}$  so very small in comparison to  $\mu\text{F}$  so neglected

$$C_s = 0.025 \mu\text{F}$$

⑥

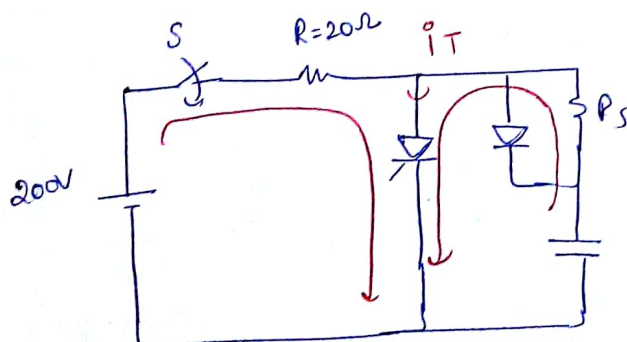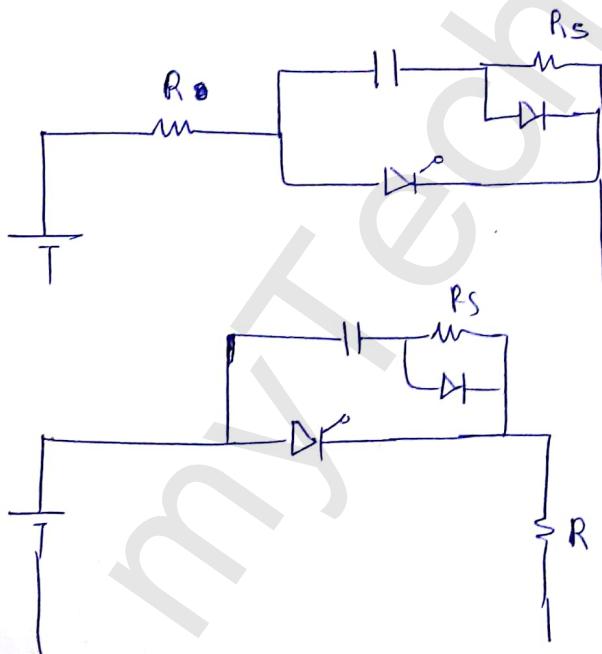



$$i_T = \frac{V_S}{R} + \frac{V_S}{R_S} = 40A$$

$$\frac{200}{20} + \frac{200}{R_S} = 40$$

$$R_S = 6.67$$



$$R_S \geq 6.67 \Omega$$

Q A SCR during turn on process has the following data Anode voltage and Anode current

Anode voltage	60V	0V
Anode current	0A	100A

during the turn on time of 5  $\mu$ sec, the anode voltage and anode current varies linearly if the ~~flickering~~ <sup>triggering</sup> freq is 100Hz find the avg power loss in the thyristor during turn on

Sol<sup>n</sup>

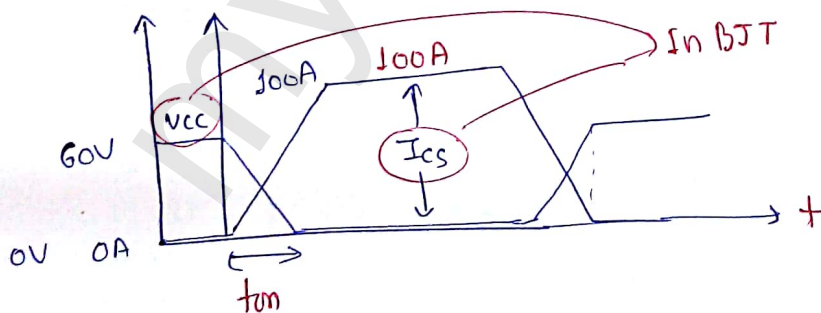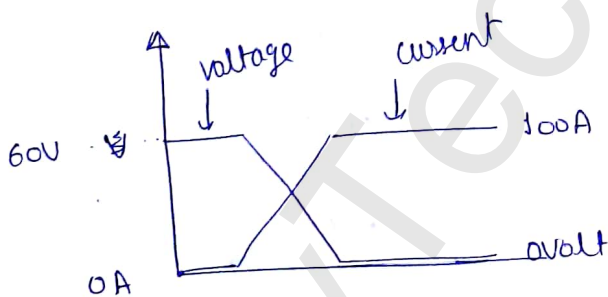

$$P_{avg} = \frac{1}{T} \int_0^{t_{on}} V_A \cdot I_A dt = \frac{VI}{6} t_{on} \cdot f$$

$$= \frac{60 \times 100}{6} \times 5 \times 10^{-6} \times 100 \times 10^3$$


$$= 10 \times 10 \times 5 \times 10^{-6} \times 10^6$$

$$= 500 \text{ watts} = 0.5 \text{ watts}$$

Q A thyristor in a power converter carries a current of the waveform shown in the figure the peak value of current is 300A. The static char of the thyristor is given by.


$$V = 1.05 + 0.95 \times 10^{-3} \times I_T$$

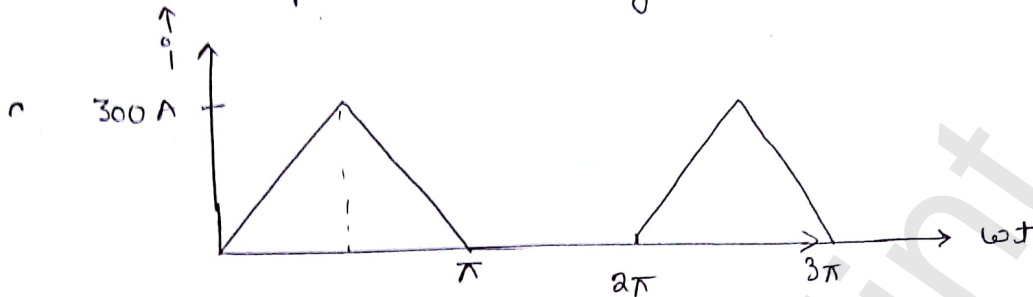determine the power loss in the thyristor.




Soln

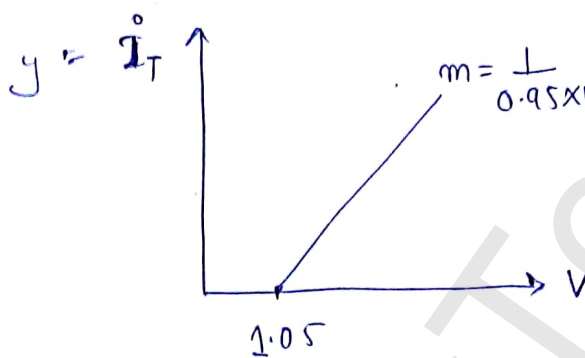Some time directly V, I curve given, some time eqn given  
Static Char means VI char



$$m = \frac{1}{0.95 \times 10^{-3}} = \frac{100000}{0.95} = 105263$$

$$y = mx + c$$

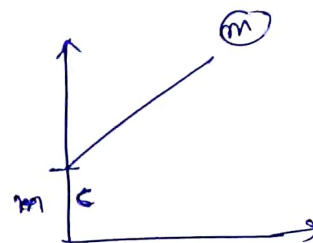


$$x = my + c$$

$$\frac{100000}{0.95}$$

$$V = 1.05 + 0.95 \times 10^{-3} \times I_T$$

$$\text{at } I_T = 0 \quad V = 1.05$$
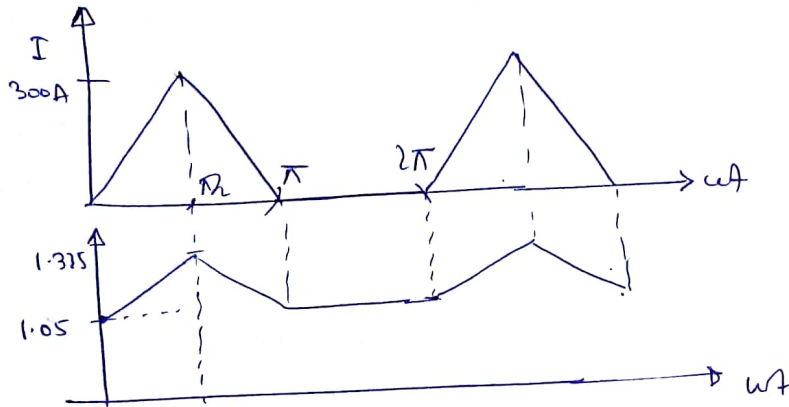
$$\text{at } I_T = 300 \quad V = 1.05 + 0.95 \times 10^{-3} \times 300 = 1.335$$



$$\begin{aligned}
 P_{avg} &= \frac{1}{T} \int_0^T v \times i \, dt \\
 &= \frac{1}{2\pi} \int_0^{2\pi} 2 \times \left( \frac{300 \times 2}{\pi} \right) \omega t \times \left( 1.05 + \frac{0.285 \times 2 \omega t}{\pi} \right) d\omega t \\
 &= \frac{1}{2\pi} \int_0^{2\pi} 1.05 \times \left( \frac{1200}{\pi} \right) \omega t \, d\omega t + \int_0^{2\pi} \frac{1200}{\pi} \omega t \frac{0.285 \times 2 \omega t}{\pi} d\omega t \\
 &\frac{1}{2\pi}
 \end{aligned}$$



By Sir

$$\begin{aligned}
 P_{avg} &= \frac{1}{2\pi} \int_0^{2\pi} V_T \cdot i_T \, d(\omega t) \\
 &= \frac{1}{2\pi} \int_0^{2\pi} (1.05 + 0.95 \times 10^{-3} i_T) \cdot i_T \, d(\omega t) \\
 &= \frac{1}{2\pi} \int_0^{2\pi} 1.05 i_T \, d\omega t + \frac{1}{2\pi} \int_0^{2\pi} 0.95 \times 10^{-3} i_T^2 \, d\omega t \\
 P_{avg} &= 1.05 (I_T)_{Avg} + 0.95 \times 10^{-3} (I_T)_{rms}^2
 \end{aligned}$$

Q The gate cathode char of an SCR is given by  $V_g = 0.5 + 8I_g$  for triggering of freq of 400 Hz the duty cycle is 0.1 compute the value of resistance to be connected in series with the gate ckt.

A rectangular trigger pulse applied to the gate ckt has an amplitude of 12 volts.

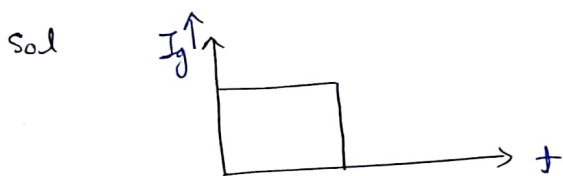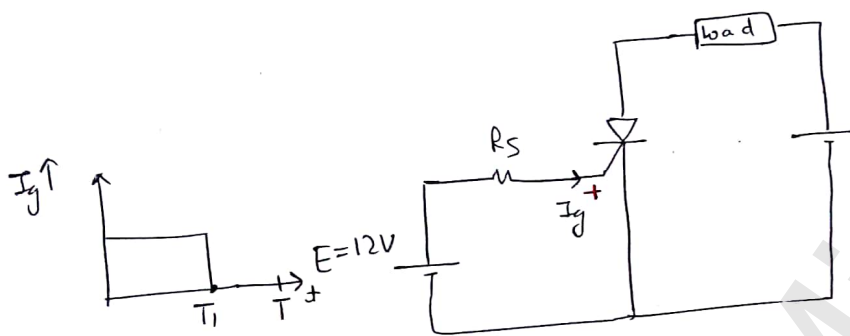The thyristor has an avg gate power loss of 0.5 watt



$$S = \frac{T_1}{T}$$

$$T_1 = TS = \frac{S}{F} = \frac{0.1}{400} = 250 \mu\text{SEC}$$

$$T_1 > 100 \mu\text{s}$$

$\therefore$  consider  $I_g$  as continuous pulse

$$\therefore V_g I_g = P_{gAV}$$

$$V_g I_g = 0.5$$

$$V_g = 0.5 + 8I_g$$

$$V_g I_g = 0.5 I_g + 8 I_g^2$$

$$8 I_g^2 + 0.5 I_g - 0.5 = 0$$

$$0.5 = 0.5 I_g + 8 I_g^2$$

$$\frac{-0.5 \pm \sqrt{(0.5)^2 + 4 \times 8 \times 0.5}}{16}$$

$$= \frac{-0.5 \pm \sqrt{2.5 + 16}}{16} = \frac{4.03 - 0.5}{16}$$

$$I_g = 0.22 \text{ A}$$

$$V_g = \frac{0.5}{0.22} = 2.27$$

$$E = I_g R_s + V_g$$

$$12 = 0.22 \times R_s + 2.27 \text{ V}$$


$$R_s = 44.21 \Omega$$

← this much resistance added to limit the gate current.

Q The specification sheet for an SCR we max<sup>m</sup> rms on state current as 50 A. if it is used in a resistive ckt compute its avg on state current rating for conduction angle of 60° if the current waveform is

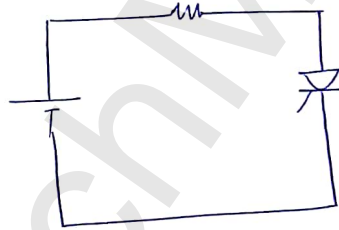
- (a) Half sine wave
- (b) Rectangular wave.

Sol<sup>n</sup>.  $i_{T \text{ rms}} = 50 \text{ A}$



By Sir

(a)

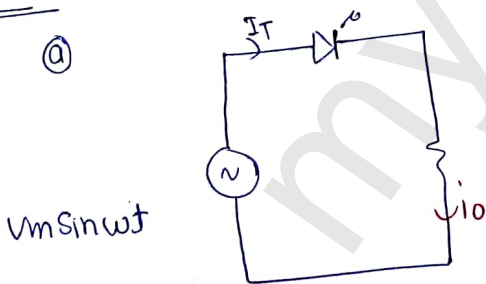


$$T \rightarrow \alpha \text{ to } \pi$$

$$T \rightarrow (\pi - \alpha) = \frac{\pi}{3} \text{ rad}^n$$

$$\alpha = \frac{2\pi}{3} \text{ rad}^n = 120^\circ$$


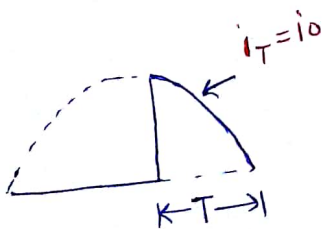
$$(I_T)_{\text{avg}} = \frac{(I_T)_{\text{RMS}}}{\text{FF}} = \frac{50}{\text{FF}}$$



$$\text{FF} = \frac{i_T \text{ RMS}}{i_T \text{ avg.}} = \frac{I_{or}}{I_o} = \frac{V_{or}/R}{V_o/R} = \frac{V_{or}}{V_o}$$

$$\frac{V_{or}}{V_o} = \frac{\frac{V_m}{\sqrt{2 \cdot 2\pi}} \left[ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}}{\frac{V_m}{2\pi} (1 + \cos \alpha)}$$

(b) Rectangular Pulse

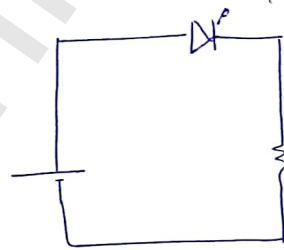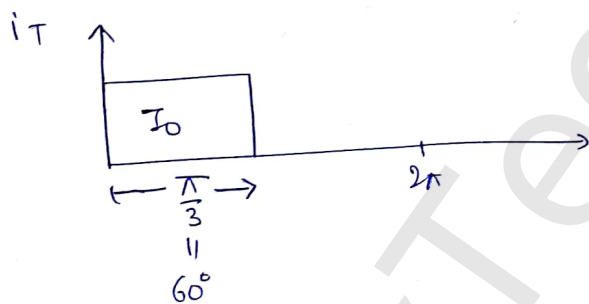

$$FF = \frac{(I_T)_{rms}}{(I_T)_{avg}}$$

$$FF = \frac{I_0 \cdot 6}{\sqrt{6} I_0}$$

$$FF = \sqrt{6} = 2.45$$

$$I_{Tavg} = \frac{I_0 \times \frac{\pi}{3}}{2\pi} = \frac{I_0}{6}$$

$$I_{Tavg}^{rms} = \sqrt{\frac{1}{2\pi} \left( I_0^2 \times \frac{\pi}{3} \right)}$$

$$\frac{I_0^2 \times \pi}{3 \times 2\pi} = \frac{I_0}{\sqrt{6}}$$

$$(I_T)_{avg \text{ rating}} = \frac{(I_T)_{rms \text{ rating}}}{FF} = \frac{50}{\sqrt{6}} = \frac{50}{2.45} = 20.408$$

Q A power switching device is rated for 600 V and 30 A the device has an on-state voltage drop of 1.5 V to 2.4 volts for conduction current in the range of 15-30 amp. the device has a leakage current of 5 mA while blocking 600V. find the a) max<sup>m</sup> conduction power loss

Sol<sup>n</sup> ON state V-drop 1.5 V to 2.4 V  
 conduction current (I<sub>a</sub>) 15 to 30 A


⑥ find the max<sup>m</sup> blocking power loss

Sol<sup>n</sup> max<sup>m</sup> conduction loss =  $2.4 \times 30 = 72 \text{ watt}$

Blocking loss =  $600 \text{ V} \times 5 \times 10^{-3} = 3 \text{ watt}$



conduction loss very high > Switching losses > Blocking loss (least)  
 ↑ ↑  
 depend on  $f_{in}$  most of the time we neglect

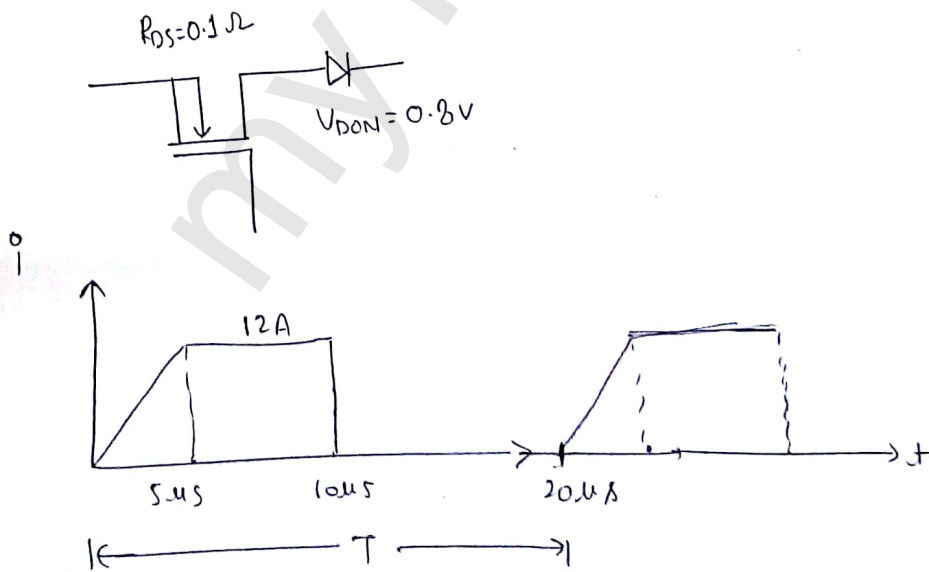Q A composite switch used in a power converter is shown in figure the periodic current through the switch is also shown



Find the power loss in the mosfet and the diode in a composite switch.

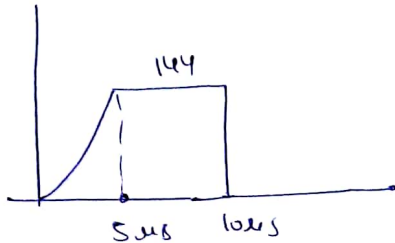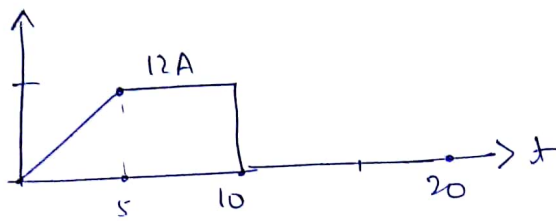Sol<sup>n</sup> finding rms value of current



$$I_{rms}^2 = \int_0^{5 \mu\text{sec}} \left( \frac{12}{5 \times 10^{-6}} \right)^2 t^2 dt + (144 \times 5 \mu\text{sec})$$

$$I_{rms} = \sqrt{\frac{1}{20 \times 10^{-6}} \left[ \frac{12}{5 \times 10^{-6}} \frac{t^3}{3} + 720 \times 10^{-6} \right]}$$

$$I_{rms}^2 = \frac{1}{20} \left[ \frac{12 \times 12 \times 125 \times 10^{-6}}{5 \times 5 \times 3} + 720 \right] = 48 \text{ A}^2$$

$$I_{rms} = 6.93$$


$$\text{Power loss in MOSFET} = I_{rms}^2 \times R_{gs} = 48 \times 0.1 = 4.8 \text{ watts}$$

$$I_{avg} = \frac{\left[ \frac{1}{2} \times 5 \times 12 + 5 \times 12 \right] \times 10^{-6}}{20 \times 10^{-6}} = 4.5 \text{ A}$$

$$\text{Power loss in diode} = V_{\text{drop}} \times I_{avg} = 0.8 \times 4.5 = 3.6 \text{ watts}$$



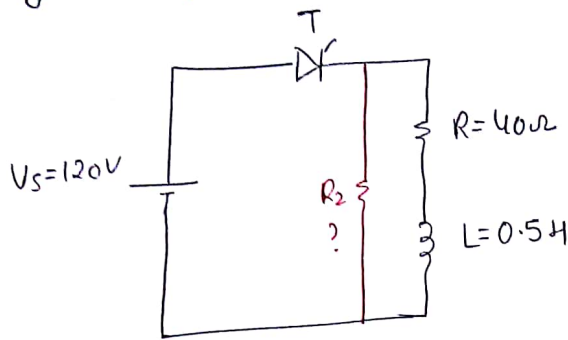Q. the latching current of a thyristor circuit as shown below is 20mA



To perfectly trigger the thyristor the additional resistance that must be connected in parallel to the load if the duration of firing pulse is 50μsec is \_\_\_\_\_ kΩ.

Sol<sup>n</sup>

$$i = \frac{V}{R} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R} = \frac{0.5}{40} = \frac{1}{80}$$


$$i = \frac{120}{40} (1 - e^{-t/\tau})$$

$$i_A \quad 20\text{mA} = \frac{120}{40} (1 - e^{-\frac{50 \times 10^{-6} R}{L}})$$

$$\frac{20}{1000 \times 10^{-3}} = 30 (1 - e^{-\frac{50 \times 10^{-6} R}{L}})$$

$$\text{at } t = 50\mu\text{s} \quad i_A = 30 (1 - e^{-\frac{50 \times 10^{-6} R}{L}})$$
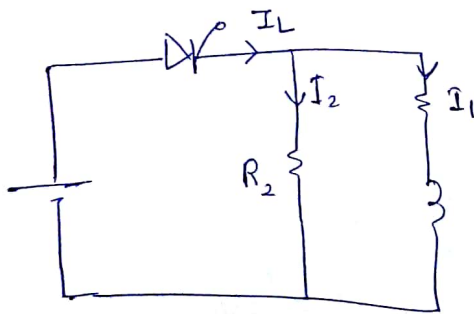
$$i_A = 11.97\text{mA} < I_L \quad \therefore \text{T fails to turn on}$$



$$I_L = I_1 + I_2$$

$$I_2 = I_L - I_1$$

$$= 20\text{mA} - 11.97\text{mA}$$

$$I_2 = 8.03\text{mA}$$

$$\frac{V_S}{R_2} = 8.03 \times 10^{-3}$$

$$R_2 = \frac{120}{8.03 \times 10^{-3}}$$



$$R_2 = 14.94\text{k}\Omega$$

If  $R_2$  is  $<$  than 14.94 (no problem) but if  $R_2 > 14.94$  the  $I_1 + I_2$  will less than latching current.



chapter - 2

Q A Single phase bridge rectifier consist of 1 SCR and 3 diode operating with firing angle of  $45^\circ$  find the avg load current and power delivered to the load where  $R = 8.356 \Omega$   $L = 8 \text{ mH}$   $E = 100 \text{ V}$  . assume that the load current is constant the ac source voltage is  $220 \text{ V}$ ,  $50 \text{ Hz}$ .

Sol<sup>n</sup>

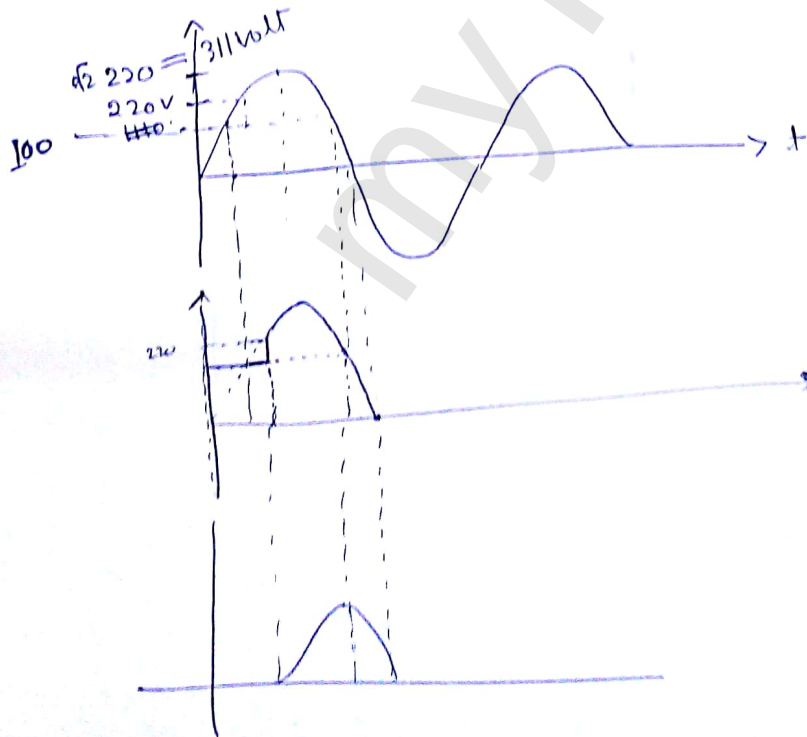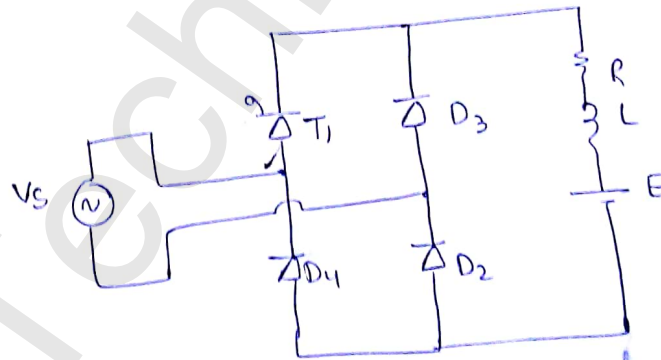

$$311 \sin 45^\circ =$$

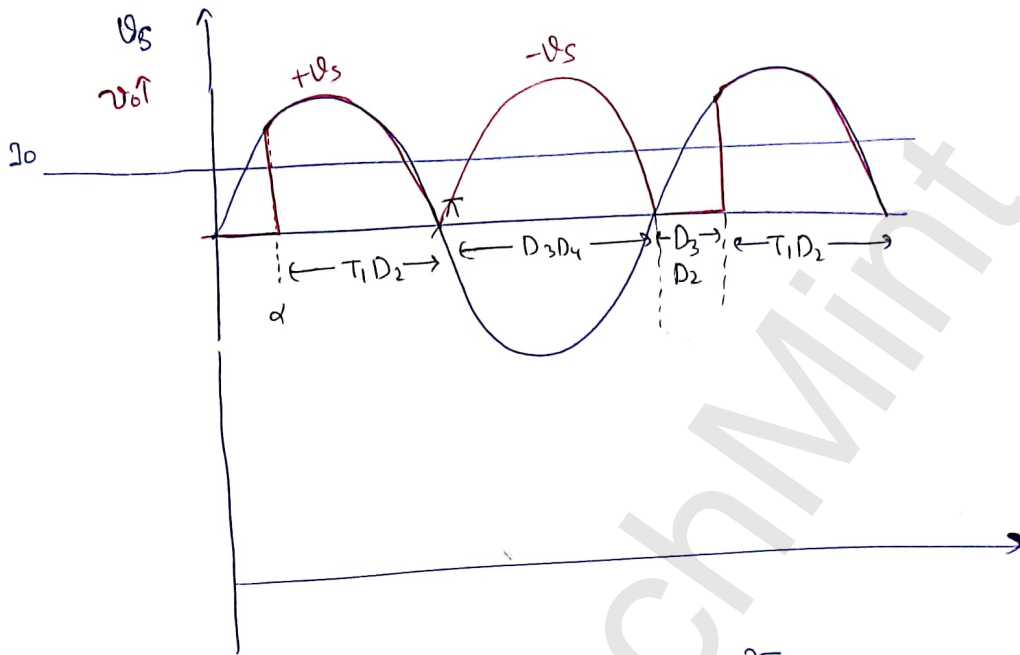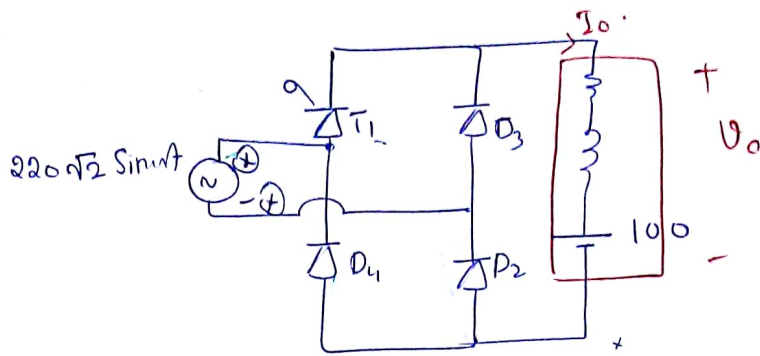

$$V_o = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t) + \int_{\pi}^{2\pi} -V_m \sin \omega t \cdot d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[ V_m (\cos \alpha - \cos \pi) + V_m (\cos(2\pi) - (\cos \pi)) \right]$$

$$\left\{ V_m \left( \frac{1}{\sqrt{2}} + 1 \right) + V_m [1 + 1] \right\}$$

$$\frac{V_m}{2\pi} \left[ 2 + 1 + \frac{1}{\sqrt{2}} \right]$$

$$V_o = \left( 3 + \frac{1}{\sqrt{2}} \right) \frac{V_m}{2\pi} = 183.56 \text{ V}$$

$$V_o = E_b + I_o R_a$$



$$I_o = \frac{V_o - E_b}{R_a} = \frac{183.56 - 100}{8.55} = I_o = 10 \text{ A}$$

$$P_{load} = V_o I_o$$

$$= 183.56 \times 10$$

$$= 1835.6 \text{ watt}$$

○ Replace  $D_2$  with  $T_2$

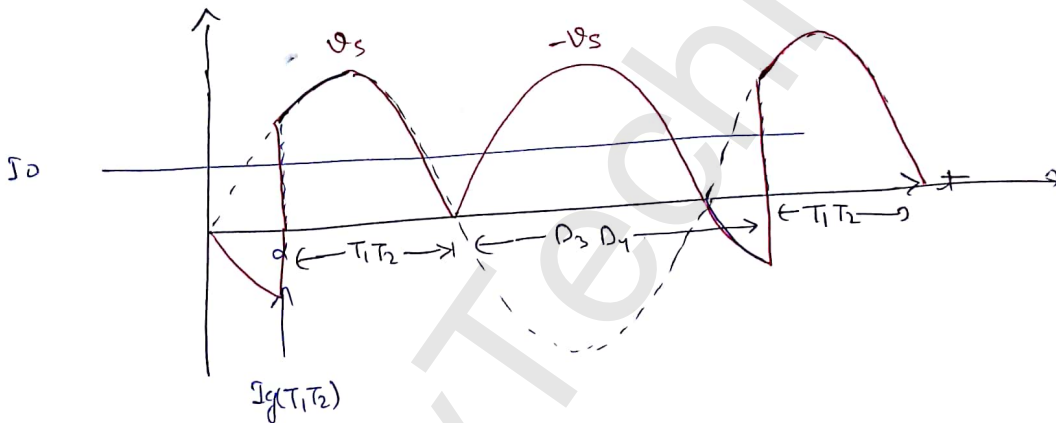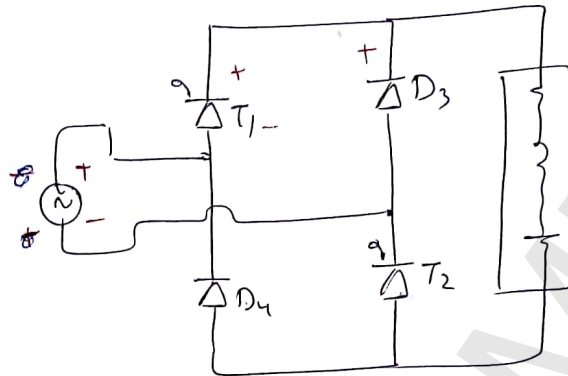

$$V_o = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi+\alpha} -V_m \sin \omega t \, d(\omega t) \right]$$

$$\frac{1}{2\pi} \left[ V_m (\cos \alpha - \cos \pi) - V_m \{ \cos \pi - \cos(2\pi + \alpha) \} \right]$$



$$V_m \frac{1}{2\pi} \left[ \left( \frac{1}{\sqrt{2}} + 1 \right) - \left( -1 - \left[ \cos 2\pi \cos \alpha - \sin 2\pi \sin \alpha \right] \right) \right]$$



$$- \left( -1 - \frac{1}{\sqrt{2}} \right)$$

$$\left[ \left( 1 + \frac{1}{\sqrt{2}} \right) + \left( 1 + \frac{1}{\sqrt{2}} \right) \right] = \frac{V_m}{\pi} \left[ 1 + \frac{1}{\sqrt{2}} \right] = \frac{220\sqrt{2}}{\pi} \left[ 1 + \frac{1}{\sqrt{2}} \right]$$

$$= 169.00$$

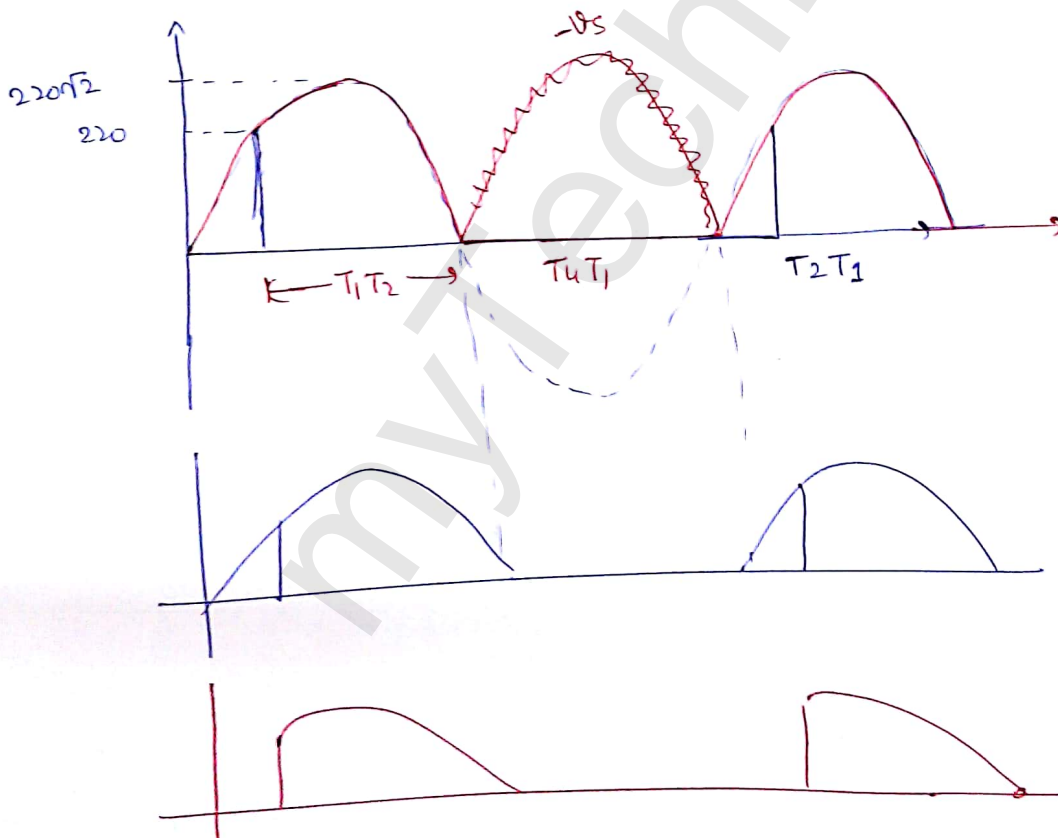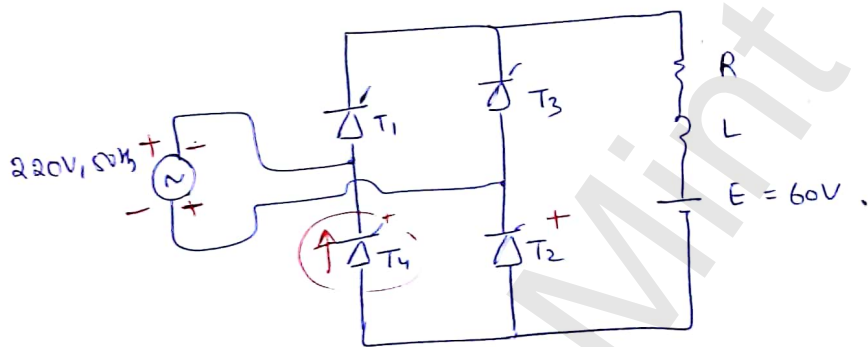Q A single phase full converter feeds power to RLE load with  $R=10\Omega$ ,  $L=6mH$ ,  $E=60V$  the ac source voltage is  $220V, 50Hz$  in case one of the 4 SCR conducts over vcted due to a fault find the avg value of load current by assuming the load current as continuous and firing angle  $45^\circ$



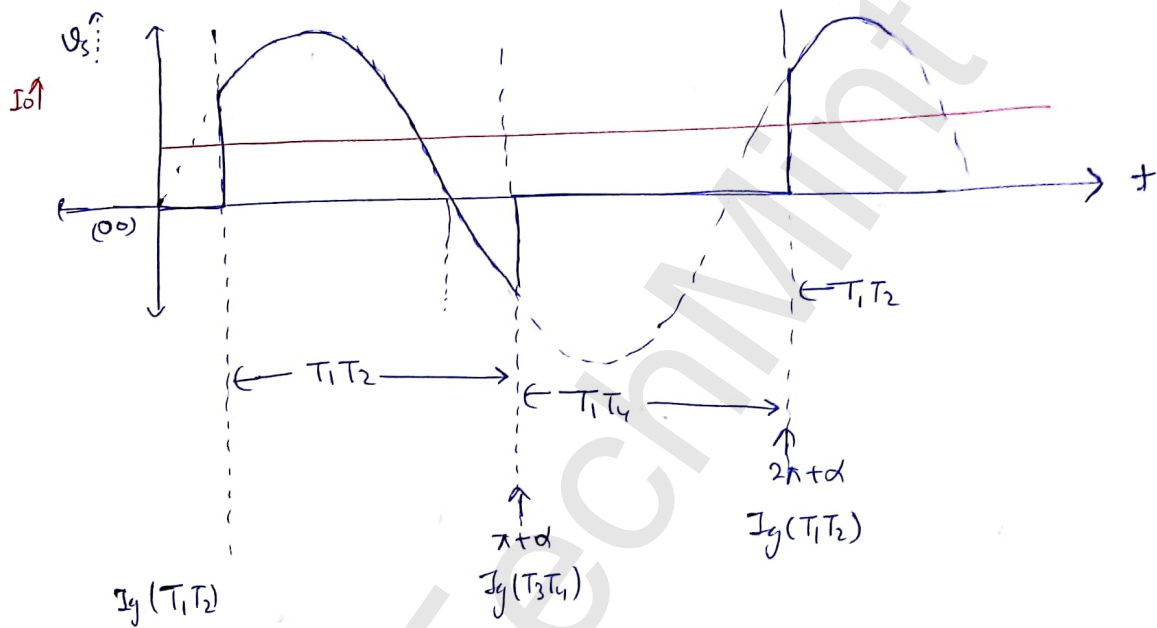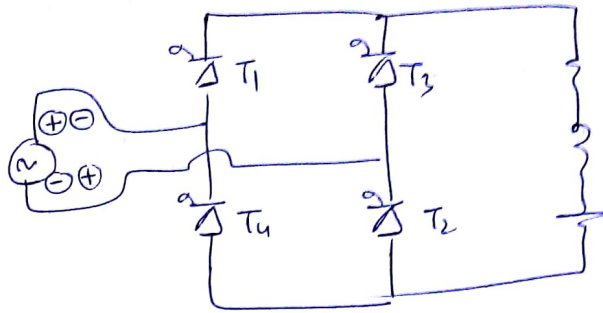

$$V_o = \int_{\alpha}^{\pi + \alpha} V_m \sin \omega t \, d\omega t = \frac{V_m \cos \alpha}{\pi}$$

$$= \frac{220\sqrt{2}}{\pi} \times \cos 45^\circ$$

$$V_o = 70.028 \text{ V}$$



$$V_o = E_b + I_o R_a$$

$$I_o = \frac{V_o - E_b}{R_a} = \frac{70 - 60}{10} = 1 \text{ A}$$

Q) A single phase one pulse converter with RLE load has the following parameters: supply voltage 230V, 50Hz,  $R = 2\Omega$ ,  $L = 1\text{mH}$ ,  $E = 120\text{V}$  extinction angle  $\beta = 220^\circ$  and  $\alpha = 25^\circ$  firing angle just before the SCR


- (a) calc the voltage across the thyristor at the instant when SCR is triggered.  
 (b) calc the ~~current~~ ~~just before the SCR is triggered.~~  
 (b) Find the voltage that appears across the SCR immediately at the instant when at which it stops conducting  
 (c) PIV of the SCR

Sol<sup>n</sup>

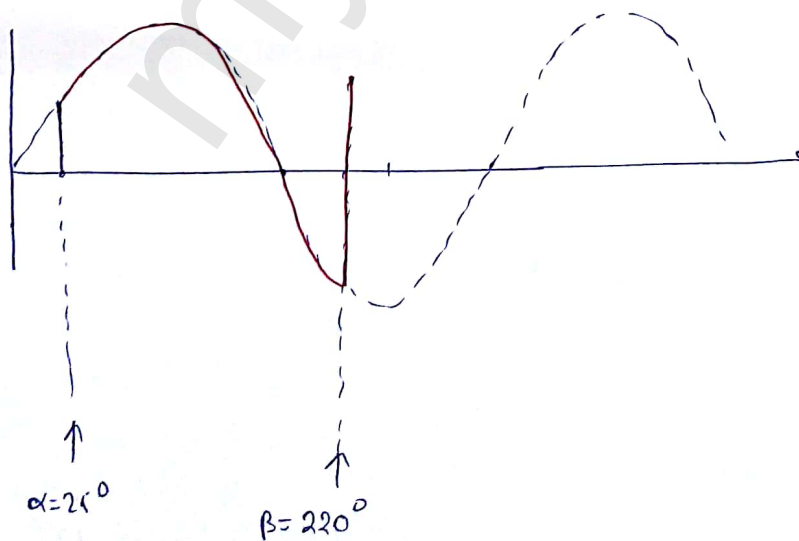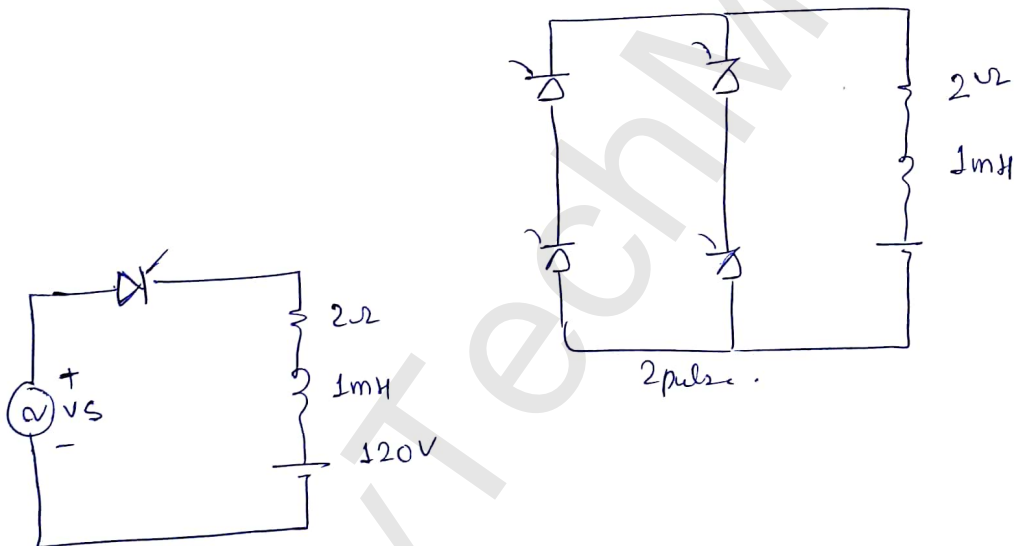



By Sir

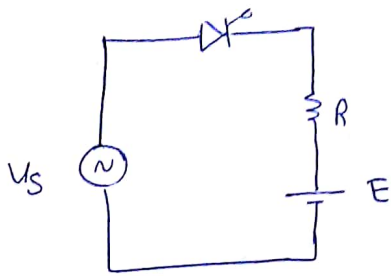

at  $\alpha^-$

$$-V_s + V_T + E = 0$$

$$V_T = V_s - E$$

$$V_T = V_m \sin \alpha - E$$

$$= 220\sqrt{2} \sin 25 - 120$$

$$= 17.46 \text{ V}$$

at  $\beta^+$


$$V_T = V_m \sin \beta - E$$

$$= 230\sqrt{2} \sin 220 - 120$$


$$= -329 \text{ V}$$

Q A 3 $\phi$  Half wave phase controlled rectifier delivers power to a resistive load of  $10 \Omega$ . If to the rectifier is  $400 \text{ V}$ ,  $50 \text{ Hz}$ , 3 $\phi$  ac supply find the power delivered to the load at  $\alpha = 60^\circ$  and  $\alpha = 15^\circ$

Soln

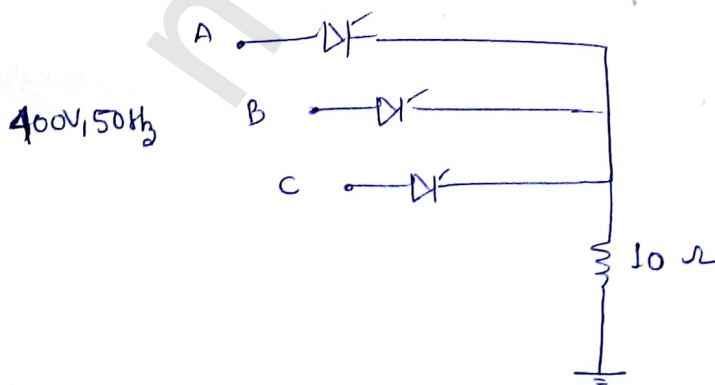

2 pulse

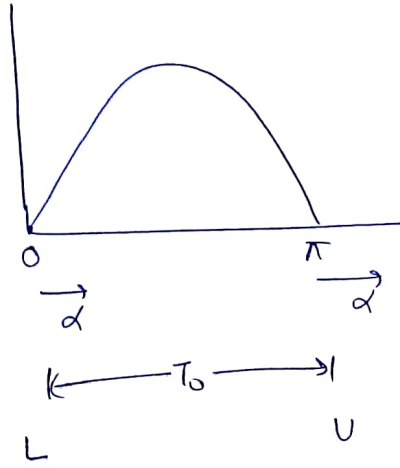

for inductive load  $\rightarrow (\theta + d)$

for resistive load upper limit =  $\pi$  only  $T_0$   
 $(\pi + \alpha) \rightarrow$  2 pulse ( $\pi$ )  
 $(\frac{5\pi}{6} + \alpha) \rightarrow$  3 pulse ( $\frac{2\pi}{3}$ )  
 $(\frac{\pi}{3} + \alpha) \rightarrow$  6 pulse ( $\frac{\pi}{3}$ )

$T_0 = \frac{2\pi}{m} = \pi$  ← no. of pulse


Inductive load [continuous conduction]  $V_{do}$  cond

2 pulse  $\Rightarrow V_o = \frac{1}{\pi} \int_{\alpha+d}^{\pi+d} V_m \sin \omega t \, d\omega t = \frac{2\sqrt{2} V_m}{\pi} \cos \alpha$

3 pulse

$T_0 = \frac{2\pi}{3} =$

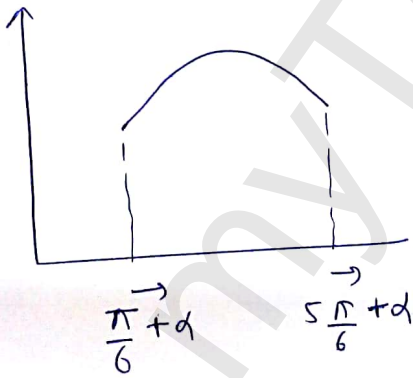
3 pulse  $= V_o = \frac{1}{(\frac{2\pi}{3})} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_{mpn} \sin \omega t \, d\omega t = \frac{3\sqrt{3} V_{mpn} \cos \alpha}{2\pi}$



$= \frac{3V_m}{2\pi} \cos \alpha$   
 $V_{do} \cdot \cos \alpha$

6 pulse  $\Rightarrow V_o = \frac{1}{\pi/3} \int_{\pi/3+\alpha}^{\frac{2\pi}{3}+\alpha} V_{mL} \sin \omega t \, d\omega t = \frac{3V_m}{\pi} \cos \alpha$   
 $= V_{do} \cdot \cos \alpha$

6 pulse

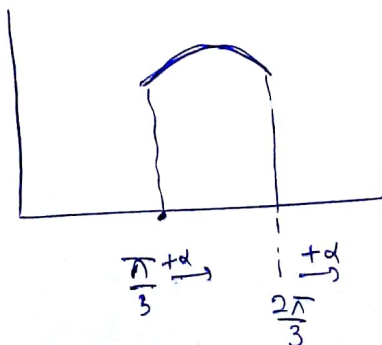

Inductive load continuous cond<sup>c</sup> waveform will remain same for PL, RLE

Ex.

$$V_{or} = \frac{V_m}{\sqrt{2 \cdot T_0}} \left[ (1-L) + \frac{1}{2} (\sin 2L - \sin 2V) \right]^{\frac{1}{2}}$$

↳ when using for 3 pulse  $V_m = V_{mph}$

↳ 6 pulse  $V_m = \frac{1}{2} V_{mnd}$

Resistive load

L	U	To
2 pulse (0+d)	( $\pi$ )	$\pi$
$\alpha \leq \pi/6, U \leq \pi$		
3 pulse ( $\frac{\pi}{6}+d$ )	( $\frac{5\pi}{6}(\frac{5\pi}{6}+\alpha)$ )	$\frac{2\pi}{3}$

$$V_o = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow \text{Discont.}$$

$$V_o = \frac{1}{2\pi/3} \int_{\pi/6+d}^{5\pi/6+d} V_{mph} \sin \omega t \, d\omega t = \frac{3\sqrt{3}}{2\pi} V_{mph} \cos \alpha = \frac{3V_{LHL}}{2\pi} \cos \alpha = V_{do} \cos \alpha$$

RL, RLE  
R ( $\alpha \leq \pi/6$ )

For R also here if  $\alpha < \pi/6$  we get continuous waveform

when  $\alpha \geq \pi/6, U \geq \pi$



3 pulse ( $\frac{\pi}{6}+d$ )	( $\frac{5\pi}{6}(\frac{5\pi}{6}+\alpha)$ )	(FD)
Discontinuous		

$$\therefore V_o = \int_{\pi/6+d}^{\pi} V_{mph} \sin \omega t \, d\omega t = \frac{V_{mph}}{3\pi/3} [1 + \cos(\frac{\pi}{6} + \alpha)]$$

inflow  $\pi$  to ( $\frac{5\pi}{6} + \alpha$ ) FD will conduct { if it is a 3 pulse + Free Wheel Diode }

Q For 3 pulse  $\alpha = 90^\circ$  draw wave form for inductive load

L	U
$(\frac{\pi}{6} + \alpha)$	$(\frac{5\pi}{6} + \alpha)$
$(30 + 90)$	$(150 + 90)$
$120^\circ$	$240^\circ$

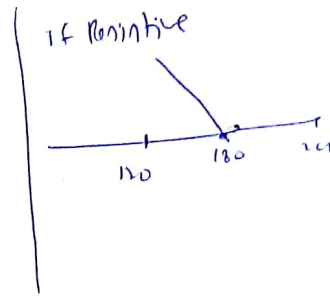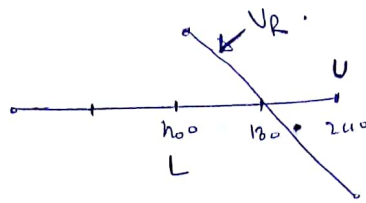


We use shortcut for reference waveform VR.


Q Draw the waveform for  $\alpha = 0$ , 3 pulse,

inductive load.

L	U
$(\frac{\pi}{6} + \alpha)$	$(\frac{5\pi}{6} + \alpha)$
$(30 + 0)$	$(150 + 0)$

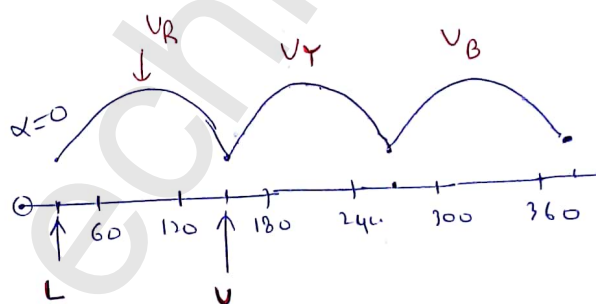


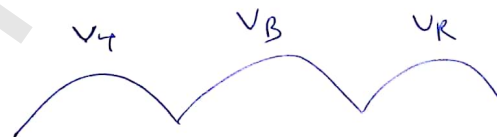if in exam  $V_T = V_m \sin \omega t$  (given)



Q  $\alpha = 180^\circ$ ,

L	U
$(30 + 180^\circ)$	$(150 + 180^\circ)$
$210^\circ$	$(330)$

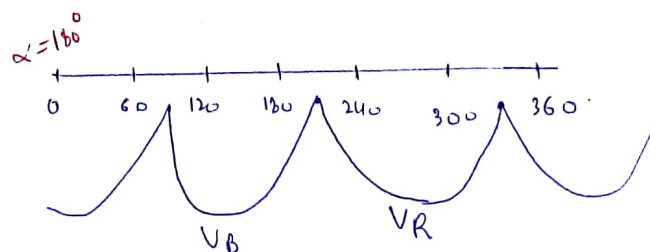

at  $\alpha = 0$  max<sup>m</sup> avg voltage.

at  $\alpha = 180 + 180^\circ$  max<sup>m</sup> -ve avg voltage.

For inductive load

$$0 \leq \alpha \leq 180$$

↑                          ↑

max<sup>m</sup> +ve avg      max<sup>m</sup> -ve avg  
voltage                          voltage

$$+\frac{3V_m}{2\pi}$$

$$-\frac{3V_m}{2\pi}$$

$$V = \frac{3V_m}{2\pi} \cos \alpha$$

For resistive load

$$0 \leq \alpha \leq 150$$

↓                          ↓

(No) max                  0V

$$\frac{3V_m}{2\pi}$$

$$V = \frac{3V_m}{2\pi} \cos \alpha$$


draw wave fm  $\alpha = 150^\circ$  for Induct for 3 pul.

$$\left(\frac{\pi}{6} + \alpha\right) \quad \left(\frac{5\pi}{6} + \alpha\right)$$

L                          U

$$(30 + 150) \quad (150 + 150)$$

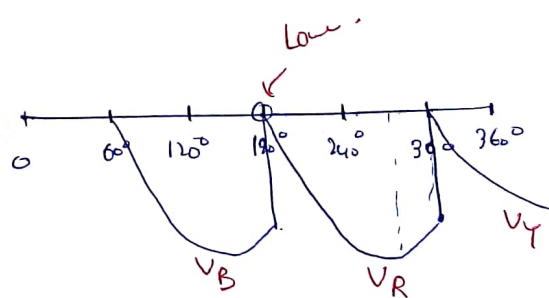$180^\circ$                    $300^\circ$






For  $\alpha = 150^\circ$  For resistive remove -ve voltage i.e we will get no output

draw<sup>back</sup> of 3 pulse in that source current contain dc which saturate Xmer. are.


**Grpulse**

Let  $V_{RY} = V_m \sin \omega t$

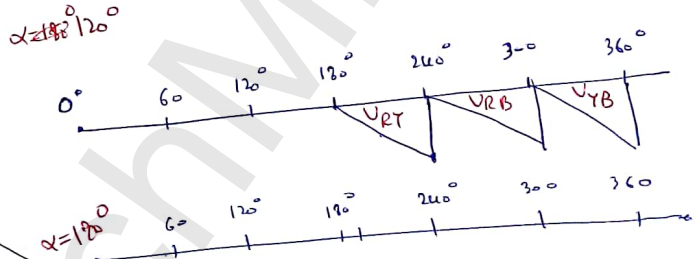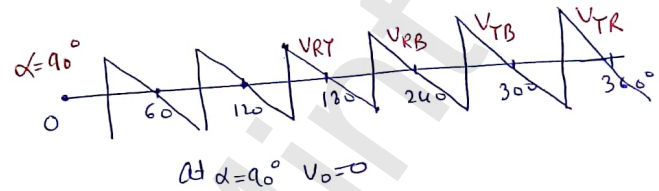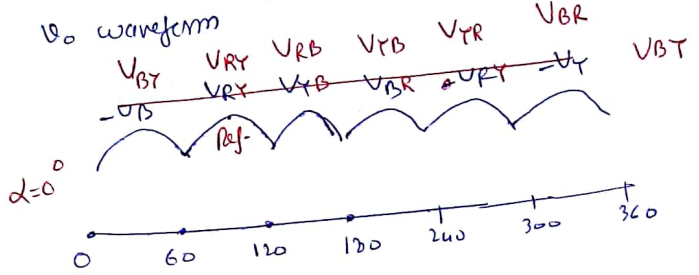

$\alpha$	L $(\frac{\pi}{3} + \alpha)$ $L = 60 + \alpha$	V $(\frac{2\pi}{3} + \alpha)$ $V = 120 + \alpha$
$\alpha = 0$	$L = 60 + 0 = 60$	$V = 120$
$\alpha = 90^\circ$	$L = 60 + 90 = 150$	$V = 120 + 90 = 210$
$\alpha = 120^\circ$	$L = 60 + 120 = 180$	$V = 120 + 120 = 240$
$\alpha = 120^\circ$	$L = 240$	$V = 360$

for  $\alpha > 60^\circ$

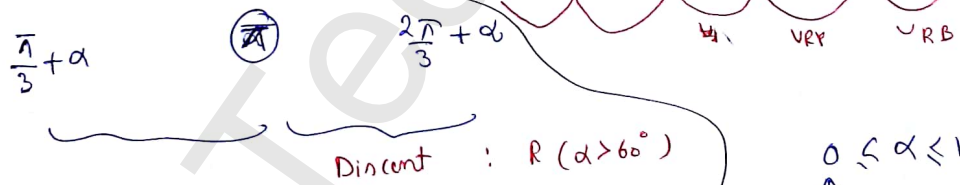

$$V_o = \frac{V_m L}{\pi/3} \left[ 1 + \cos\left(\frac{\pi}{3} + \alpha\right) \right]$$

$0 \leq \alpha \leq 120^\circ$

$$\begin{aligned} + (V_o)_{\max} &= \frac{3V_m}{\pi} \\ - (V_o)_{\max} &= -\frac{3V_m}{\pi} \end{aligned}$$

For Resistive Load  $\alpha$  (ranges btw 0 to  $120^\circ$ )

$0 \leq \alpha \leq 120^\circ \rightarrow R \text{ Load}$

$\downarrow$   $\downarrow$

$+(V_o)_{\max}$   $0V$

$\frac{3V_m}{\pi}$

$$V_o = \frac{3V_m}{\pi} \cos \alpha$$

at  $\alpha = 90^\circ, V_o = 0$

$\alpha < 90^\circ, V_o, +ve$   
 $\alpha > 90^\circ, V_o, -ve$

(PT)

AC  $\xrightarrow{P}$  DC  
(Rectification mode)

$$V_o = E_b + I R$$

used for charging of battery and dc motors.


$$\alpha > 90^\circ$$

$$V_o = I_o R + \dots \text{ (P-)}$$

$$A_c \leftarrow P \rightarrow DC \text{ (Inv)}$$


$$V_o = -E + I_o R$$

used in solar cells.

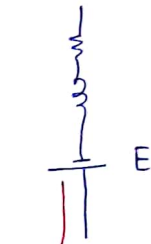

Power flow from DC to DC

For 12 pulse

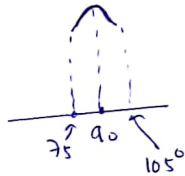

6 pulse

For Inductive Load

$$V_o = \frac{3V_m}{\pi} \cos \alpha$$

$$0 \leq \alpha \leq 180^\circ$$

max avg voltage

$$= \frac{3V_m}{\pi}$$

min avg voltage

$$= -\frac{3V_m}{\pi}$$

Here  $\alpha$  is less than  $60^\circ$

$$V_o = \frac{3V_m}{\pi} \cos \alpha$$

6 pulse

For Resistive Load

$$0 < \alpha \leq 120$$

+ (V<sub>o</sub>) max

$$\frac{3V_m}{\pi}$$

0V

if  $\alpha < 60^\circ$

if  $\alpha > 60^\circ$

$$V_o = \frac{V_m}{\sqrt{3}} \left[ 1 + \cos \left( \frac{\pi}{3} + \alpha \right) \right]$$



Sol<sup>n</sup>:- 3 pulse

R load

$$\alpha = 15^\circ \left\{ \begin{array}{ll} L & U \\ \frac{\pi}{6} + \alpha & \frac{5\pi}{6} + \alpha \\ 3\alpha + \alpha & 5\alpha + \alpha \end{array} \right.$$

$$V_{or} = \frac{V_{m\phi h}}{\sqrt{2 \cdot \frac{2\pi}{3}}} \left\{ \frac{4\pi}{6} + \frac{1}{2} \left[ \sin\left(\frac{\pi}{3} + 2\alpha\right) - \sin\left(\frac{5\pi}{3} + 2\alpha\right) \right] \right\}^{\frac{1}{2}}$$

$$= \frac{V_{m\phi}}{\sqrt{2\pi}} \left\{ \frac{4\pi}{6} + \frac{1}{2} \left[ \sin\left(\frac{\pi}{3} + 2\alpha\right) - \sin\left(\frac{5\pi}{3} + 2\alpha\right) \right] \right\}^{\frac{1}{2}}$$

$$V_{or} = V_{m\phi} \left\{ \frac{1}{6} + \frac{1}{8\pi} \sqrt{3} \cos \alpha \right\}^{\frac{1}{2}}$$

$$P = I_{or}^2 R = \frac{V_{or}^2}{R}$$

for  $\alpha = 15^\circ$

7.243 KW

$$\alpha = 60^\circ$$

$\alpha > 30^\circ$  means Upper limit  $> 120^\circ$

For resistive load

Upper limit always don't go above  $180^\circ$  i.e.  $180^\circ$

$$V_{or} = \frac{V_{mL}}{2\sqrt{\pi}} \left\{ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin \left( \frac{\pi}{3} + 2\alpha \right) \right\}^{1/2}$$

$\uparrow$   
 $\pi/3$

$$P = \frac{V_{or}^2}{R} = 4 \text{ Kw}$$

10 A

Q A 3 $\phi$  Half wave controlled rectifier is operated from a 3 $\phi$  230V, 50Hz supply with load resistance of 10 $\Omega$  an avg op voltage is 25% max possible.

op voltage @ determine the firing angle  $\alpha$

(b) determine the avg and rms value of load current

Sol<sup>n</sup> 3 pulse max<sup>m</sup> op voltage


$$V_o = \frac{3V_m}{2\pi} \cos \alpha =$$

at  $\alpha = 0$

$$V_{o\max} = \frac{3V_m}{2\pi}$$

$$0.25 \frac{3V_m}{2\pi} = \frac{3V_m}{2\pi} \cos \alpha \times 0.25$$

$$\alpha = 75.52^\circ$$

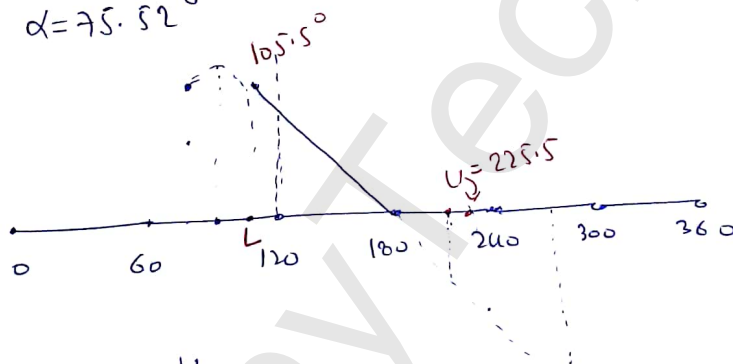

$$L \quad U$$


$$\left(\frac{\pi}{6} + \alpha\right) \quad \left(\frac{5\pi}{6} + \alpha\right)$$

$$(30 + 75.5) \quad (150 + 75.5)$$

$$105.5 \quad 225.5$$

$$V_{o\text{avg}} = \frac{3}{2\pi} \left[ \int_{105.5^\circ}^{180^\circ} V_m \sin \omega t \right]$$

By Sir.

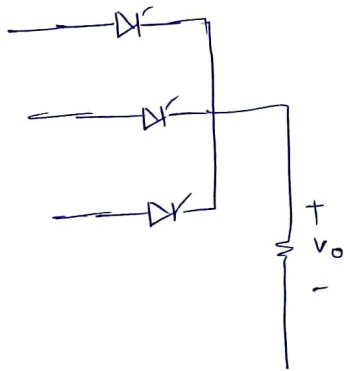

$0 \leq \alpha \leq 150$  ← R load  
 $(V)_{max}$        $0V$   
 $(\frac{\pi}{6} + \alpha)$        $(\frac{5\pi}{6} + \alpha)$       when  $\alpha \leq \frac{\pi}{6}$

when  $\alpha > \frac{\pi}{6}$

$(\frac{\pi}{6} + \alpha)$        $(\pi)$

$(\alpha \leq \frac{\pi}{6})$   
 $(\frac{\pi}{6} + \alpha)$        $(\frac{5\pi}{6} + \alpha)$   
 R load

$\alpha > \frac{\pi}{6}$ ,  $U > \pi$  · R load  $\alpha > \frac{\pi}{6}$

$(\frac{\pi}{6} + \alpha)$        $\frac{U}{\pi}$

$$V_o = \frac{3V_m}{2\pi} \cos \alpha$$

$$V_o = \frac{V_{mph}}{2\pi/\sqrt{3}} \left[ 1 + \cos \left( \frac{\pi}{6} + \alpha \right) \right]$$

I don't know  $\alpha$  so which formula to use.

to trial w/ Form left side similar

$$V_o = 25 \cdot 1 \cdot g (V_o)_{max}$$

$$V_o = \frac{1}{4} \cdot \frac{3V_m}{2\pi}$$

$$\frac{3V_m}{2\pi} \cos \alpha = \frac{1}{4} \cdot \frac{3V_m}{2\pi}$$

$\alpha = 95.5^\circ$  · if we use above

Formula then  $\alpha$  should come less than  $30^\circ$  but it came  $95.5^\circ$ .

*Don't use here (wow)*

$$V_o = \frac{3V_{mph}}{2\pi} \left[ 1 + \cos \left( \frac{\pi}{6} + \alpha \right) \right] = \frac{1}{4} \cdot \frac{3V_m}{2\pi}$$

$$1 + \cos(\pi + \alpha) = \frac{\sqrt{3}}{4}$$

$$\alpha = 94.5^\circ$$

$$I_0 = \frac{V_0}{R}$$

$$V_0 = 25\% \text{ of } (V_0)_{\max}$$

$$= \frac{1}{4} \cdot \frac{3V_m}{2\pi}$$

$$= \frac{1}{4} \cdot \frac{3 \cdot 230\sqrt{2}}{2\pi}$$

$$= 36.6 \text{ V}$$

$$V_{091} = \frac{V_{mL}}{2\pi} \left\{ \left( \frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \cdot \sin \left( \frac{\pi}{3} + 2\alpha \right) \right\}^{\frac{1}{2}}$$

$\uparrow$   
 $94.5 \times \frac{\pi}{180^\circ}$

$$I_{091} = \frac{V_{091}}{R}$$

Find the rectification  $\eta$  for the above problem


$$\text{Rectification } \eta = \frac{P_{dc}}{P_{ac}} = \frac{V_o \cdot I_o}{V_{sr} \cdot I_{sr}} \times 100$$

$$\text{TUF} = \frac{P_{dc}}{\text{kVA rating of T/F}}$$

$$= \frac{V_o \cdot I_o}{V_{sr} \cdot I_{sr}} \leftarrow \text{secondary rms voltage and current of Xmer.}$$

Q A 3 $\phi$  Half wave phase controlled rectifier is fed from a 3 $\phi$ , 400 volts 50Hz source and is connected to a load taking a constt current of 30 A SCR's are having a v-drop of 1.9 volt during their conduction calc

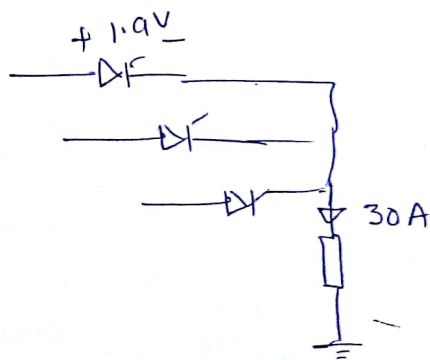- (a) Avg load voltage at Firing angle of  $\alpha = 30^\circ$  and  $\alpha = 60^\circ$
- (b) avg and rms current ratings of thyristors and as well as PIV
- (c) Power loss in each SCR
- (d) if free wheeling diode is connected across the load Find the avg value of  $V_D$  voltage, avg and rms value of free wheeling diode current for firing angles of  $30^\circ$  and  $60^\circ$ .




$$\alpha = 30^\circ$$

$$L \quad U$$

$$\left(\frac{\pi}{6} + \alpha\right) \quad \left(\frac{5\pi}{6} + \alpha\right)$$

$$(30 + 30) \quad (150 + 30)$$

$$60 \quad 180^\circ$$

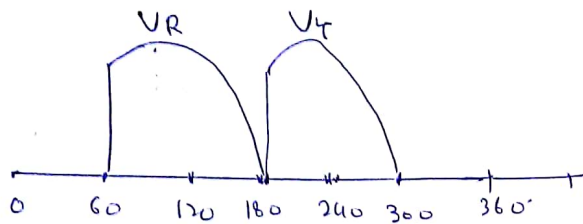

$$V_o = \frac{3V_m}{2\pi} \cos \alpha$$

$$= \frac{3 \times 400\sqrt{2}}{2\pi} \cos 30^\circ$$

By sir load current <sup>cutt & o</sup> Continious conduction.

$$\text{for } \alpha = 30^\circ$$

$$\frac{\pi}{6} + \alpha$$

$$\frac{5\pi}{6} + \alpha$$

$$V_o = \frac{3V_m}{2\pi} \cos \alpha - V_{drop}$$

this formula derived for Ideal thyristor.

$$V_o = \frac{3 \times 400\sqrt{2}}{2\pi} \cos 30^\circ - 1.9$$

$$V_o = 232 \text{ volt}$$


$$\alpha = 60^\circ \quad V_o = \frac{3 \times 400\sqrt{2}}{2\pi} \cos 60^\circ - 1.9$$

$$V_o = 133.15V$$

$$(b) (I_T)_{avg} = I_0 \left( \frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3} = \frac{30}{3} = 10A$$

$$(I_T)_{rms} = I_0 \left( \frac{2\pi/3}{2\pi} \right) = \frac{I_0}{\sqrt{3}} = \frac{30}{\sqrt{3}} = \sqrt{3} \times 10 A$$

PIV rating

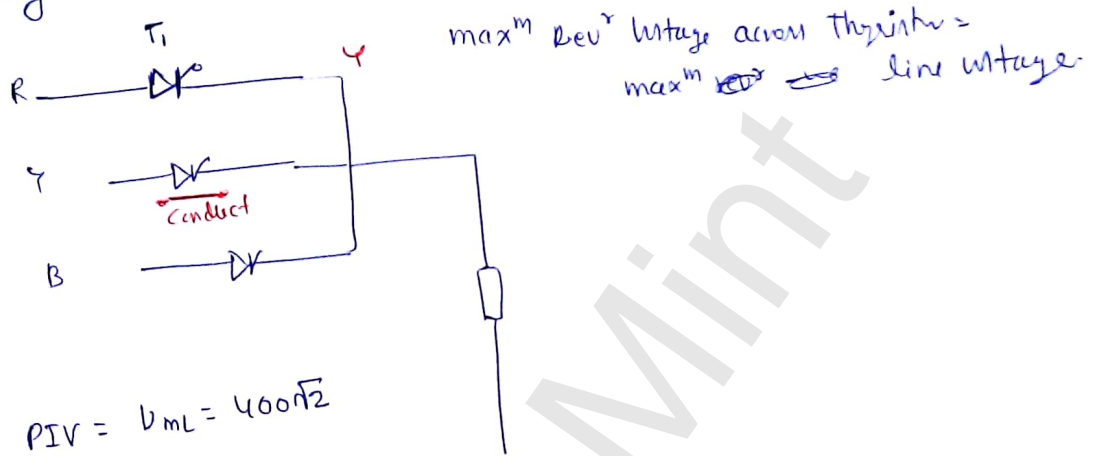

$$PIV = V_{mL} = 400\sqrt{2}$$

$$(c) \text{ Power loss in each thyristor} = (V_{drop}) (I_T)_{avg} = 1.9 \times 10 = 19 \text{ watt}$$

(d) For  $30^\circ$  No use of FWD freewheeling diode.

$$\text{So } V_0 = 232 \text{ Same as before. } (I_{FD})_{avg} = (I_{FD})_{rms} = 0.$$

$\alpha \leq 30^\circ, U \leq 180^\circ$  iFD shown effect when  $U > 180^\circ$

For  $60^\circ$   
when

$$\alpha > 30^\circ \quad U > 180^\circ$$

$$\frac{\pi}{6} + \alpha \quad \text{(T)} \quad \pi \quad \text{(FD)} \quad \frac{5\pi}{6} + \alpha$$

during freewheeling

$$V_0 = \frac{V_{mph}}{2\sqrt{3}} \left[ 1 + \cos\left(\frac{\pi}{6} + \alpha\right) \right] - V_{angf}$$

$$V_{mph} = \frac{400\sqrt{2}}{\sqrt{3}}$$


$$= 3 \cdot \frac{400\sqrt{2}}{2\pi} \left[ 1 + \cos 90^\circ \right] - 1.9$$

$$= 154 \text{ volts}$$

$$= 268 - 1.9 \text{ volt}$$



$\alpha \leq 30$  FD will not conduct.

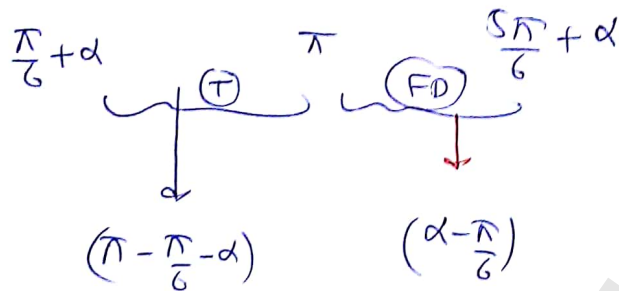

$$\frac{5\pi}{6} - \alpha$$

conduction angle of  
the thyristor

$\alpha > 30$

$$\alpha = 60 = \frac{\pi}{3}$$

$$(I_{FD})_{avg} = 30 \left[ \frac{\alpha - \frac{\pi}{6}}{2\pi/3} \right]$$


$$= 30 \left[ \frac{\frac{\pi}{3} - \frac{\pi}{6}}{2\pi/3} \right] = 30 \times \left( \frac{30}{120} \right)$$

$$= 30 \left[ \frac{\pi/3}{6\pi/3} \right]^{1/2} = \frac{30}{4} = 7.5 \text{ A}$$

$$(I_{FD})_{rms} = 30 \left[ \frac{\frac{\pi}{3} - \frac{\pi}{6}}{2\pi/3} \right]^{1/2} = 30 \left( \frac{30}{120} \right)^{1/2} = 1 \text{ SA}$$

Q A battery consisting  $R=5\Omega$   $E=150$  Volts is charging through a 3  $\phi$  Half wave phase controlled rectifier. i/p voltage to the converter is 230V (rms) from any line to neutral and firing angle for the SCR is  $30^\circ$  find the avg current flowing through the battery.

Sol<sup>n</sup> 3 pulse

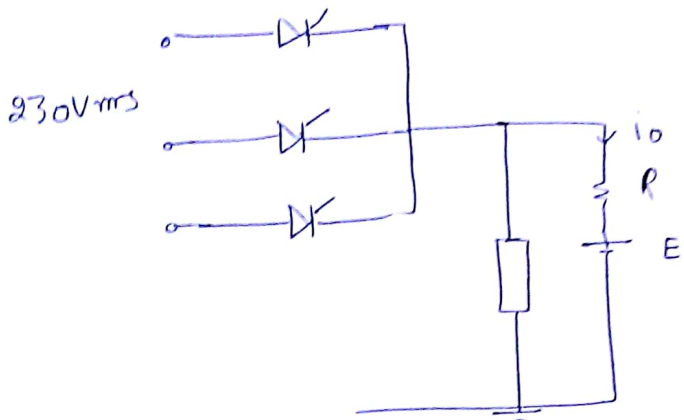


$$230 \text{ V (rms)} = V_{ph} \text{ rms}$$

$$\frac{L}{\left(\frac{\pi}{6} + \alpha\right)}$$

$$\frac{U}{\left(\frac{5\pi}{6} + \alpha\right)}$$
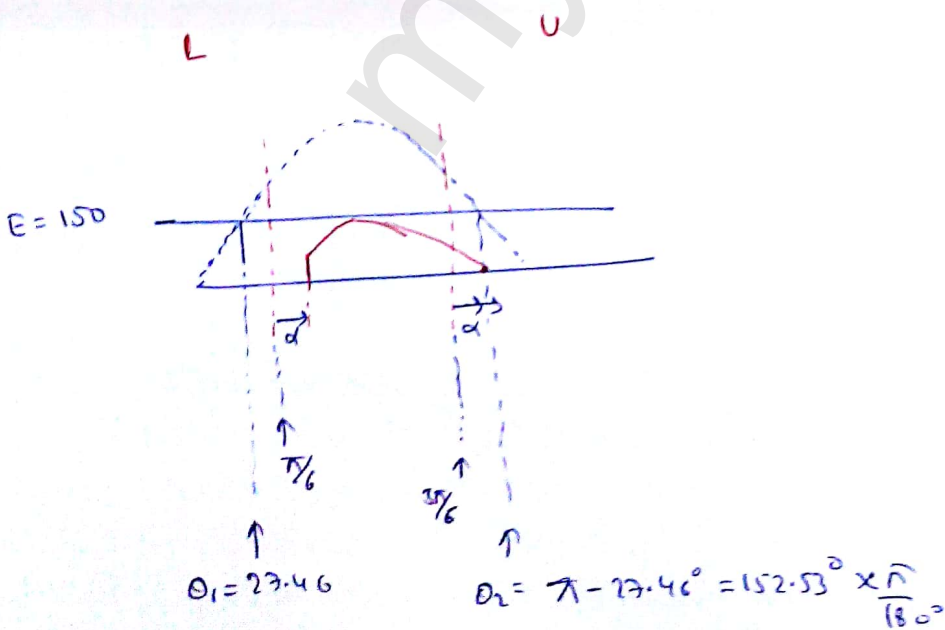
$$\alpha = \sin^{-1}\left(\frac{E}{V_m}\right) = \sin^{-1}\left(\frac{150}{230\sqrt{2}}\right) = 27.46$$



$$I_0 = \frac{1}{2\pi/3} \int_{\pi/6}^{\theta_2} \left( \frac{V_{mp} \sin \omega t - E}{R} \right) d\omega t$$

$$V_{mp} = 230\sqrt{2}$$

$$I_0 = \frac{1}{2\pi/3} \left[ \int_{60^\circ}^{152.53^\circ} \frac{230\sqrt{2}}{5} \sin \omega t - \int_{60^\circ}^{152.53^\circ} \frac{150}{5} d\omega t \right]$$

$$\frac{3}{2\pi} \left\{ \frac{230\sqrt{2}}{5} (\cos 60^\circ - \cos 152.53^\circ) - \left( \frac{150}{5} \right) \left[ (152.53 - 60) \times \frac{\pi}{180} \right] \right\}$$

$$\frac{3}{2\pi} \{ 90.24 - 48.44 \}$$

$$I_0 = 19.96 \text{ A}$$

Date 20 August

Q A 3 $\phi$  full controlled bridge conv<sup>r</sup>, 415 Vlt supply (0.04  $\Omega$  resistance/phase and .25  $\Omega$  reactance per phase) A is operating in the inversion mode at a firing advance angle of 35°. The load is RLE load with R = 0.2  $\Omega$  and inductance is large enough to make load current constt at 80 Amp. and the load emf is E volts Find the load emf E.


Sol<sup>n</sup> 6 pulse.

source resistance and reactance given consider them.

$$\alpha = 35^\circ$$


Inductive load.
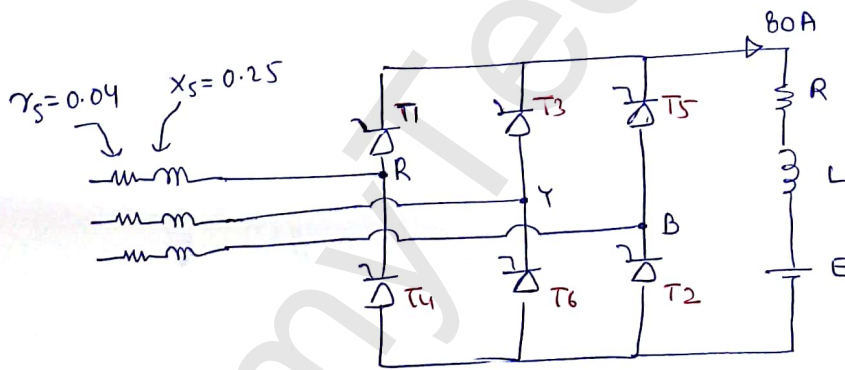
$$\left(\frac{\pi}{3} + \alpha\right) \quad \left(\frac{2\pi}{3} + \alpha\right)$$



Some time they may given source drop in thyristor. Here not given

$$V_o = \dots$$

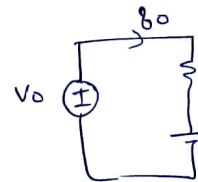

$$m = 6$$

$$\Delta V_o = 6 f L I_o$$

$$\frac{V_o - E}{R} = I_o$$

~~the formula valid~~

$$V_o = V_{do \text{ Cond}} - \Delta V_{do}$$

↙ reduction in op voltage

↓

max<sup>m</sup> avg op voltage

m	$\Delta V_{do}$
1	$fL_s I_o$
2	$4fL_s I_o$
3	$3fL_s I_o$
6	$6fL_s I_o$

← In bimbra this formula using

$$V_{do} = (V_o)_{\text{max}}$$

$$= \frac{2V_m}{\pi} \quad (m=2)$$

$$= \frac{3V_m}{2\pi} \quad (m=3)$$


$$= \frac{3V_m}{\pi} \quad (m=6)$$

$V_o = V_{do \text{ Cond}}$  ← Formula applicable when every thing is ideal.

6 pulse

$$V_o = V_{do \text{ Cond}} - \Delta V_{do} - \left\{ \begin{array}{l} \text{source} \\ \text{inductance drop} \\ \text{resistance drop} \end{array} \right\} - \left\{ \begin{array}{l} \text{drop in thyristor} \times 2 \\ \text{the avg current which is flowing in load} \end{array} \right\}$$
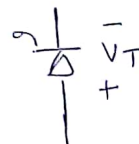
$$V_o = V_{do \text{ Cond}} - 6fL_s I_o - 2r_s I_o - 2V_T$$




$$V_o = \frac{3V_m}{\pi} \text{ Cond} - 6fL_s I_o - 2r_s I_o$$

drop of two thyristors  
 { bec at a time any two thyristor will be in conduction }.

eq<sup>n</sup> for inversion mode =

$$V_o = -E + I_o R_a$$

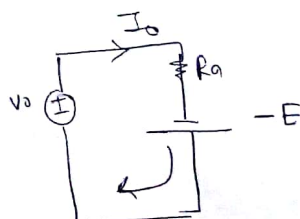

$$\alpha = 180 - \text{firing advance angle} = 180 - 35^\circ = 145^\circ$$

$$V_o = \frac{3 \times 415 \times \sqrt{2} \times \cos(145^\circ)}{\pi} - 6 \times 50 \times 10^{-3} \times 80 - 2 \times 0.04 \times 80$$

$$X_L = \omega L =$$

$$0.25 = 2\pi \times 50 \times L$$

$$L = \frac{0.25}{2\pi \times 50}$$

$$V_o = -459 - 19.09 - 6.4$$

$$V_o = -484.49$$

$$V_o = -E_b + I_o R_a$$

$$E_b = I_o R_a - V_o$$

$$E_b = 80 \times 0.2 - (-484.49)$$

$$E_b = 500.5 \text{ V}$$

Q A 3 $\phi$  full conv<sup>r</sup> is fed from a 230 V 50Hz supply having source inductance of 4mH/phase the load current 10 A & ripple free

- ① Calculate the voltage drop in the dc ap voltage due to source inductance
- ② If dc ap voltage is 210 volts find the firing angle and overlap period.
- ③ In case the bridge is made to operate as line commutated inverter with dc voltage of 210 volts find the firing angle for the same load current.

Sol<sup>n</sup>  
only source inductance given

$$\begin{aligned} \text{① Given } V_o &= V_{do} \cos \alpha - \Delta V_{do} \\ &= \frac{3 \sqrt{3} V_m \cos \alpha}{\pi} - 6 f L_s I_o \\ &= \frac{3 \times 230 \sqrt{2}}{\pi} \cos \alpha - \end{aligned}$$

$$\begin{aligned} \Delta V_{do} &= 6 f L_s I_o \\ &= 6 \times 50 \times 4 \times 10^{-3} \times 10 \\ &= 12 \text{ volt.} \end{aligned}$$

②

$$V_o = 210$$

$$V_o = V_{do} \cos \alpha - 6 f L_s I_o$$

$$210 = \frac{3\sqrt{V_m}}{\pi} \cos \alpha - 12$$

$$222 = \frac{3 \times 230 \sqrt{2}}{\pi} \cos \alpha$$

$$\alpha = 44.38^\circ$$

overlap angle

③

$$\Delta V_{do} = \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)] = 6 f L_s I_o$$

$$= \frac{3V_m}{2\pi} [\cos 44.38 - \cos(\alpha + \mu)] = 12$$

$$\cos 44.38 - \cos(\alpha + \mu) = 0.0772675$$

$$\cos(\alpha + \mu) = 0.63744$$



$$\alpha + \mu = 50.398$$

$$\mu = 50.398 - 44.38 = 6.018^\circ$$

③

we need to find  $\alpha$  in inversion mode.

load current = same = ~~80~~ A 10.

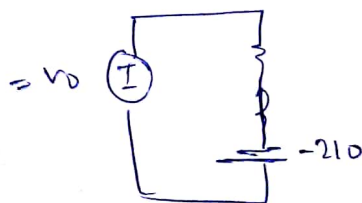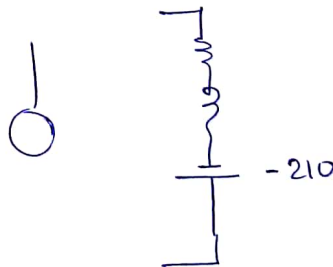

③ Inversion mode so

\* \* \*  $V_o = -210$  given.

$$-210 = V_{do} \cos \alpha - 6 \text{ f l s } 50$$

$$-210 = \frac{3V_m}{\pi} \cos \alpha - 12$$

$$-210 + 12 = \frac{3V_m}{\pi} \cos \alpha$$

$$\alpha = 129.6^\circ$$


m	$\Delta V_{do}$	same:	$\Delta V_{do} = \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$
1	LIF		
2	4 LIF	$V_{do} = \text{max}^m$	
3	3 LIF	$\frac{2V_m}{\pi}$	
4	6 LIF	$\frac{3V_m}{2\pi}$	
		$\frac{3V_m}{\pi}$	

← this formula for 2, 3, 6 pulse.

$$V_o = V_{do} \cos \alpha - \Delta V_{do}$$



① Quasi-Squarewave.

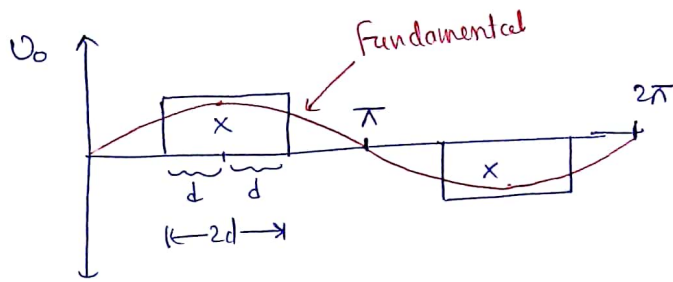

$$m = 1, 3, 5, \dots$$

[Even harmonic are removed due to half wave symmetry]

$$C_n = \frac{4X}{n\pi} \sin nd$$

$$V_o = a_0 + \sum_{n=1,3,5}^{\infty} C_n \sin(n\omega t + \phi_n)$$

$$C_1 = \frac{4X}{\pi} \sin d$$

$C_1$  can be less than or more than  $X$  depends on pulse width  
 as pulse width more  $C_1$  ↑ and more than  $X$ .  
 " " " less  $C_1$  ↓ and less than  $X$ .

$$V_o = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

↑  
DC

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \cdot \sin n\omega t dt$$

when  $x$  axis is in radian.

$$\text{Let } T = 2\pi \quad a_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \cdot \cos n\omega t \cdot d\omega t$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \cdot \sin n\omega t \cdot d\omega t$$



Harmonic present in Quasi wave. when

$$2d = \frac{2\pi}{3}$$

$$n = 6k \pm 1$$

7, 11, 13, 17, 19, ...

$$g = \frac{3}{\pi} \quad \text{THD} = 31\%$$


$$g = \text{THD} = \sqrt{\left(\frac{1}{g}\right)^2 - 1}$$

$$g = \frac{2\sqrt{2} \sin d}{\sqrt{(2d) \cdot \pi}}$$

In rectifier. generally fundamental  $f_w = 50 \text{ Hz}$  So we can be asked to find the  $f_m$  of harmonic.

In rect  $2\pi$   $f_m$  may not be  $50 \text{ Hz}$ .

③ 6 step wave form

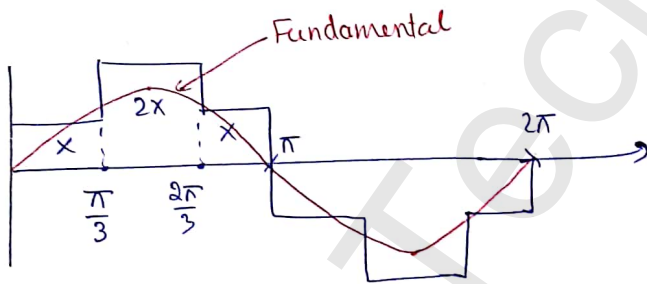

$$n = 6k \pm 1$$

$$g = \frac{3}{\pi}$$

$$\text{THD} = 31.1\%$$


$$C_n = \frac{6x}{n\pi}$$

$$C_1 = \frac{6x}{2\pi}$$

$$g = \frac{3(2x)}{\pi}$$


$$C_1 > x$$

$$C_1 < 2x$$

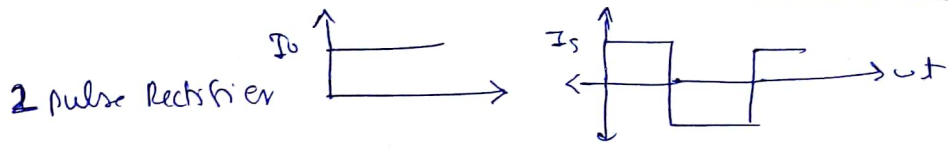

1 $\phi$  Semi cond<sup>c</sup> for  $I_s$  — Quasi Square wave


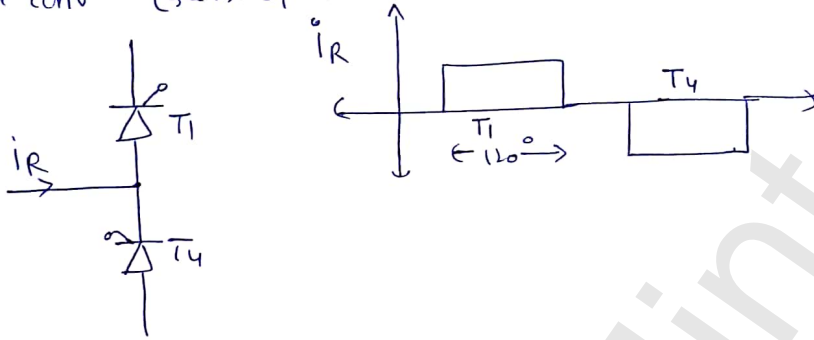
6 pulse conv<sup>r</sup> {Quasi Square wave} Source phase current



A Battery with a ~~nominal~~ nominal voltage of 200 volts and internal resistance 10 m $\Omega$  has to be charged at const current of 20 A. from a 220 volts 50 Hz ac supply. which of the following converter ckt will give better performance in terms of distortion factor in the source current and fundamental power factor. and total i/p power factor.

- a) 3 $\phi$  full conv<sup>r</sup>
- b) 3 $\phi$  semi conv<sup>r</sup> (consider  $\alpha > \pi/3$ )

Soln

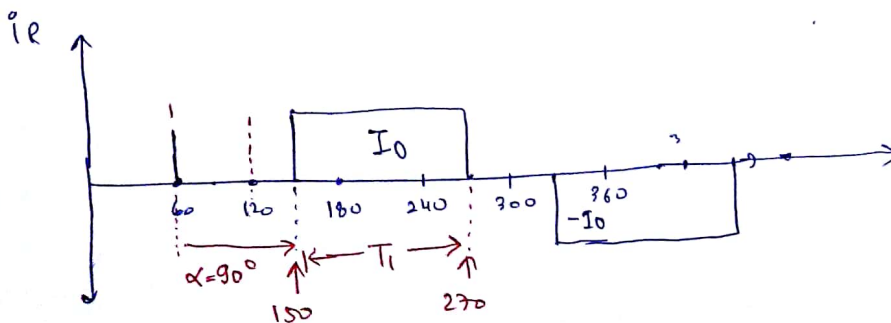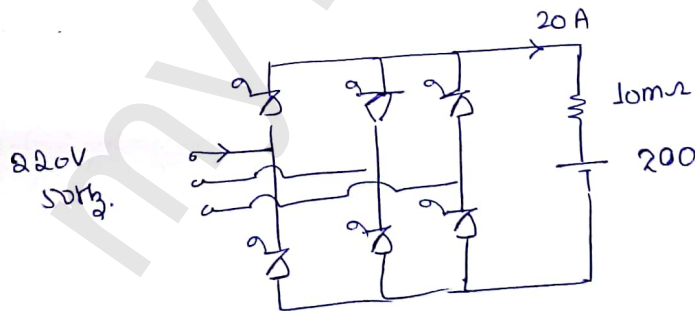

$$\alpha_1 = 90^\circ$$

$$2d = \frac{2\pi}{3}$$

$$\eta = 6k \pm 1$$

$$g = \frac{3}{\pi}$$

$$THD = 31.1\%$$

$$PF = g \cdot FDF$$

$$PF = \frac{3}{\pi} \cdot \cos \alpha$$

\*\*\*  
Active power

$$P = \sqrt{3} V_{sr} \cdot I_{s1} \cos \alpha$$

$$= V_o \cdot I_o$$

Fundamental angle

For Full Conv<sup>r</sup>: High inductive load



AC side harmonic ( $i_s$ )  $\rightarrow$  no. of pulse  $m k \pm 1$

2 pulse  $\rightarrow 2k \pm 1 = 1, 3, 5, 7, \dots$

6 pulse  $\rightarrow 6k \pm 1$

12 pulse  $\rightarrow 12k \pm 1 = 1, 11, 13, 23, \dots$

DC side harmonic for dp side waveform ( $i_o$ )  $\rightarrow m k$

$\rightarrow 2k = 2, 4, 6, \dots$

$\rightarrow 6k = 6, 12, 18, \dots$

$\rightarrow 12k = 12, 24, \dots$


In exam they can ask for of Harmonics.

ASK?

$$m = 2$$


$$DC \text{ side Harmonic} = 2k$$

2, 4, 6,

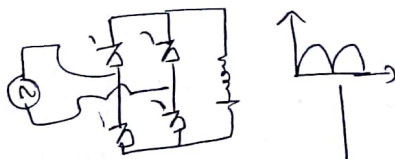


How we will know that this waveform contain 2, 4, 6 Harmonics.

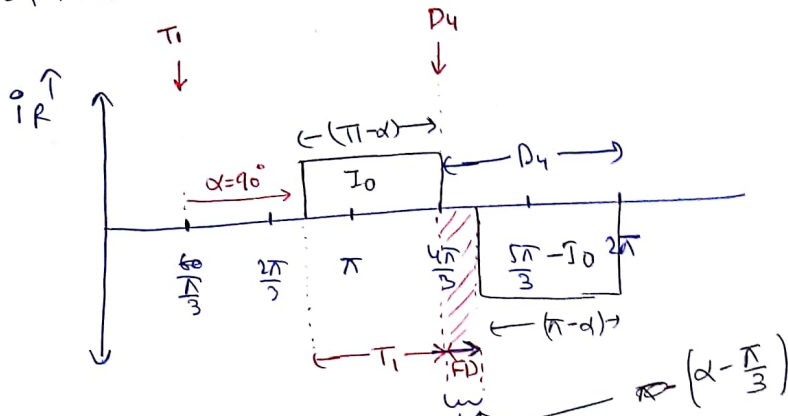(b) 3 $\phi$  Full wave semiconv (drawing waveform for  $\alpha=90^\circ$ )



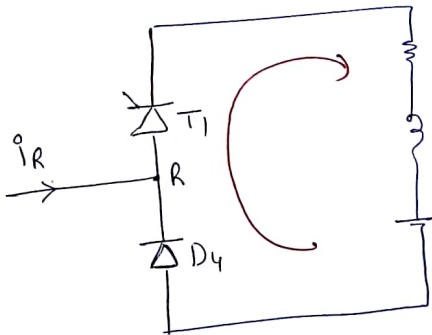For this region  $T_1$  &  $D_4$  both conducting  
so freewheeling.



this current waveform not <sup>half wave</sup> symmetric so even and odd harmonic both present.

Rms value of fundamental source current is

Rembr this  $\rightarrow$

$$I_{s1} = \frac{\sqrt{6}}{\pi} I_0 \cdot \cos \frac{\alpha}{2}$$

$$FDF = \cos \frac{\alpha}{2}$$

$$I_{s1} = I_0 \left( \frac{\pi - \alpha}{\pi} \right)^{1/2}$$

$$g = \frac{I_{s1}}{I_{s8}} = I_0 \frac{(\pi - \alpha)^{1/2}}{\pi}$$

$$g = \frac{\frac{\sqrt{6}}{\pi} I_0 \cos \frac{\alpha}{2}}{I_0 \left( \frac{\pi - \alpha}{\pi} \right)^{1/2}}$$

$$g = \sqrt{\frac{6}{\pi(\pi - \alpha)}} \cdot \cos \frac{\alpha}{2}$$

$$THD = \left( \frac{1}{g^2} - 1 \right)^{1/2}$$

$\uparrow$  Here  $g$  is more reduced bcz these harmonics are more.

$$\uparrow \text{PF} = \downarrow g \text{ FDF} \uparrow$$

FDF is  $\uparrow$ ed bec  $\cos \left( \frac{\alpha}{2} \right)$  this term is less than  $\frac{\alpha}{2}$

as  $g \downarrow$  THD  $\uparrow$


$$\uparrow \text{THD} = \left( \frac{1}{g^2} - 1 \right)^{\frac{1}{2}} \quad \text{THD} \uparrow \text{ bec } \uparrow \text{ even Harmonic also present.}$$



The supply current contains both even and odd harmonics except triplen harmonic (bec multiple of 3rd harmonic not there)

For same avg DC load current ( $I_D$ ) and firing angle  $\alpha$  3 $\phi$  semiconverter has better fundamental P.F., and power-factor (PF) but the distortion factor is lesser (i.e.  $g \downarrow$ ) when compared with the 3 $\phi$  fully controlled rectifier THD is more in 3 $\phi$  semi conv<sup>r</sup>

\* 1 $\phi$  semi conv<sup>r</sup> is better in every aspect than 1 $\phi$  full conv<sup>r</sup>.

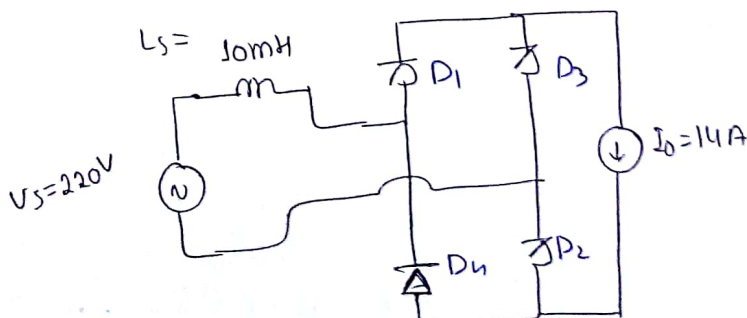Q The figure below is an uncontrolled diode bridge rectifier supplied from 220V, 50Hz 1 $\phi$  ac source the load ~~draws~~ draws a avg current of 14 A. the cond<sup>r</sup> angle of the diode  $D_1$  in degrees is.



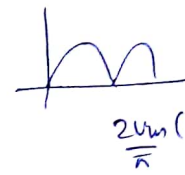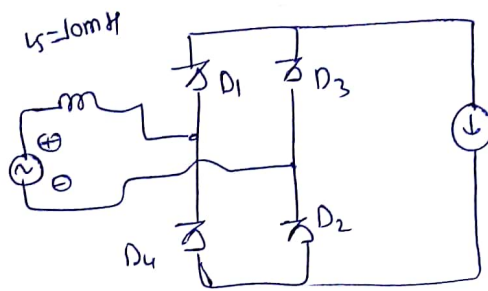

$$\text{Gen } \Delta U_{do} = \frac{U_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)] = 48 L_s I_o$$

$$= \frac{2V_m}{\pi \cdot 2} [\cos 0 - \cos \mu] = 4 \times 50 \times 10 \times 10^{-3} \times 14$$



$$\frac{V_m}{\pi} [1 - \cos \mu] = \frac{200 \times 10 \times 14}{1000} = 28$$

$$[1 - \cos \mu] = \frac{28 \times \pi}{220 \sqrt{2}}$$

$$1 - \cos \mu = 0.2827$$

$$\cos \mu = 0.71727$$

$$\mu = 44.170^\circ$$

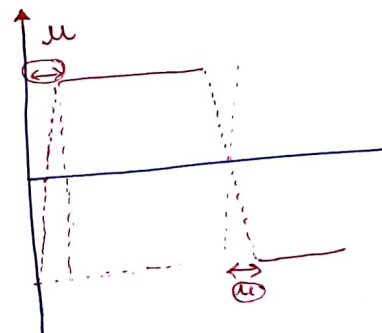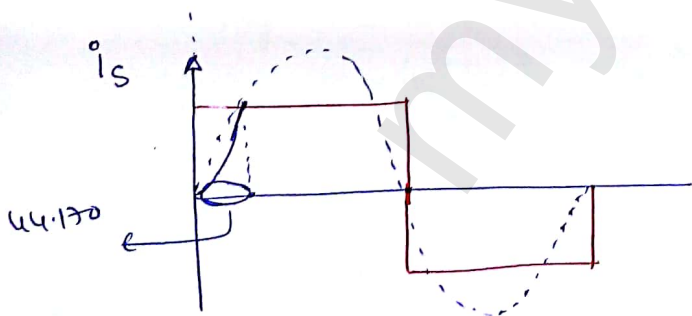



$$\text{conduction angle of diode} = 180 - 44.17$$

$$= 135.83^\circ$$



By Sir

When no source inductance.

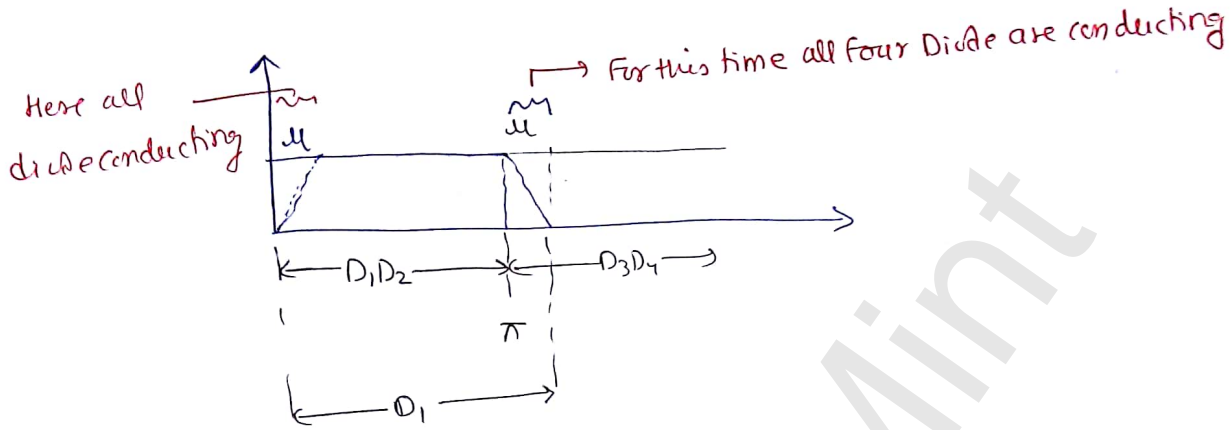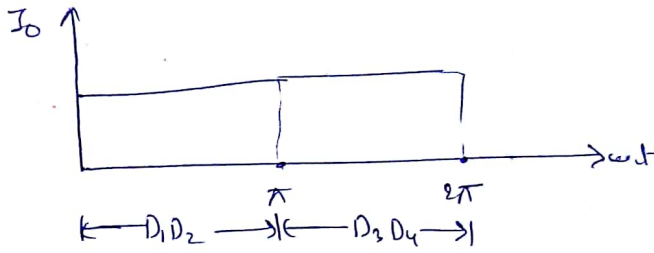

$$D_1 = 180 + \mu$$

$$D_1 \rightarrow 180 + 44.17$$

Q the ip wptage given to the conv<sup>r</sup> and used drawn are expressed as.

$$v = 300 \sin(100\pi t) + 100 \sin(300\pi t + \frac{\pi}{4})$$

$$i = 10 \sin(100\pi t - \frac{\pi}{3}) + 5 \sin(300\pi t + \frac{\pi}{4}) + 2 \sin(500\pi t - \frac{\pi}{6})$$

find the ip P.F of the converter =

$$PF = \frac{\text{active power}}{\text{Apparent power}}$$

$$PF = \frac{\frac{300}{\sqrt{2}} \cdot \frac{10}{\sqrt{2}} \cos(\frac{\pi}{3}) + \frac{100}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}} \cos(\frac{\pi}{4})}{\frac{10}{\sqrt{2}} \times \frac{300}{\sqrt{2}} + \frac{5}{\sqrt{2}} \cdot \frac{100}{\sqrt{2}}}$$

$$PF = \frac{750 + 176.77}{1500 + 250} = 0.529$$

By Sir

In voltage also harmonic are present.

$$V = 300 \sin(100\pi t)$$

$$i = \text{same as given}$$

then we can use

$$PF = g \cdot FDF$$

but here we use can't use  $PF = g \cdot FDF$


$$PF = \frac{\text{Active power}}{\text{Apparent power}} = \frac{P}{V_{sr} I_{sr}}$$

$$V_{sr} = \sqrt{\left(\frac{300}{\sqrt{2}}\right)^2 + \left(\frac{100}{\sqrt{2}}\right)^2} = 223.6067$$

$$I_{sr} = \sqrt{\left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2} = \sqrt{50 + 12.5 + 2} = 8.03$$

$$PF = \frac{926.78 \text{ W}}{223.606 \times 8.03} = 0.516$$

① Buck

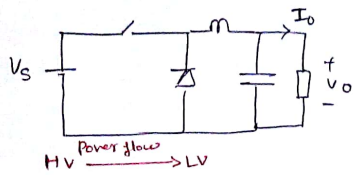

① Inductor ripple current

$$\Delta I_L = \frac{\alpha(1-\alpha)V_S}{fL}$$

→ Switch & diode block  $V_S$  (source voltage)

$$\rightarrow \frac{V_O}{V_S} = \frac{I_S}{I_O} = \alpha$$

$$\rightarrow I_{max} = (i_L)_{avg} + \frac{\Delta I_L}{2}$$

$\downarrow$   
 $I_O$

→ Ripple in op voltage ( $\Delta V_O = \Delta V_C$ )


$$\Delta V_O = \Delta V_C = \frac{\alpha(1-\alpha)V_S}{8f^2LC}$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

$$C_c =$$

Choppers

② Boost

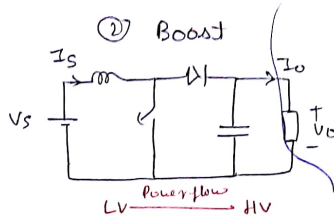

$$\Delta I_L = \frac{\alpha V_S}{fL}$$

→ Switch and diode block  $V_O$  voltage

$$\rightarrow \frac{V_O}{V_S} = \frac{I_S}{I_O} = \frac{1}{1-\alpha}$$


$$I_{max} = (i_L)_{avg} + \frac{\Delta I_L}{2}$$

$\downarrow$   
 $I_S$

$$\Delta V_O = \frac{\alpha I_O}{fC}$$

$$L_c = \frac{\alpha(1-\alpha)^2 R}{2f}$$

③ Buck Boost

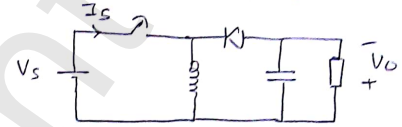

$$\Delta I_L = \frac{\alpha V_S}{fL}$$

→ Switch and diode block  $(V_S + V_O)$  voltage

$$\rightarrow \frac{V_O}{V_S} = \frac{I_S}{I_O} = \frac{\alpha}{1-\alpha}$$

$$I_{max} = (i_L)_{avg} + \frac{\Delta I_L}{2}$$

$\downarrow$   
 $(I_O + I_S)$


$$\Delta V_O = \frac{\alpha I_O}{fC}$$

$$L_c = \frac{(1-\alpha)^2 R}{2f}$$
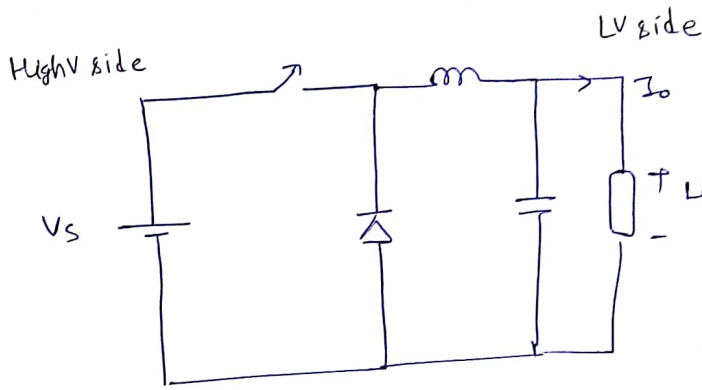
# Choppers


Buck conv<sup>r</sup> ( $V_o < V_s$ )  
 ↑  
 output < I/P supply

Power flow in Buck.  
 HV → LV  
 LV → HV in Boost.



PIV of diode =  $V_s$   
 Holding voltage of CH =  $V_s$

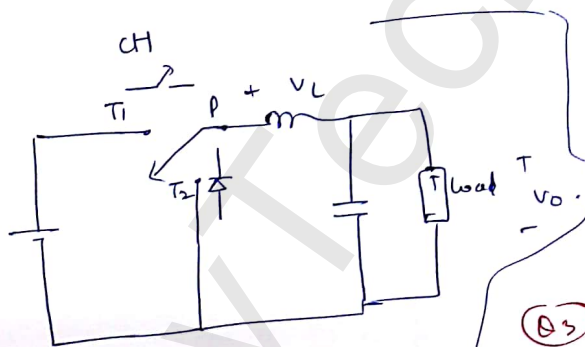Q.1 Ind<sup>c</sup> current ripple - { 1st find Indu. vltg by apply KVL (when switch on) }



Switch on [ $0 < t < T_{on}$ ]

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$


$$L \frac{di}{dt} = V_s - V_o$$

$$\Delta I_L = \frac{V_s - V_o}{L} \cdot T_{on}$$

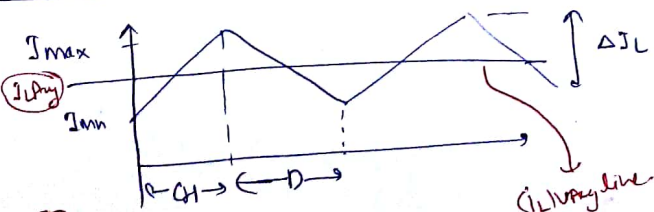Q.5  $I_L = \alpha \frac{(1-\alpha) V_s}{fL}$

Switch and diode block  $V_s$   
 • small 3 conv<sup>r</sup> current waveform same.

in Boost and BB this term not present but like this



Q.6  $Tf_{func} = \frac{V_o}{V_s} = \frac{I_s}{I_o} = \alpha$

Q.5 what max<sup>m</sup> current the diode and switch will handle

$$I_{max} = (I_L)_{avg} + \frac{\Delta I}{2}$$


$I_o \rightarrow$  (Buck)

$I_s \rightarrow$  (Boost)

$(I_s + I_o) \rightarrow$  (Buck Boost)

Q.6 if asked I<sub>min</sub> just put -ve sign

Boost

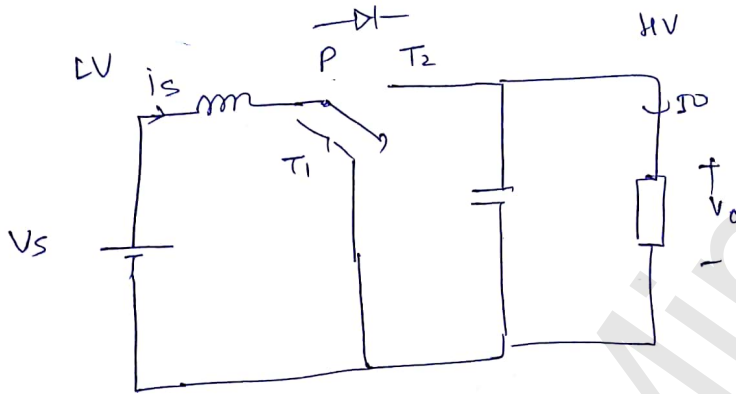

switch and diode will block load voltage  $V_o$


$$\Delta I \quad V_L = V_S$$

$$L \frac{di}{dt} = V_S$$

$$di = \frac{V_S}{L} \int_0^{T_{on}} dt = \frac{V_S}{L} T_{on}$$

$$\frac{V_o}{V_S} = \frac{I_S}{I_o} = \frac{1}{1-\alpha}$$

Buck Boost.

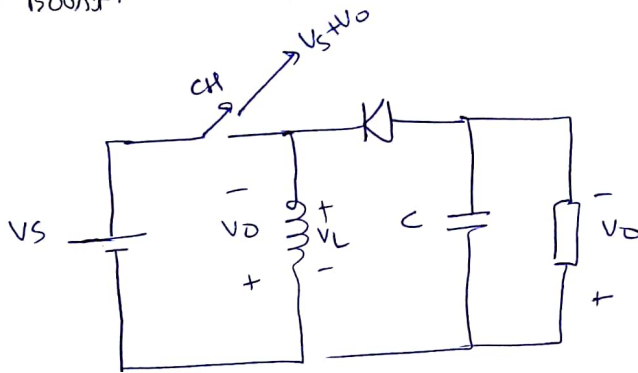

Switch & diode will block  $(V_s + V_o)$  voltage.

Purchase a switch which block  $V_s + V_o$

PIV of diode


$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{\alpha}{1-\alpha}$$

or KV

At last when we don't get any idea

put  $(V_o)_{avg} = 0$  {we may get any  $V_o$  known}.

At the boundary

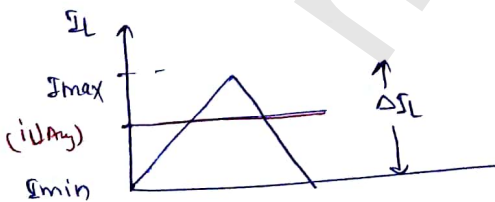

(8)

$$(i_L)_{avg} = \frac{\Delta I_L}{2} \quad \left[ \text{this relation holds only at boundary} \right]$$



$I_o$  (Buck)

$i_L$  avg is  $I_o$  for Buck

$I_s$  (Boost)

$I_s + I_o$  (Buck Boost)


$$\Delta V_o = \Delta V_c = \frac{\alpha(1-\alpha)V_s}{8f^2LC} \quad (\text{Buck})$$

Ripple in voltage

$$\Delta V_o = \frac{\alpha I_o}{fC} \quad (\text{Boost, Buck-Boost})$$

Gate 2017

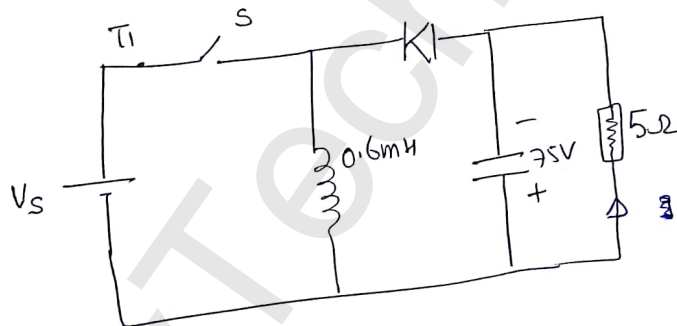In the ckt shown all elements are ideal and the switch  $S$  is operated at  $10\text{ kHz}$  and  $60\%$  duty cycle. The cap is large enough so that the ripple across it is negligible and at steady state acquires a voltage as shown in figure. Find the peak value of current drawn from the  $50\text{ V}$  dc source.




$$f = 10\text{ kHz}$$


$$D = 0.6$$

$$I_{\text{max}} = (i_L)_{\text{avg}} + \frac{\Delta I_L}{2}$$

$$(I_s + I_o) + \frac{\Delta I_L}{2}$$

$$I_o = \frac{75}{5} = 15\text{ A}$$

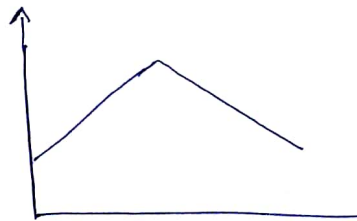

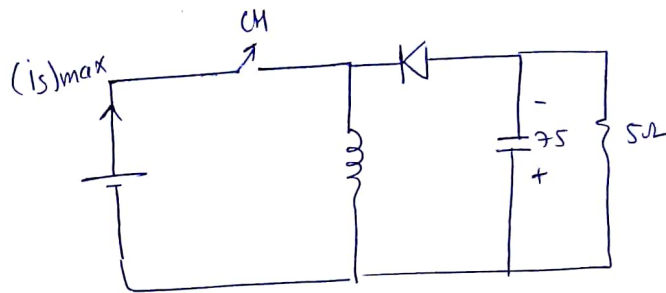

$$I_{mx} = (i_L)_{avg} + \frac{\Delta I_L}{2}$$

$$= (I_s + I_o) + \frac{\Delta I_L}{2}$$

$$I_o = \frac{75}{5} = 15A$$

$$I_s = \frac{\alpha I_o}{(1-\alpha)}$$

$$I_s = \frac{0.6 \times 15}{1-0.4} = \frac{6 \times 15}{4} = \frac{90}{4} = 22.5A$$


$$\Delta I_L = \text{for Buckboost} = \frac{\alpha V_s}{fL} = 5A$$

$$= (22.5 + 15) + \frac{5}{2}$$

$$= 37.5 + 2.5$$



$$(\Delta I_L)_{mx} = 40A$$

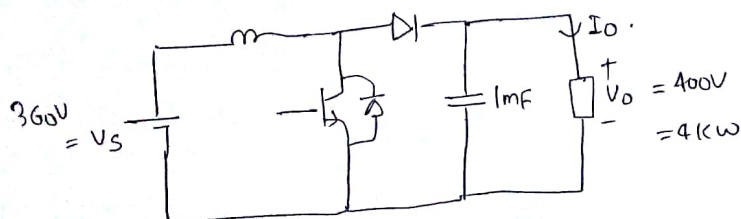Q A DC-DC Boost converter as shown in the figure below is used to boost 360V to 400V. at a power of 4KW. all devices are ideal. Considering continuous inductor current the rms value of current in the switch is \_\_\_\_.





# SM Boost Chopper

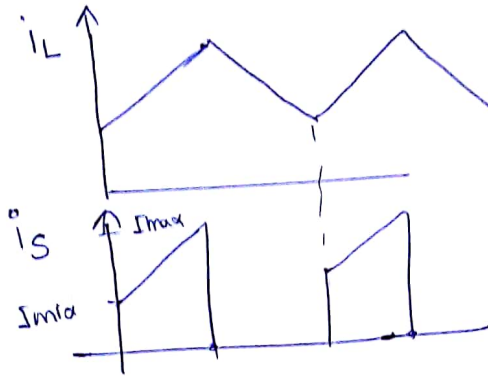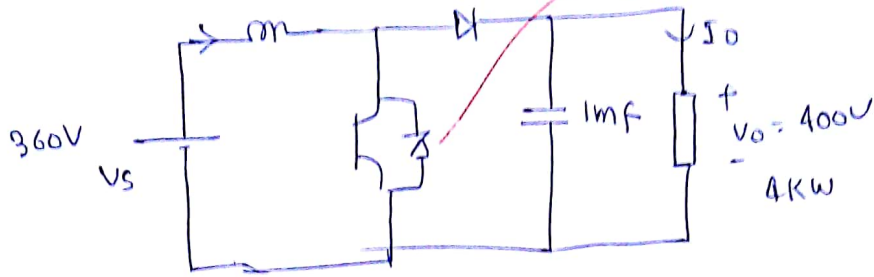

$$\frac{V_0}{V_s} = \frac{\alpha}{1-\alpha}$$

$$V_0 = \frac{V_s}{1-\alpha}$$

$$1-\alpha = \frac{360}{400}$$


$$\frac{(I_{max} + I_{min})}{2}$$

$$1 - \frac{360}{400}$$

$$1 - 0.9 = \alpha$$

$$\alpha = 0.1$$

$$I_0 = \frac{4000}{400} = 10A$$

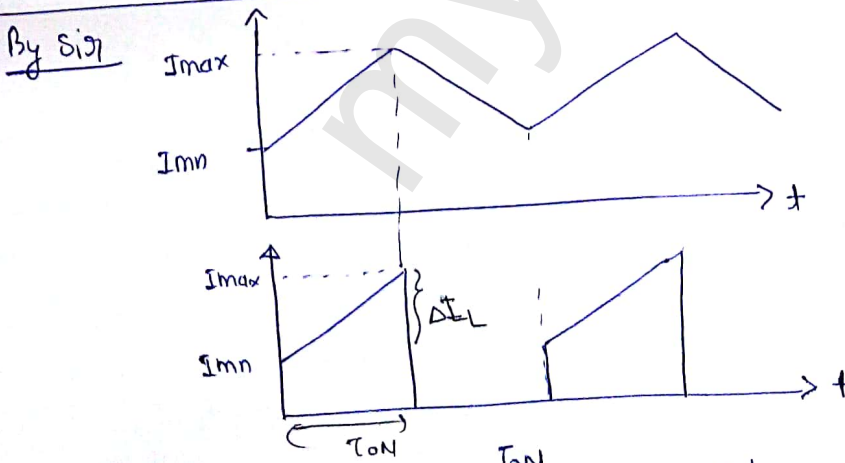

$$I_{sw\ RMS} = \left\{ \frac{1}{T} \int_0^{Ton} (i_{sw})^2 \cdot dt \right\}^{1/2}$$

$$m = \frac{di}{dt} = \frac{\Delta I_L}{T_{on}}$$

$$i_{sw} = mt + I_{mn}$$


$$\Delta I_L \text{ for Boost} = \frac{\alpha V_s}{fL}$$

↑  
 $f_{m^c}$  not given cant find  $\Delta I_L$

$f_{m^c}$  is not given choppers work for high  $f_{m^c}$  assume very high  $f_{m^c}$

$$\Delta I_L = \frac{\alpha V_s}{fL} \approx 0 \quad \text{] negligible}$$

i.e.  $i_s = i_L \uparrow$

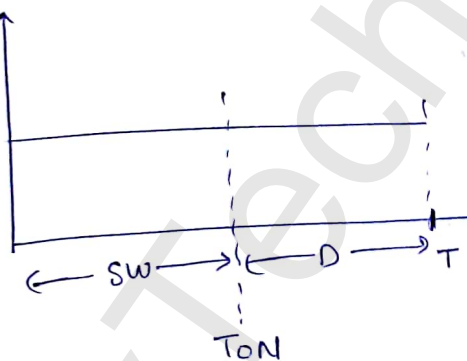

$$\begin{aligned} I_{sw} &= I_s \left( \frac{T_{on}}{T} \right)^{1/2} \\ &= \sqrt{\alpha} \cdot I_s \\ &= \sqrt{0.1} \times 11.1 \\ &= 3.5 \text{ A} \end{aligned}$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{1}{1-\alpha}$$

$$I_s = \frac{I_o}{1-\alpha}$$

$$I_s = 11.1 \text{ A}$$

\* whenever asked rms draw waveform and if  $f_{m^c}$  not given neglect ripple i.e.  $f_{m^c}$  very high.

Q The ip voltage to a boost converter is 8 volts the required avg op voltage is 16 volts and the avg load current is 0.5 amp. the switching fm<sup>c</sup> of the converter is 30kHz if L = 160 μH the value of C = 380 μF Calc


- (a) Peak to peak ripple in the inductor current
- (b) Peak value of current in the switch
- (c) Rms value of current in the switch
- (d) Ripple in the cap<sup>c</sup> voltage

Sol<sup>n</sup> .  $V_s = 8$      $V_o = 16$      $I_o = 0.5$      $f = 30\text{kHz}$      $L = 160\mu\text{H}$   
 $C = 380\mu\text{F}$

$$V_o = \frac{V_s}{1-\alpha}$$

$$16 = \frac{8}{1-\alpha}$$

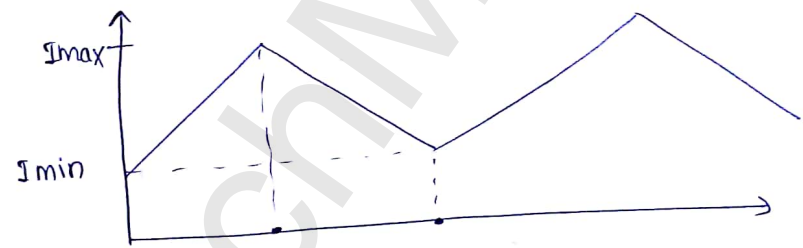
$$1-\alpha = \frac{8}{16} = \frac{1}{2}$$



$$1-\alpha = 0.5$$

$$\alpha = 0.5 = \frac{T_{on}}{T}$$

$$T_{on} = \frac{0.5 \times 1000}{30}$$

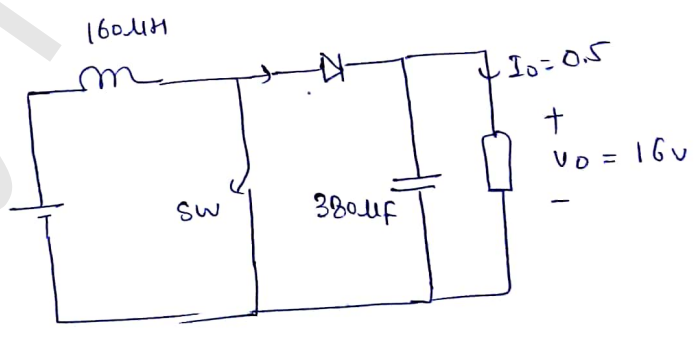

$$\Delta I_L = \frac{\alpha V_s}{fL} = \frac{0.5 \times 8 \times 10^6}{30 \times 10^3 \times 160}$$

$$\Delta I_L = 0.833\text{A}$$

here ripple current is more than avg load current

$$i_{max} = (i_L)_{avg} + \frac{\Delta I_L}{2}$$



$$= I_s + \frac{0.833}{2}$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{1}{1-\alpha}$$

$$I_s = \frac{0.5}{1-0.5} = 1 \text{ amp}$$

$$I_{max} = 1 + \frac{0.933}{2} = 1.416 \text{ A}$$

③ rms current in switch

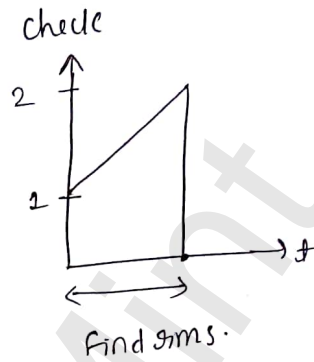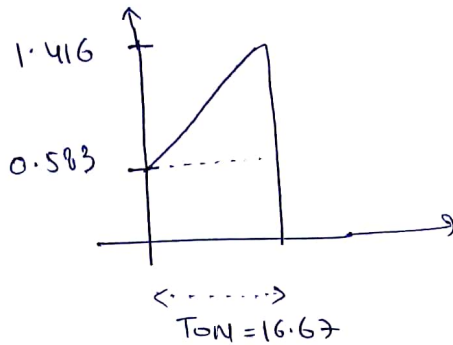

$$\text{slope} = \frac{0.833}{(T/f)} = 49980$$

$$I_{sw rms} = \left\{ \frac{1}{T} \int_0^{T_{ON}} (49980t + 0.583)^2 dt \right\}^{1/2}$$


$$I_{sw rms} = 0.727 \text{ A}$$

approximation  
 $I_{sw rms} = \sqrt{\alpha} \cdot I_s$

$$\sqrt{0.5} \times 1$$

$$= 0.717 \text{ A}$$

$$0.727 \approx 0.717$$

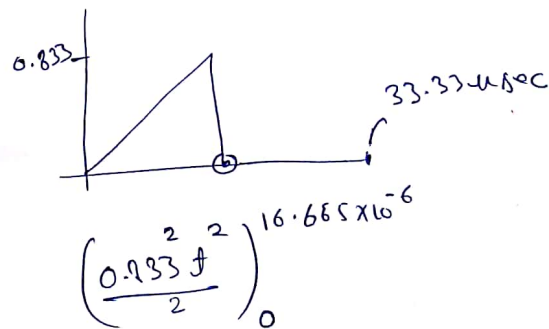


$$\frac{1}{2} \left\{ \frac{(0.833)^2}{2} (16.65) \times 10^{-12} \right\} + \left\{ (0.583)^2 \times (16.65)^2 \times 10^{-12} \right\}$$

$$\frac{\hspace{10em}}{33.33 \times 10^{-6}}$$

Q the ip voltage to a buck-board conv<sup>r</sup> is 10V the switch is operating with a duty ratio of  $\alpha = 0.3$  and switching  $f_m$  of 25 kHz the filter inductance is 150  $\mu$ H and the filter cap<sup>c</sup> is 220  $\mu$ F. avg load current is 1.2 amperes determine

- ① peak to peak ripple in the output voltage
- ② " " " " " " inductor current.
- ③ the peak and avg current of the switch.

Sol<sup>n</sup>

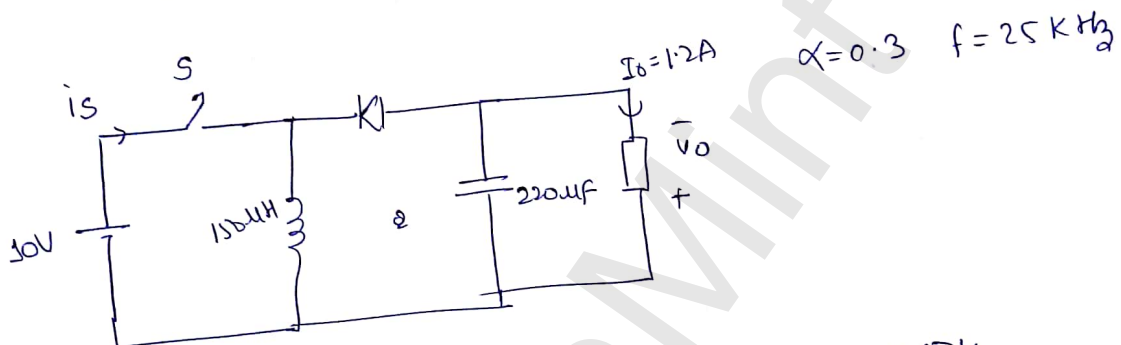

$$\Delta V_o = \frac{\alpha I_o}{fC} = \frac{0.3 \times 1.2}{25 \times 10^3 \times 220 \times 10^{-6}} = 0.0654 = 65.4 \text{ mV}$$

$$\Delta I_L = \frac{\alpha V_s}{fL} = \frac{0.3 \times 10}{25 \times 10^3 \times 150 \times 10^{-6}} = 0.8 \text{ Amp.}$$

Peak value of switch cur.

$$I_{\text{max}} = I_s + \frac{\Delta I_L}{2}$$

$$= (I_s + I_o) + \frac{\Delta I_L}{2}$$

$$= (0.514 + 1.2) + \frac{0.8}{2}$$

$$= 1.714 + 0.4$$

$$= 2.114 \text{ A}$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{\alpha}{1-\alpha}$$

$$I_s = \frac{0.3 \times 1.2}{1-0.3}$$

$$I_s = 0.514$$


avg value of switch current = value of supply current

$$I_{\text{avg}} = 0.514$$

Till now we used non-isolated Buck conv<sup>r</sup>  $\rightarrow$  Non Isolated DC  $\rightarrow$  DC  
 In smps we use isolate buck conv<sup>r</sup>

$$V_o = \alpha V_s \text{ (for non isolate)}$$

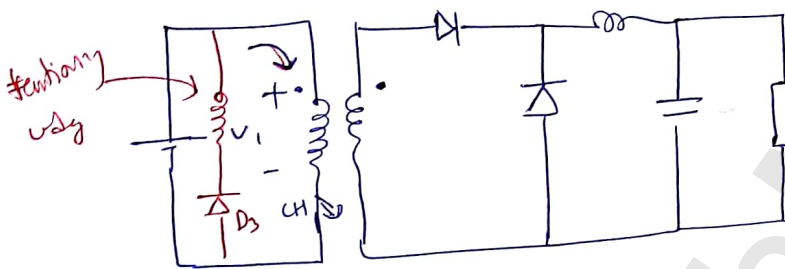
Isolated Buck conv<sup>r</sup> = Forward conv<sup>r</sup>



$$\alpha = \frac{N_2}{N_1}$$

$V_o = \alpha \cdot \alpha V_s$   $\rightarrow$  isolate  
 [as  $i$  on the switch  $X$ mer draws magnifying current]

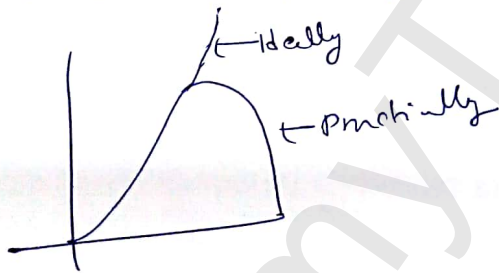In old buck problem that differ b/w VP and OP less & less  
 we can't get high OP voltage




In Buck we reduce OP voltage i.e.  $\uparrow I_o$

$$\downarrow V_o \uparrow I_o = \rightarrow V_s \cdot I_s$$


So voltage Buck converter = current Boost conv<sup>r</sup>

Q A battery with a terminal voltage of 200V is supplied with ~~an~~ power to a type A chopper the o/p voltage of the chopper consist of rectangular pulses of 2ms duration in overall cycle time of 5ms internal resistance of battery is negligible. calc

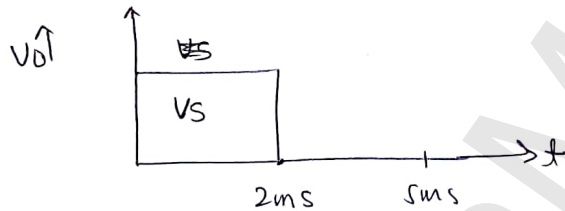- (a) Ripple factor
- (b) Avg and rms value of o/p voltage
- (c) Rms value of fundamental component of o/p voltage
- (d) Ac ripple voltage



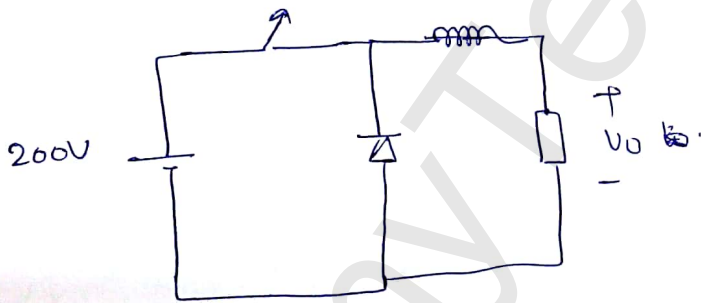Sol<sup>n</sup> the waveform tells that the chopper is without filter.



$$\alpha = \frac{T_{ON}}{T} = \frac{2}{5} = 0.4$$

$$V_{\text{ripple}} = \sqrt{(FF)^2 - 1}$$

$$FF = \frac{V_{or}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s} = \frac{1}{\sqrt{\alpha}}$$

$$\text{URF (V-ripple)} = \sqrt{\frac{1}{\alpha} - 1}$$

$$= \sqrt{\frac{1}{0.4} - 1}$$

$$\text{URF} = 1.224$$

$$\textcircled{b} \quad V_o = \alpha V_s = 0.4 \times 200 = 80$$

$$V_{om} = \sqrt{\alpha} V_s = 126.49$$

$$\textcircled{c} \quad V_o = \underbrace{\alpha V_s}_{\text{DC}} + \underbrace{\sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin n\pi\alpha \cdot \sin(n\omega t + \phi_n)}_{\text{AC}}$$

$$\phi_n = \tan^{-1} \left[ \frac{\cos n\pi\alpha}{\sin n\pi\alpha} \right]$$

$$V_{on} = \frac{2V_s \sin n\pi\alpha}{n\pi} \cdot \sin(n\omega t + \phi_n)$$

$$\text{rms value of } n^{\text{th}} \text{ harmonic} = \frac{1}{\sqrt{2}} \frac{2V_s \sin n\pi\alpha}{n\pi}$$

$$\text{Fundamental RMS} = \frac{\sqrt{2} V_s \sin \pi\alpha}{\pi} = \frac{\sqrt{2} \times 200 \times 0.951}{\pi} = 85.6 \text{ V}$$

$$\textcircled{d} \quad V_{or}^2 = V_o^2 + V_{ac}^2$$

$$V_{ac}^2 = V_{o1}^2 + V_{o2}^2 + V_{o3}^2 + \dots$$

$$V_{ac} = \sqrt{V_{or}^2 - V_o^2}$$


$$V_{ac} = \sqrt{(126.49)^2 - (80)^2} = 97.98 \text{ V}$$




Q An Ideal chopper at  $500\text{Hz}$  feeds an RL load having load resistance  $R=30\Omega$  and load inductance  $L=9\text{mH}$  from a  $48\text{V}$  battery. The load is shunted by a ~~Free~~ Diode. battery is low level assuming duty cycle of the chopper is to be  $50\%$ . find.

- (a) Peak value of load current.
- (b) min<sup>m</sup> value of load current
- (c) Avg load current, avg load voltage
- (d) Avg load wtage
- (e) Current excursion  $\Delta I$  in the load current or Ripple

Soln.

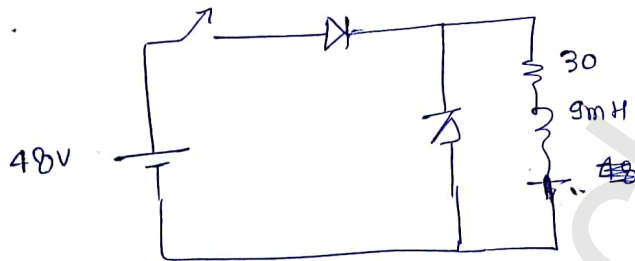

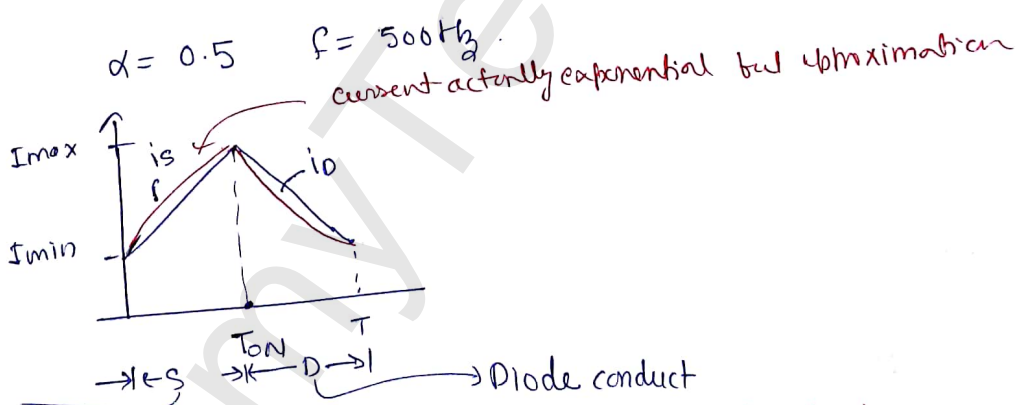
load is shunted across free wheel diode means LC filter is not there.




$$I_{max} = (\Delta I)_{avg} + \frac{\Delta I}{2} \quad \leftarrow \text{i can't apply this formula here}$$

$$I_{max} = \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} \right] - \frac{E_b}{R_a}$$

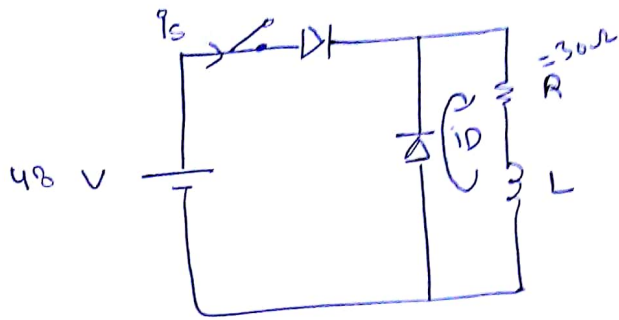$\leftarrow$  this formula was derived for RLE load and we have to use formula for RL load, we can't put  $E_b=0$  in above eqn to


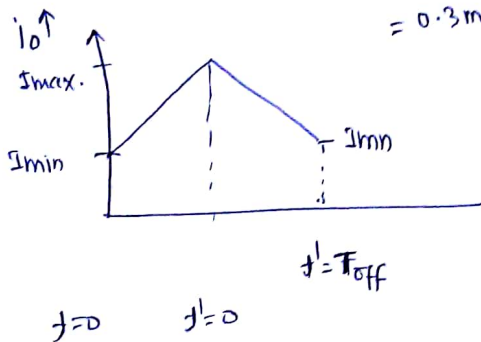
$$\tau = \frac{L}{R} = \frac{9 \times 10^{-3}}{30} = 0.3 \times 10^{-3} = 0.3 \text{ msec}$$



$$i_s = \frac{V}{R} (1 - e^{-t/\tau}) + I_{mn} e^{-t/\tau}$$

$$i_s = \frac{48}{30} (1 - e^{-t/0.3}) + I_{mn} e^{-t/0.3}$$

$$I_{mx} = \frac{48}{30} (1 - e^{-T_{on}/0.3}) + I_{mn} e^{-T_{on}/0.3}$$

$$i_D = I_{mx} \cdot e^{-t/\tau}$$

$$I_{mn} = I_{mx} \cdot e^{-T_{off}/0.3}$$

$$I_{mx} = \frac{48}{30} (1 - e^{-T_{on}/0.3}) + I_{mx} e^{-T_{off}/0.3} \cdot e^{-T_{on}/0.3}$$

$$I_{mx} = \frac{\frac{48}{30} (1 - e^{-T_{on}/0.3})}{1 - e^{-T_{off}/0.3}} = \frac{1.6 (1 - e^{-1.5429})}{0.998} \approx 1.544 \text{ A}$$

$$T_{on} = \frac{\alpha}{f} = \frac{0.5}{500} = 1 \times 10^{-3} \quad I_{mx} = 1.54 \text{ A}$$


$$I_{mn} = I_{mx} e^{-T_{off}/0.3} = 1.54 \times e^{-\frac{1 \times 10^{-3}}{0.3}} = 0.0549 \text{ A}$$

RL :

$$I_{mx} = \frac{V_s}{R} \left[ \frac{1 - e^{-T_{on}/\tau_0}}{1 - e^{-T/\tau_0}} \right]$$

← eq<sup>n</sup> for RL load.

$$I_{mn} = I_{mx} e^{-T_{off}/\tau_0}$$

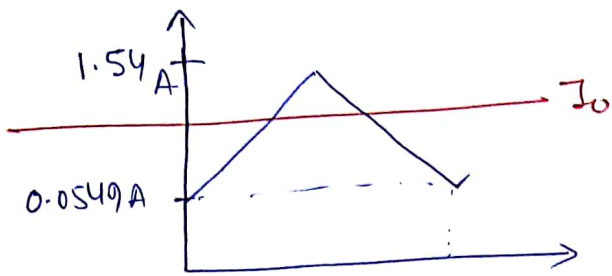

$$I_0 = \frac{0.0549 \times T + \frac{1}{2} \times T \times (1.54 - 0.0549)}{T}$$

$$I_0 = 0.0549 + 0.74255$$

$$I_0 = 0.79745 \text{ A}$$

$$V_0 = I_0 R$$

$$V_0 = 0.79745 \times 30$$

$$= 23.9235 \text{ V}$$

$$V_0 = \alpha V_s$$

$$= 0.5 \times 48 = 24$$


Current ripple  $\Delta I_L = 1.54 - 0.0549$

$$= 1.4851 \text{ A}$$

Till Now we have used non-isolated Buck converter means dc voltage source is directly connected to chopper.


Disadvantage of this is that we can't get a large difference b/w i/p voltage  $V_s$  and o/p voltage  $V_o$

because practically as we ↑  $\alpha$

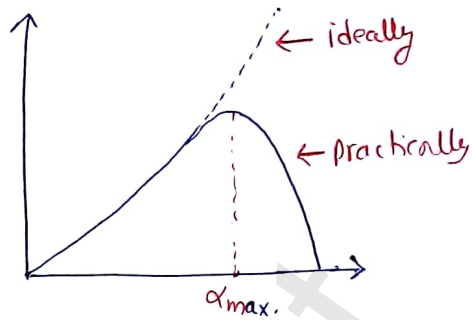

So we started concept of Isolated Buck conv<sup>r</sup> or Forward converter.

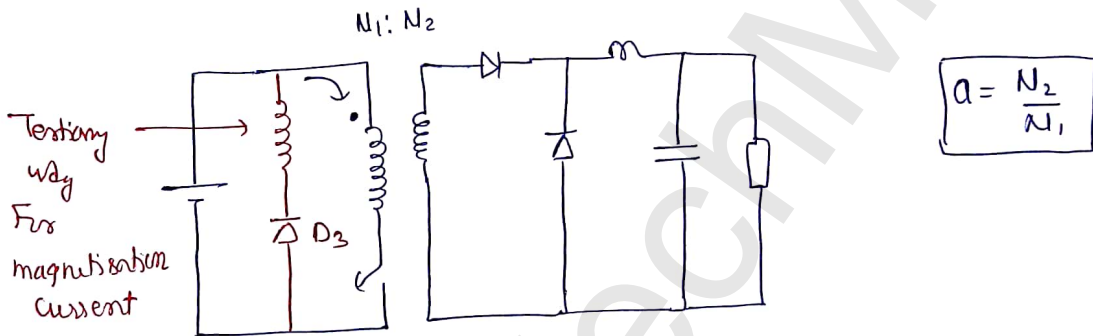→ Isolated Buck conv<sup>r</sup> are used in SMPS.



$$a = \frac{N_2}{N_1}$$

For Non Isolated conv<sup>r</sup>

$$V_o = \alpha V_s$$


For Isolated Buck conv<sup>r</sup>

$$V_o = a \cdot \alpha \cdot V_s$$

in Buck conv<sup>r</sup> we reduce o/p voltage i.e. ↑  $I_o$


$$\downarrow V_o \uparrow I_o = V_s I_s$$

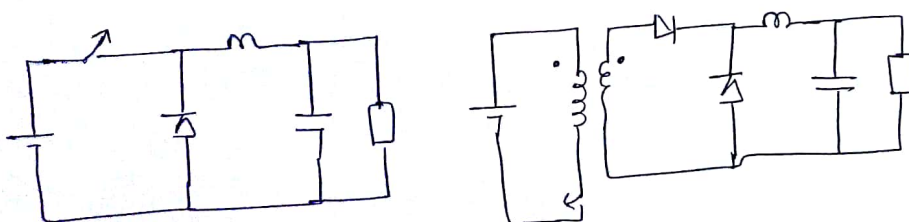Voltage buck conv<sup>r</sup> = Current Boost conv<sup>r</sup>



# Inverters.

## 1 $\phi$ Half bridge

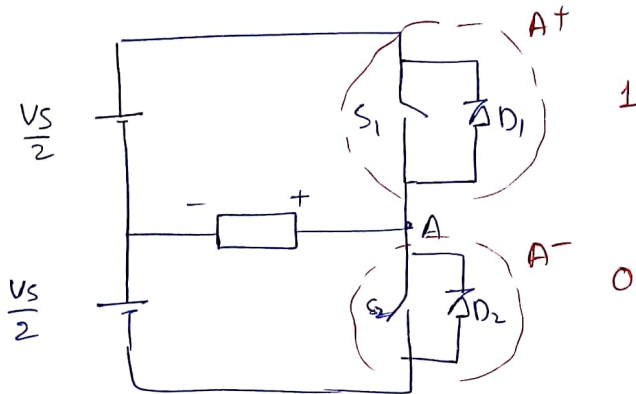


Switch allow the power  
Diode " fre power -


$V_{AO} \rightarrow$  pole vltz of A

$A^+ (S_1 \text{ or } D_1)$

$A^- (S_2 \text{ or } D_2)$

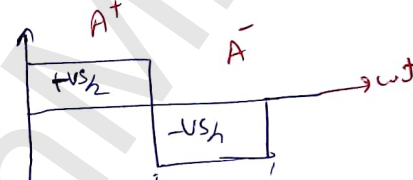

whatever load vltz waveform fixed

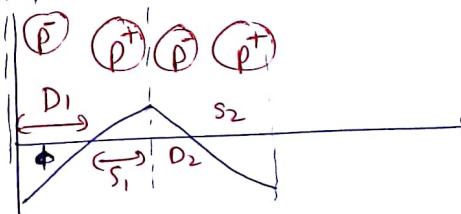


Diode angle = impedance angle





$V_{SI} \rightarrow V_o$  (vltz waveform fixed)  
as load changes circuit waveform changes

GSF  $\rightarrow$  opposite.

# Inverter

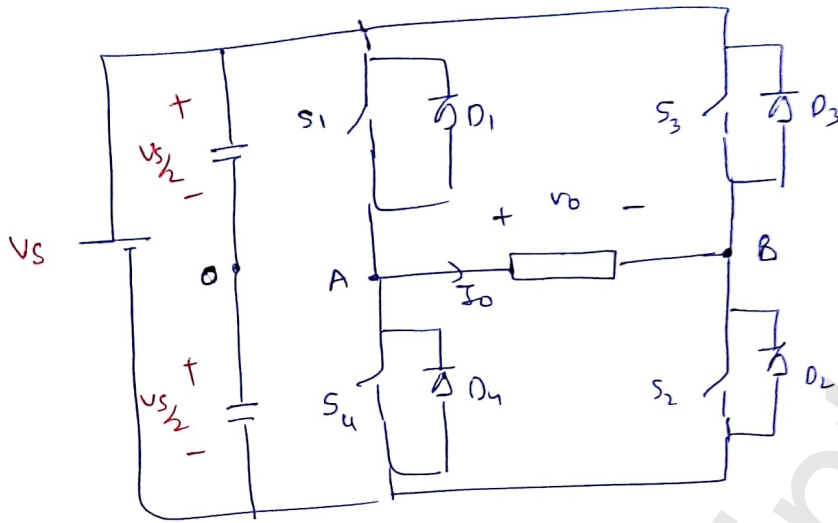



(10)

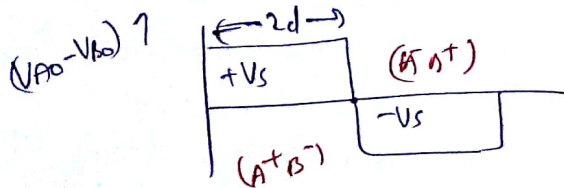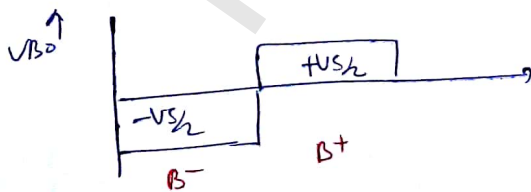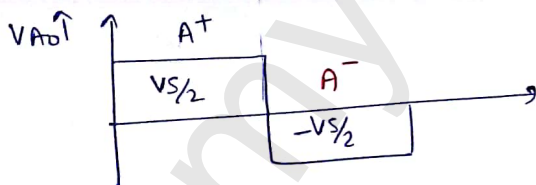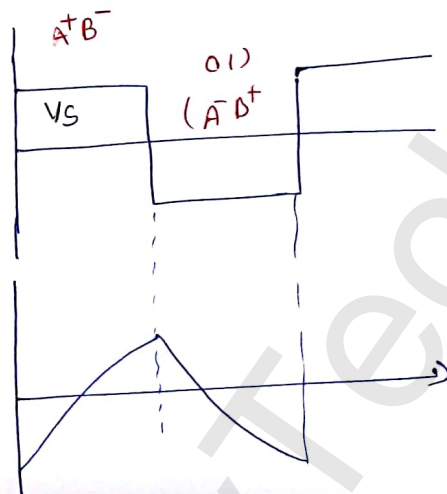




$$V_{or} = V_s \left( \frac{2d}{\pi} \right)^{1/2}$$


$\pi$   
 $\uparrow$   
 $2d$   
 $\uparrow$   
 pulse width =  $2d = \pi$

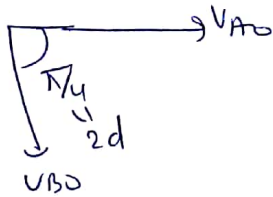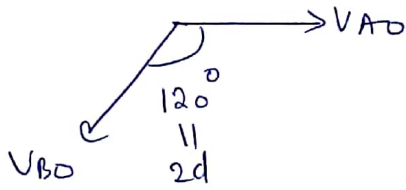By varying phase angle difference  $\theta$  w.r.t.  $\omega t$  A and  $\omega t$  B we can change pulse widths and by changing pulse width  $\omega$  can change  $V_{rms}$




3  $\phi$  VSI

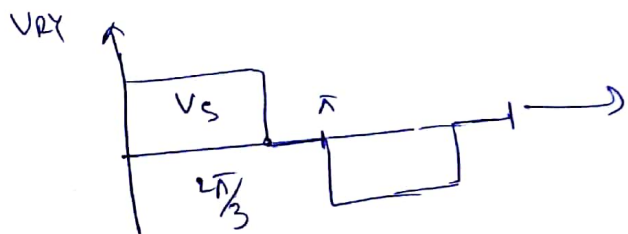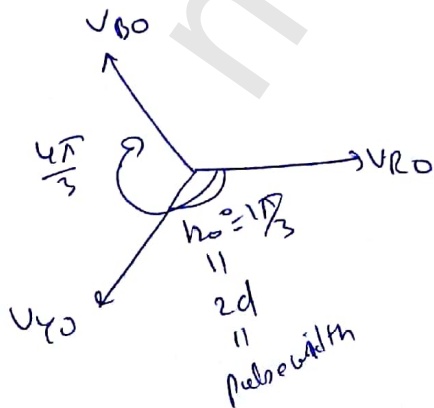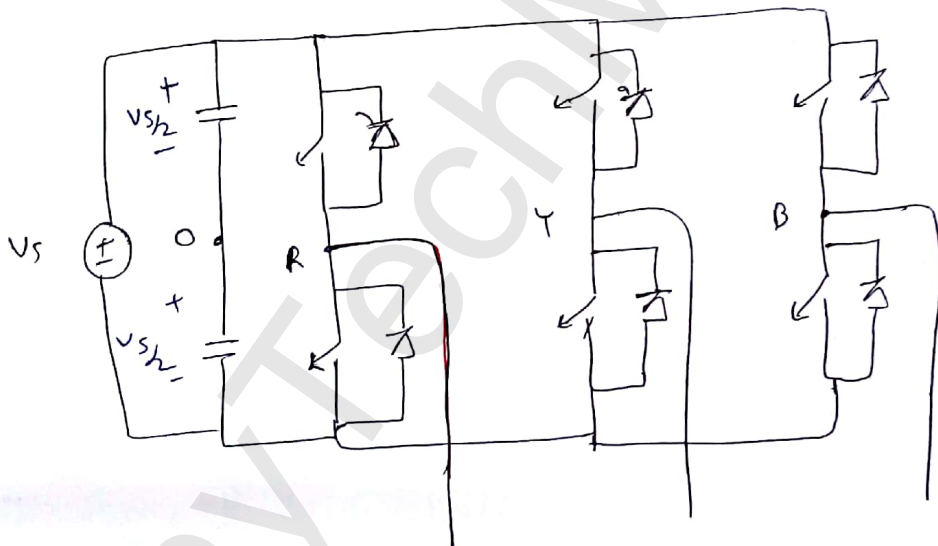

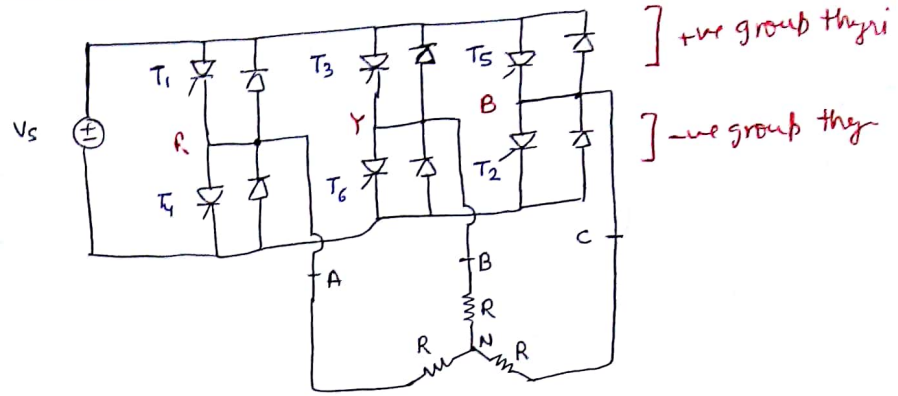

180° cond<sup>c</sup> mode

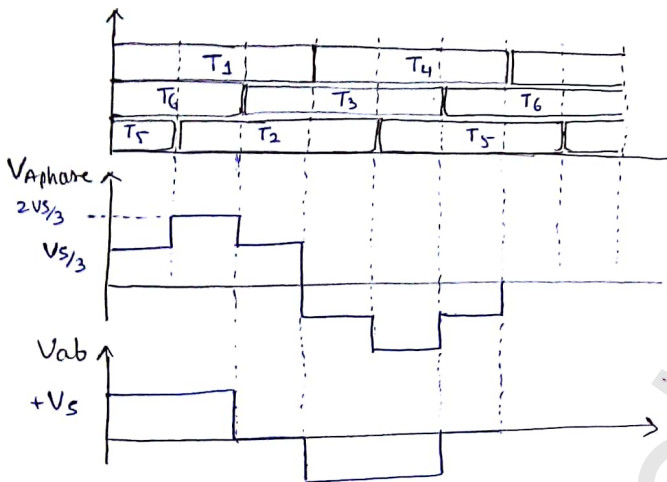

Each thyristor conduct for 180°  
at a time 3 thyristor conduct


$$V_{phrms} = \frac{\sqrt{2} V_s}{3}$$

Phase  $\xrightarrow{\sqrt{3}}$  line

$$\text{Total} \quad \frac{\sqrt{2} V_s}{3}$$

fundam  $\downarrow \frac{3}{\pi}$

120° conduction mode

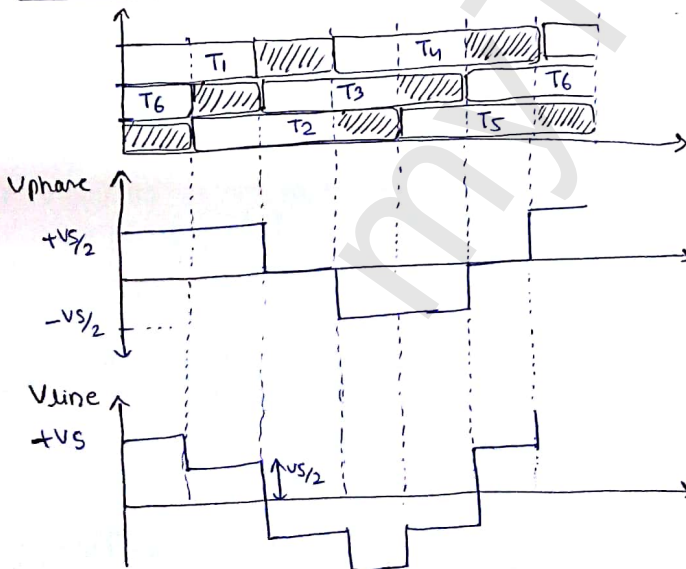

Each thyristor conduct for 120°  
at a time 2 thyristor conduct

$$V_{phrms} = \frac{V_s}{\sqrt{6}}$$

Phase  $\xrightarrow{\sqrt{3}}$  line

$$\text{Total} \quad \frac{V_s}{\sqrt{6}}$$

fundam  $\downarrow \frac{3}{\pi}$



120° की line की waveform  
120° की phase की  $\frac{1}{\sqrt{6}}$  पर 120° की phase की mag  
 $\frac{1}{2}$  पर  $\frac{1}{\sqrt{6}}$  पर  $V_s \frac{1}{\sqrt{6}}$



Q A single phase full bridge VSI delivers power at  $500\text{ Hz}$  to RLC load with  $R=5\Omega$ ,  $L=0.3\text{ H}$ ,  $C=50\mu\text{ F}$ . The dc link voltage is  $220\text{ volts}$ . Determine

- expression for load current upto 5th harmonic.
- Power delivered to the load and the fundamental power.
- Rms and peak values of current in each switch.
- Conduction time of switches and diodes by considering only fundamental component.

Sol<sup>n</sup>

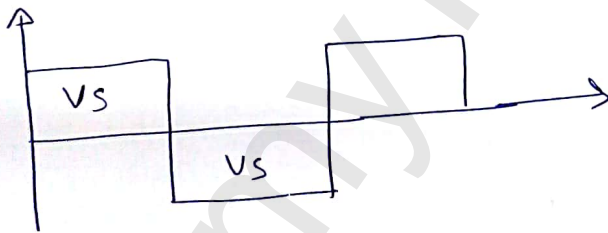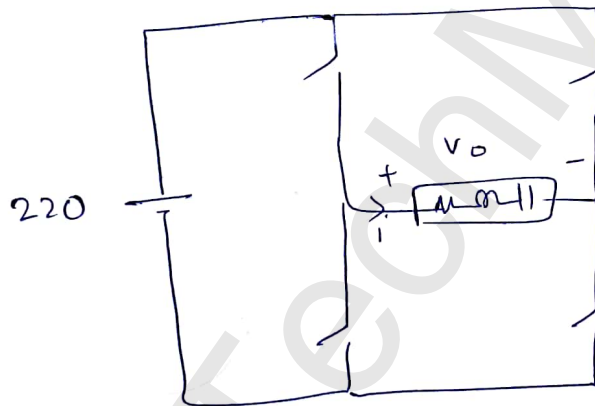

$$V_o = \frac{4V_s}{\pi} \sin \omega t + \frac{4V_s}{3\pi} \sin 3\omega t + \frac{4V_s}{5\pi} \sin 5\omega t + \frac{4V_s}{7\pi} \sin 7\omega t$$

$$I_o = \frac{4V_s}{|Z_1| \pi} \sin(\omega t - \phi_1) + \frac{4V_s}{|Z_3| 3\pi} \sin(3\omega t - \phi_3) + \frac{4V_s}{|Z_5| 5\pi} \sin(5\omega t - \phi_5)$$

$$+ \frac{4V_s}{|Z_7| 7\pi} \sin$$

By Sir

$$a) V_{om} = \frac{4V_s \sin n\omega t}{n\pi}$$

$$i_{om} = \frac{4V_s}{Z_n} \frac{V_{om}}{Z_n}$$

$$= \frac{V_{om}}{|Z_n| \cos \phi_n} = \frac{V_{om} \cos \phi_n}{|Z_n|} = \frac{4V_s \sin(n\omega t - \phi_n)}{n\pi |Z_n|}$$

$$i_o = i_1 + i_3 + i_5 +$$

$$i_o = \frac{4V_s}{\pi |Z_1|} \sin(\omega t - \phi_1) + \frac{4V_s}{3\pi |Z_3|} \sin(3\omega t - \phi_3) + \frac{4V_s}{5\pi |Z_5|} \sin(5\omega t - \phi_5)$$

⊕

$$|Z_n| = \sqrt{R^2 + (X_{Ln} - X_{Cn})^2}$$

$$|Z_1| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$|Z_3| = \sqrt{R^2 + (3\omega L - \frac{1}{3\omega C})^2}$$

$$|Z_5| = \sqrt{R^2 + (5\omega L - \frac{1}{5\omega C})^2}$$

$$\phi_1 = \tan^{-1} \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$\phi_3 = \tan^{-1} \left( \frac{3\omega L - \frac{1}{3\omega C}}{R} \right)$$

$$\phi_5 = \tan^{-1} \left( \frac{5\omega L - \frac{1}{5\omega C}}{R} \right)$$

$$R = 5 \Omega$$

$$L = 0.3 \text{ H}$$

$$C = 50 \mu\text{F}$$

$$\omega L = 314 \times 0.3 = 94.2$$

$$\frac{1}{\omega C} = 63.69$$

$$|Z_1| = 30.98 \Omega$$

$$\phi_1 = 80.73^\circ$$

$$|Z_3| = 261.5 \Omega$$

$$\phi_3 = 88.9^\circ$$

$$|Z_5| = 458.53 \Omega$$

$$\phi_5 = 89.37^\circ$$

$$\frac{4V_s}{\pi} = \frac{4 \times 220}{\pi} = 280.11$$

$$i_o = \frac{280.11}{30.98} \sin(\omega t - 80.73^\circ) + \frac{280.11}{3 \times 261.5} \sin(3\omega t - 88.9^\circ) + \frac{280.11}{5 \times 458.53} \sin(5\omega t - 89.37^\circ)$$

$$i_o = 9 \sin(\omega t - 80.73^\circ) + 0.357 \sin(3\omega t - 88.9^\circ) + 0.122 \sin(5\omega t - 89.37^\circ)$$

$$I_{or} = \sqrt{\left(\frac{9}{\sqrt{2}}\right)^2 + \left(\frac{0.357}{\sqrt{2}}\right)^2 + \left(\frac{0.122}{\sqrt{2}}\right)^2}$$

$$I_{or} = 6.37 \text{ A}$$

Fundamental power

$$P_1 = V_{o1} \cdot I_{o1} \cos \phi_1$$

$$= 198 \times \frac{9}{\sqrt{2}} \times \cos(80.73)$$

$$P_1 = 202.98 \text{ watt}$$

$$P_3 = 66.02 \times \frac{0.357}{\sqrt{2}} \times \cos 88.9$$

$$= 0.3199$$

$$P_5 = 39.61 \times \frac{0.122}{\sqrt{2}} \times \cos 89.37$$

$$= 0.0375$$

$$P = P_1 + P_3 + P_5$$

$$= 202.98 + 0.3199 + 0.0375$$

$$P = \underline{203.3375}$$

• End

$$P = I_{or}^2 R$$

$$(6.37)^2 \times 5$$

$$= 202.8845$$

(3)


$$V_{o1} = \frac{2\sqrt{2} V_s}{\pi}$$

$$V_{o1} = \frac{2\sqrt{2} V_s}{\pi} = \frac{2\sqrt{2} \times 220}{\pi} = 198.07$$

$$V_{o3} = \frac{2\sqrt{3} V_s}{3\pi} = 66.02$$

$$V_{o5} = \frac{2\sqrt{2} V_s}{5\pi} = 39.61 \text{ V}$$

③

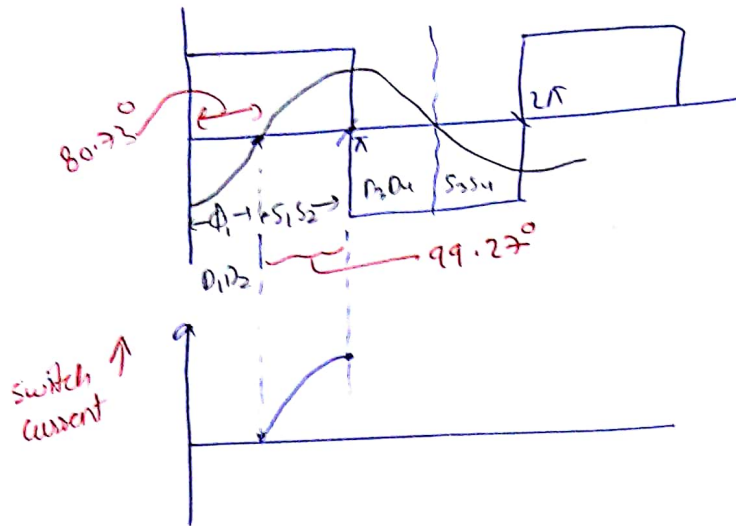

$$\begin{aligned}
 I_{rms}^2 &= \left\{ \frac{1}{2\pi} \int_0^{99.27^\circ} 9^2 \sin^2 \omega t \, d\omega t \right\} \\
 &= \frac{81}{2\pi} \int_0^{99.27^\circ} \frac{1 - \cos 2\omega t}{2} \, d\omega t \\
 &= \frac{81}{2 \cdot 2\pi} \left[ \frac{(99.27 - 0) \times \pi}{180} - \left[ \sin 2\omega t \right]_0^{99.27^\circ} \right] \\
 &= 6.405 [1.7325 + 0.3179] \\
 &= 13.215 \\
 I_{rms} &= \sqrt{13.215} = 3.635
 \end{aligned}$$


④ Cond<sup>n</sup> angle of Diode =  $\phi_1 = 80.73^\circ$

$$\omega t = \frac{80.73 \times \pi}{180} = 1.409$$

Conduction time of diode =  $\frac{1.409}{2\pi f} = 4.48 \text{ m sec}$

- Q A 3 $\phi$  VSI operating in 120° mode feeds a star connected load of  $R = 5\Omega$ , DC source voltage is 230 volts and  $\omega$  is 50 rad/s
- Rms value of line to line  $\omega$ p voltage and line to neutral  $\omega$ p voltage and  $n^{\text{th}}$  line current in fourier series up to 5 $^{\text{th}}$  harmonic component
  - Rms value of line to line and line to neutral voltage
  - Rms value of line to line and line to neutral voltages at fundamental frequency
  - Total Harmonic distortion for line current
  - Load power & avg value of source current
  - avg and rms value of switch current.

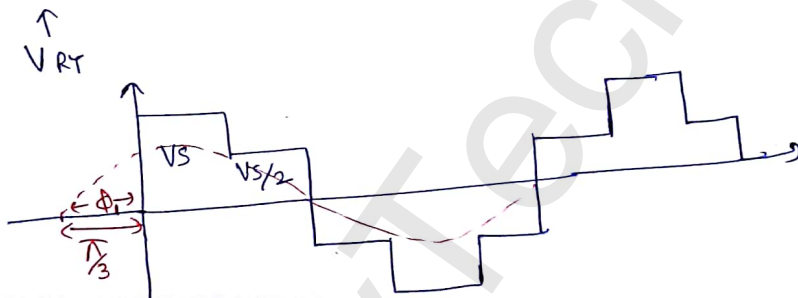50 rad/s 3 $\phi$ , 120°  $\Delta$  connected load.



$$C_n = \frac{6X}{n\pi} = \frac{6 \cdot V_S/2}{n\pi} = \frac{3V_S}{n\pi}$$

$$V_{Rn} = \frac{3V_S}{n\pi} \sin n(\omega t + \pi/3)$$

$$V_{R1} = \frac{3V_S}{\pi} \sin(\omega t + \pi/3)$$

$$V_{R5} = \frac{3V_S}{5\pi} \sin 5(\omega t + \pi/3)$$

$$V_{R7} = \frac{3V_S}{7\pi} \sin 7(\omega t + \pi/3)$$

$$V_{R11} = \frac{3V_S}{11\pi} \sin 11(\omega t + \pi/3)$$

$$V_{RY} = \frac{3V_s}{\pi} \sin(\omega t + \frac{\pi}{2}) + \frac{3V_s}{5\pi} \sin 5(\omega t + \frac{\pi}{3}) + \frac{3V_s}{7\pi} \sin 7(\omega t + \frac{\pi}{3}) + \frac{3V_s}{11\pi} \sin 11(\omega t + \frac{\pi}{3})$$

$$\frac{3V_s}{\pi} = \frac{3 \cdot 230}{\pi} = 219.6$$

$$V_{RY} = 219.6 \sin(\omega t + \frac{\pi}{3}) + 43.92 \sin 5(\omega t + \frac{\pi}{3}) + 31.37 \sin 7(\omega t + \frac{\pi}{3}) + 19.9 \sin(11\omega t + \frac{\pi}{3})$$

$V_R$

Phase:

$$\hookrightarrow V_R = \frac{2V_s}{\pi} \sin \frac{\pi}{3} \sin(\omega t + \frac{\pi}{6}) + \frac{2V_s}{5\pi} \sin \frac{5\pi}{3} \sin 5(\omega t + \frac{\pi}{6}) + \frac{2V_s}{7\pi} \sin \frac{7\pi}{3} \sin 7(\omega t + \frac{\pi}{6})$$

$$+ \frac{2V_s}{11\pi} \sin \frac{11\pi}{3} \sin 11(\omega t + \frac{\pi}{6})$$

$$V_R = 126.7 \sin(\omega t + \frac{\pi}{6}) - 25.36 \sin(5\omega t + \frac{5\pi}{6}) + 18.15 \sin(7\omega t + \frac{7\pi}{6})$$

$$- 11.52 \sin(11\omega t + \frac{11\pi}{6})$$

$$I_R = 25.34 \sin(\omega t + \frac{\pi}{6}) - 5.072 \sin(5\omega t + \frac{5\pi}{6}) + 3.63 \sin(7\omega t + \frac{7\pi}{6}) - 2.304 \sin(11\omega t + \frac{11\pi}{6})$$

$$I_{R_{rms}} = \sqrt{I_{R1}^2 + I_{R5}^2 + I_{R7}^2 + I_{R11}^2}$$

(b)  $V_L = \frac{V_s}{\sqrt{2}} = \frac{230}{\sqrt{2}} = 162.63$

$$V_{pn} = \frac{V_L}{\sqrt{3}} = 93.89$$

(c)  $V_{RY1_{rms}} = \frac{219.6}{\sqrt{2}} = 155.28$

$$V_{R1_{rms}} = \frac{126.7}{\sqrt{2}} = 89.6$$

(d) 31.1. bcz load is resistive

e) Load power

$$3 I_{ph}^2 R$$

$$I_{ph} = \frac{V_{ph}}{R} = \frac{93.89}{5} = 18.77$$

$$P = 3 I_{ph}^2 R = 5.289 \text{ kW}$$

f) avg value of Supply current.  
Supply current will be dc.





$$V_s \cdot I_s = P_o = 5.289 \times 10^3$$

$$I_s = 22.9 \text{ A}$$

if in qun<sup>n</sup>  $I_s$  asked then first find  $P_o$  then use power balance eq<sup>n</sup>.

g) avg and rms value of switch current

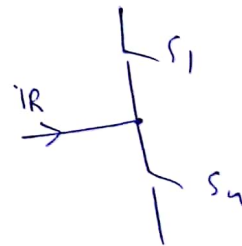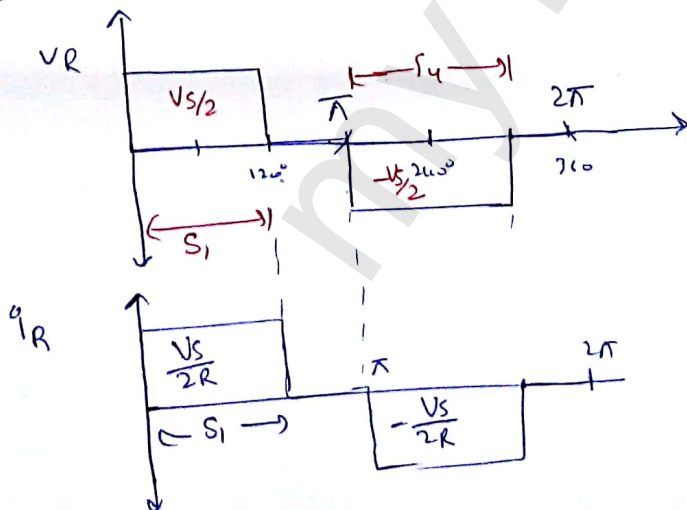



$$I_{s \text{ avg}} = \frac{V_s}{2R} \left( \frac{2\pi/3}{2\pi} \right) = \frac{V_s}{2R} \cdot \frac{1}{3} = \frac{230}{2 \cdot 5 \cdot 3} = 7.66 \text{ A}$$

$$I_{s \text{ rms}} = \frac{V_s}{2R} \left( \frac{2\pi/3}{2\pi} \right)^{1/2} = \frac{V_s}{2R \cdot \sqrt{3}} = 13.279 \text{ A}$$

Date: 21 August

Q A 3 $\phi$  Full conv<sup>r</sup> Bridge<sup>o</sup> fed to  $\Delta$  Xmer

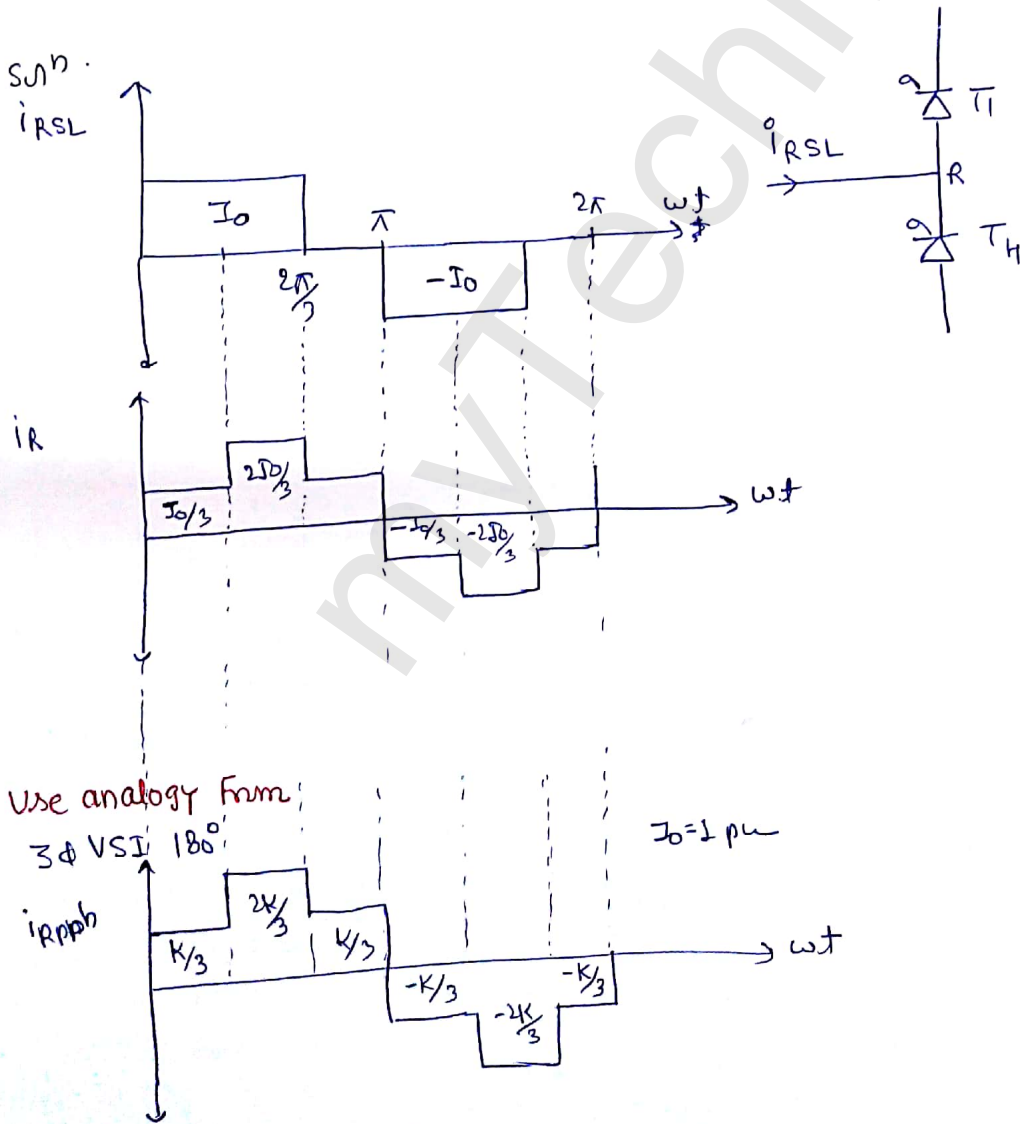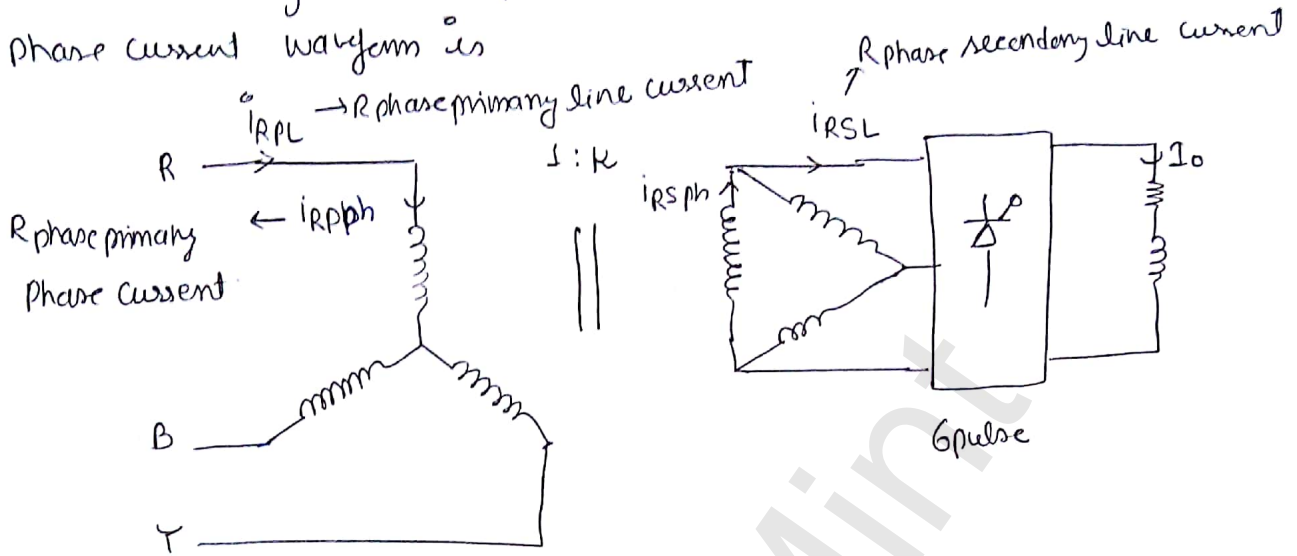the conv<sup>r</sup> is operated at a firing angle of  $30^\circ$ . assuming the load current  $I_o$  to be virtually const<sup>t</sup> at 1 pu and Xmer to be an ideal one, the i/p phase current waveform is







# PWM Inverters

ONE ques<sup>n</sup> PWM


Gate and IES

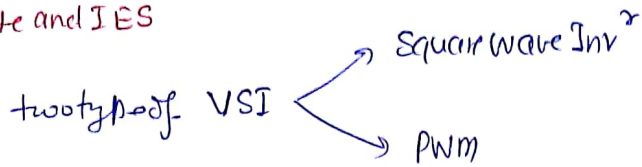

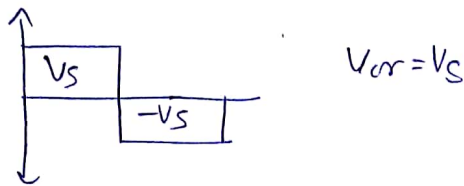Square wave Inv<sup>r</sup> (drawback we can vary freq<sup>c</sup> NOT the rms




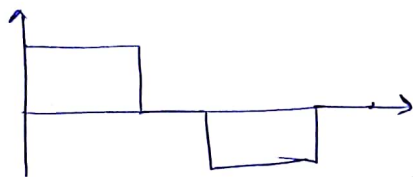3 $\phi$  - VSI (180 $^\circ$  mode) is also called Square wave mode




may be voltage waveform is Quasi wave but its called square wave mode bcz we can't change the rms of the waveform.

## ① Single PWM Tech

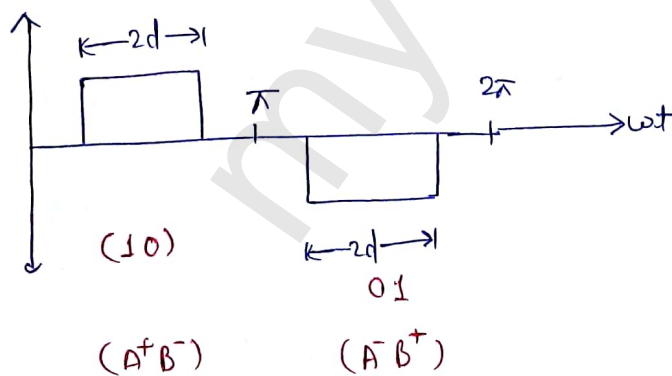

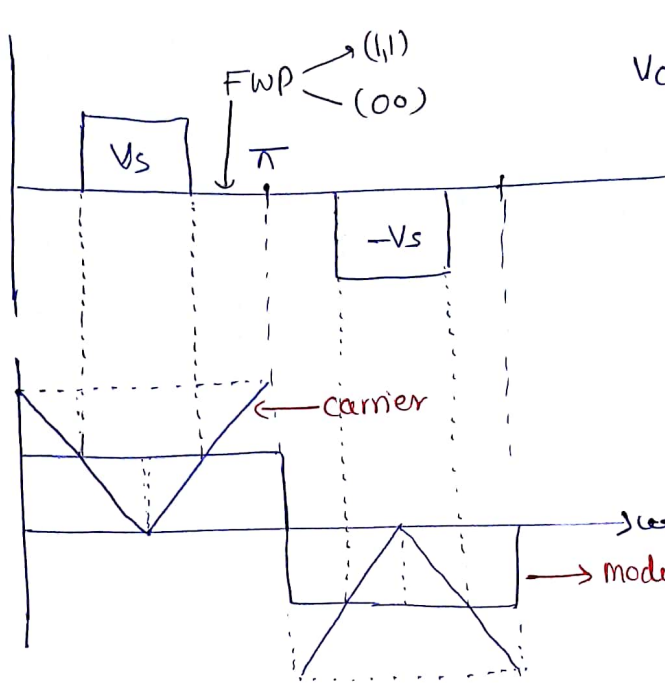we will control the gate sig pulse of  $A^+$ ,  $A^-$ ,  $B^+$ ,  $B^-$ , we have four switch here  $A^+$   $A^-$   $B^+$   $B^-$  and every switch has one gate sig pulse.



$$V_{or} = V_s \left( \frac{2d}{\pi} \right)^{\frac{1}{2}}$$

Power sig  $V_s$  is of KV's.

$$V_{om} = \frac{4V_s}{n\pi} \sin n d \sin n \omega t$$

FWP [Free wheeling period]

if  $|A_m| > |a_c| \rightarrow (1,0)$  if  $a_c^+$   
 $\rightarrow (0,1)$  if  $a_c^-$


$|A_m| < |a_c| \rightarrow$  FWP  $\begin{cases} (1,1) \\ (0,0) \end{cases}$

if use (1,1) logic - upper switch used more

if " " (0,0) " - lower " " "

Remedy

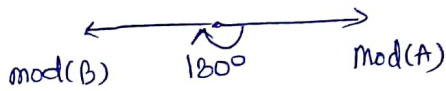- 1 modulating sig to control the switches of leg A
- 2nd " " " " " " " " leg B




$$\text{mod}(A) > a_c \rightarrow 1 \quad (A^+)$$

$$\text{mod}(A) < a_c \rightarrow 0 \quad (A^-)$$

---


$$\text{mod}(B) > a_c \rightarrow 1 \quad (B^+)$$
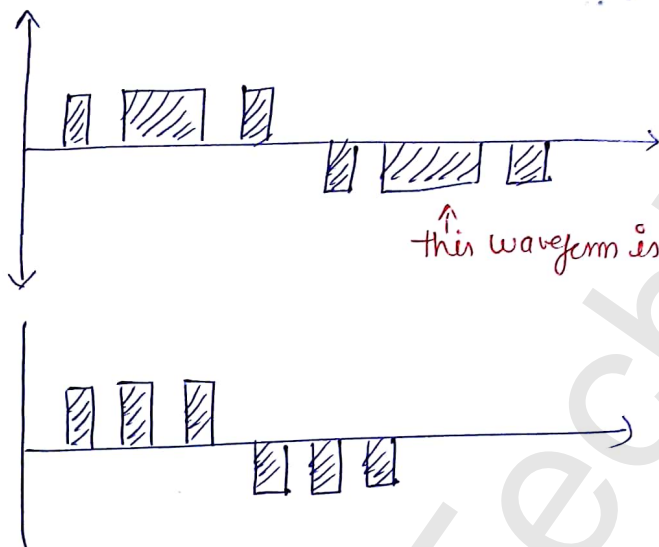
$$\text{mod}(B) < a_c \rightarrow 0 \quad (B^-)$$




we will use sinusoidal modulated sig

↑ this waveform is better than below. bcz THD ↓ es.

Sin-Triangle unipolar PWM

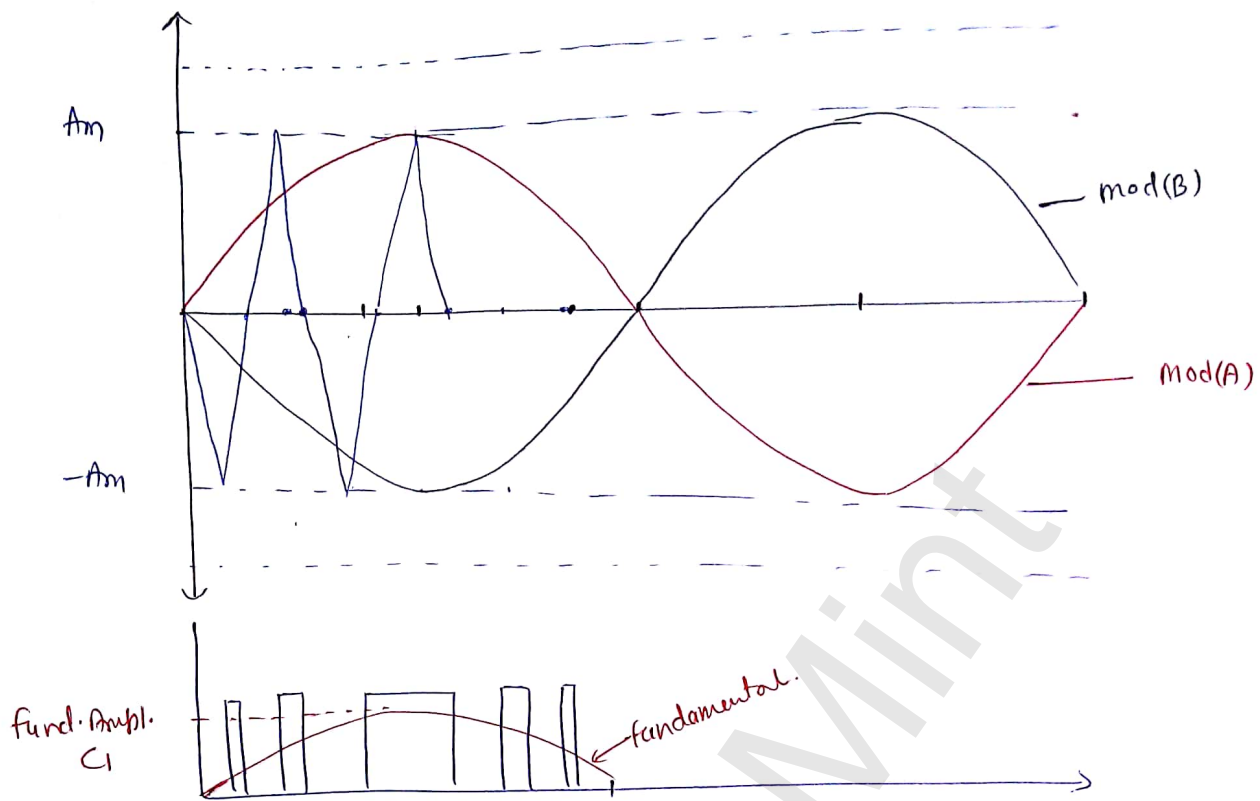we will use two modulating sig one for leg A and one for leg B.





How many carrier we have b/w A and B that many pulses.

$$\uparrow M_A = \frac{A_m \uparrow}{A_c}$$

Amplitude modulation Index decides the mag. of Fundamental amplitude.

as  $A_m \uparrow$ , Fundamental Amp  $\uparrow$ es.

$V_{o1} \rightarrow$  Fundamentals

$\hat{V}_{o1} \rightarrow$  Peak Funda i.e  $C_1$

Rembr

$$\hat{V}_{o1} = M_A \hat{V}_s \rightarrow 1 \phi \text{ Full bridge Inv}^r$$

$$\hat{V}_{o1} = M_A \cdot \frac{V_s}{2} \rightarrow 1 \phi \text{ Half bridge Inv}^r$$

$$\hat{V}_{L1} = M_A \cdot \frac{\sqrt{3} V_s}{2} \rightarrow 3 \phi V_{s1}$$


these all when

$M_A \leq 1$

Linear Modulation

Peak value of Fundamental line voltage

# 1 $\phi$ VSI Square wave mode

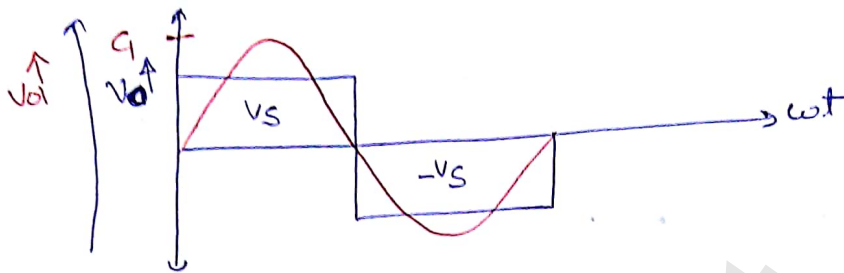

$$C_n = \frac{4V_s}{n\pi}$$

$$\hat{V}_{o1} = \frac{4V_s}{\pi} = 1.27V_s$$


max

$$\frac{\hat{V}_{o1}}{V_s} = 1.27$$

max


$$\hat{V}_{o1} = M_A \hat{V}_s \rightarrow 1\phi \text{ full bridge}$$

$$\frac{\hat{V}_{o1}}{V_s} = M_A$$

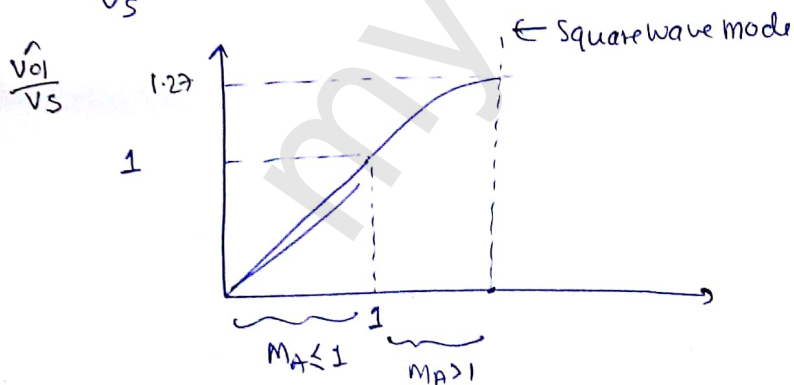

3 $\phi$  VSI - Square wave mode ( $\theta = 0^\circ$ )

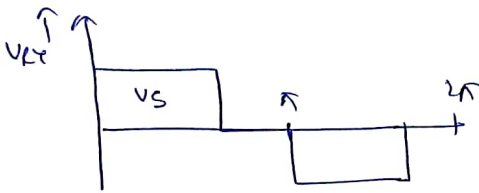3 $\phi$  VSI : PWM mode ( $M_A \leq 1$ )



$f_m$  modulation index

$$M_F = \frac{f_c}{f_m}$$

$f_m$  - modulating  $f_m$  is decided by  $\omega_p$   $f_m$   
 sig of ~~inv~~ sig

$$f_m = f_{op} = \frac{f}{2} =$$

$$\uparrow M_F = \frac{f_c \uparrow}{f_m}$$

$\rightarrow$   $M_F$  decides harmonic spectrum

Harmonic Spectrum :  $n = \pm M_F \pm k$

If  $J = 1, 3, 5, \dots$   $k = 0, 2, 4, 6$

$\downarrow$   
 $J$  can't be 0

If  $J = 2, 4, 6, \dots$   $k = 1, 3, 5$

$M_F$  should be multiple of 3 to


$M_F$  should be an odd integer to satisfy kW symm.

$J = 1$   
 First side band  
 $f_m$

$$n = M_F \pm k$$

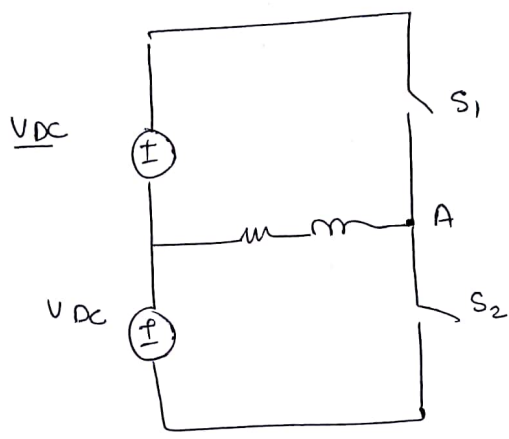Q.10

The figure shows a half bridge VSI supplying an RL load with  $R=40\Omega$  &  $L=\frac{0.3}{\pi}H$ , The desired fundamental  $\hat{I}_m$  of the load with  $f=50Hz$  & the switch control sigs of the each  $cnV^2$  are generated using sinusoidal PWM with modulation index = 0.6 at 50 Hz. RL load draws an active power of 1.44kW. Find the value of DC source voltage  $V_{dc}$ .



sol<sup>n</sup> Diode absent is it wrong  $\rightarrow$  No bcz Switch  $S_1$  &  $S_2$  can be RCT and RCT contain inbuilt diode so ckt correct only

$R=40\Omega$      $L=\frac{0.3}{\pi}H$


$f_1=50Hz$

Sinusoidal PWM ;  $M_A=0.6$


$=\frac{4x}{\pi}$

At 50Hz ,  $P=1.44kW$

$\hat{V}_{o1} = \frac{4V_{dc}}{\pi}$

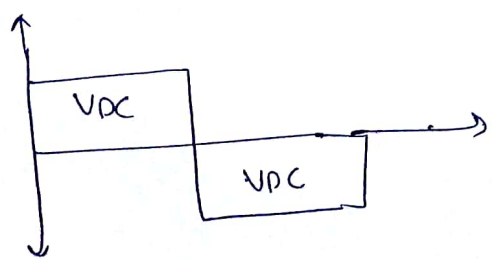

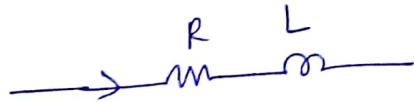$M_A = \frac{A_m}{A_c}$        $M_A = \frac{\hat{V}_{o1}}{V_s}$



$$P = V_{01} I_{01} \cos \phi$$

$$1.44 \times 10^3 = \frac{4V_{DC}}{\pi \sqrt{2}} \times \frac{4V_{DC}}{\pi \sqrt{2} |Z_1|} \cos \phi_1$$

$$I_{01} = \frac{4V_{DC}}{\pi \sqrt{2} |Z_1|}$$

$$\phi_1 = \tan^{-1} \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$I_{01} = \frac{4V_{DC}}{\pi \sqrt{2} \times 50}$$

$$\phi_1 = \tan^{-1} \left( \frac{314 \times 0.3}{40 \pi} \right)$$

$$1.44 \times 10^3 = \frac{16V_{DC}^2}{\pi^2 \times 2 \times 50} \times \cos 36.86^\circ$$

$$\phi_1 = \tan^{-1} \left( \frac{2 \pi \times 50 \times 0.3}{40 \pi} \right)$$

$$\tan^{-1} \frac{100 \times 3}{400}$$

$$\phi_1 = \tan^{-1} \left( \frac{3}{4} \right) = 36.86^\circ$$

$$Z_1 = \sqrt{(40)^2 + \left( \frac{314 \times 0.3}{\pi} \right)^2}$$

$$|Z_1| = 50$$



By  
sir

$$V_{ol} = M_A \cdot \frac{V_S}{2} \quad \leftarrow \text{use this formula when } (M_A \leq 1)$$

$$\frac{V_S}{2} = V_{DC}$$

$$V_{ol} = \frac{0.6 \times V_{DC}}{\sqrt{2}}$$

Fundamentals

$$P_1 = V_{ol} \cdot I_{ol} \cdot \cos \phi_1$$

$$I_{ol} = \frac{V_{ol}}{|Z_1|} = \frac{V_{ol}}{\sqrt{R^2 + X_1^2}}$$

$$\phi_1 = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$\phi = 36.86^\circ$$

$$P_1 = V_{ol} \cdot I_{ol} \cdot \cos \phi_1$$


$$1.44 \times 10^{-3} = \frac{V_{ol} \cdot V_{ol}}{|Z_1|} \cos \phi_1$$

$$= V_{ol}^2 \cdot \frac{1}{50} \cdot \cos 36.86^\circ$$

$$1.44 \times 10^{-3} = \left( \frac{0.6 V_{DC}}{\sqrt{2}} \right)^2 \times \frac{1}{50} \cdot \cos(36.86^\circ)$$

$$V_{DC} = 500\sqrt{2}$$

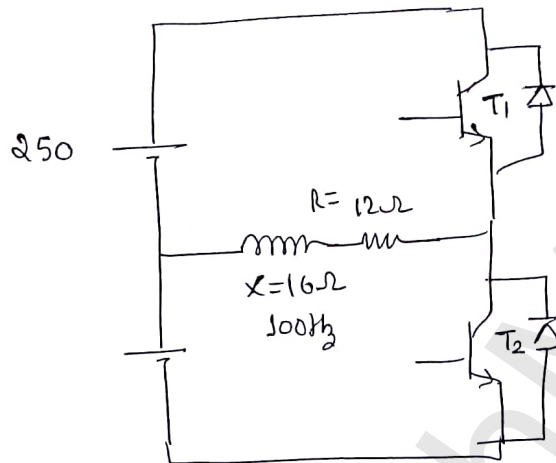Q The switches  $T_1$  and  $T_2$  are switched in a complementary fashion with sinusoidal pulse width modulation Technique the modulating voltage is  $V_m(t) = 0.8 \sin(200\pi t)$  V and the triangular carrier voltage magnitude is  $V_c = 1$  volt the carrier  $f_c$  is  $5 \text{ kHz}$ . Find the peak value of  $100 \text{ Hz}$  component of load current.



$$\text{Sol}^n \quad V_m(t) = 0.8 \sin(200\pi t)$$

$$\therefore 200\pi t = \omega t$$

$$200\pi \times \frac{1}{2} = 2\pi f$$

$$f = 100 \text{ Hz}$$

$$V_c = 1 \text{ volt}$$

$$f_c = 5 \text{ kHz}$$

$$M_f = \frac{f_c}{f_m} = \frac{5 \times 10^3}{100} = \frac{5000}{100} = 50$$

$$I_L = I_{o1} + I_{o2} + \dots$$

$$I_1 = \hat{I}_{o1} \sin(\omega t - \phi_1)$$

$$\hat{I}_{o1} = \frac{\hat{V}_{o1}}{|Z_L|}$$

By Sir

$$V_m(t) = 0.8 \sin(200\pi t)$$

$f_m = 100 \text{ Hz} = \text{Fundamental } f_{mc}$

modulation  $m_f = 1$

$$A_c = V_c = 1 \text{ V}$$

$$M_A = \frac{A_m}{A_c} = \frac{0.8}{1} = 0.8$$



$$\hat{V}_{O1} = M_A \cdot \frac{V_S}{2} \quad \leftarrow (M_A \leq 1) \text{ we can use formula.}$$

$$\hat{V}_{O1} = 0.8 \times 250$$

$$\hat{V}_{O1} = 200 \text{ V}$$

$$\hat{I}_G = \frac{\hat{V}_{O1}}{|Z_{L1}|} = \frac{200}{\sqrt{(12)^2 + (16)^2}} = 10 \text{ A}$$

Q) A single phase bidirectional VSI voltage source conv<sup>r</sup> VSC is shown in the figure given below all devices are ideal it is used to charge a battery at 400V with power of 500W from ac source of  $V_S = 220 \text{ V (rms)}$  at 50Hz sinusoidal ac at unity p.f. if its ac side interfacing inductor is 5mH and the switches are operated at 20kHz then the phase shift angle ( $\delta$ ) b/w the ac mains voltage  $V_S$  and fundamental ac rms VSC voltage ( $V_{G1}$ ) in degree is —.

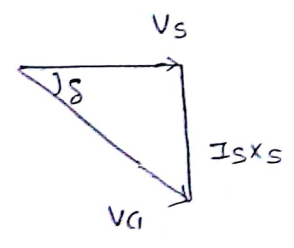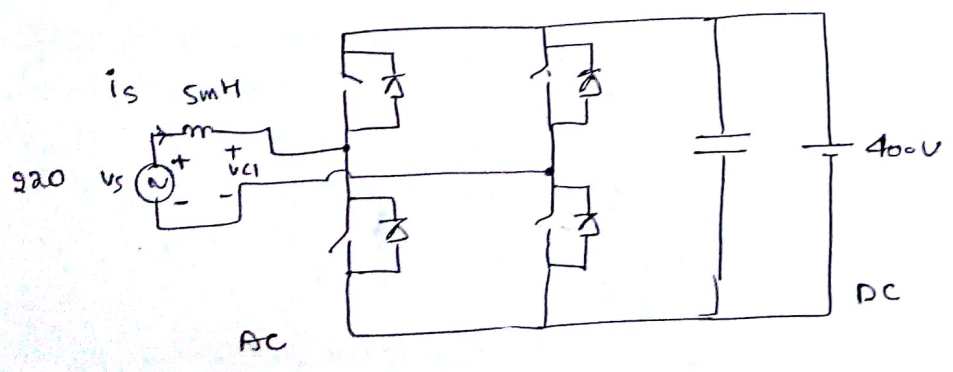


See on DC side - it is VSC

we can use VSC as Inverter and converter


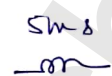
Supply is 60 Hz why we have to have to operate switch at  $f_c = 2000 \text{ Hz}$ .

PF=1 means no harmonic

Power flowing from ac  $\xrightarrow{\text{to}}$  DC

$V_s$  is 

$i_s$  is ?

i will make  $i_s$   using  and CH switch (9 am using PWM switches)


so  $i_s$  now  almost

$$P = V_{sr} \cdot I_{sr} \cdot PF$$

$$5 \times 10^3 = 220 \times I_{sr} (1)$$

$$I_{sr} = 22.7 \text{ A}$$
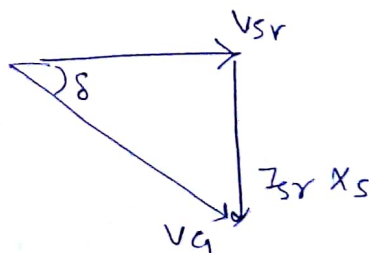
$$\tan \delta = \frac{I_{sr} X_s}{V_{sr}} = \frac{22.7 (2\pi f \cdot L_s)}{220} \quad \begin{matrix} 50 \\ \downarrow \\ 5 \times 10^{-3} \end{matrix}$$



$$\delta = 9.2$$

- Q A DC chopper is used for regenerative braking of a separately excited dc motor. The dc supply voltage is 400V. The motor has arm<sup>r</sup> resistance  $R_A = 0.5 \Omega$ ,  $K_m = 1.25 \text{ Vs/rad}$ . The avg arm<sup>r</sup> current during regenerative braking is kept const at 300A with negligible ripple for a duty cycle of 50%. Determine
- ① Power return to the dc supply
  - ② max<sup>m</sup> and min<sup>m</sup> permissible braking speed.
  - ③ Speed during regenerative braking.

Sol<sup>n</sup>: 2nd quadrant chopper is used in regenerative braking  
 2nd " " use boost chopper concept not exactly Boost chopper.  
 1st quadrant chopper (i.e Buck) used in motoring mode.



by Sir regenerative power for 2<sup>nd</sup> quad chopper

$$\begin{aligned}
 P &= V_o I_o \\
 &= V_s (1-d) I_o \\
 &= 400 (1-0.5) 300 \\
 &= 60 \text{ kW}
 \end{aligned}$$

during braking m/c behave as B' gear<sup>n</sup>  
 150 rev<sup>n</sup> or<sup>n</sup>

$$E_b = V_o + I_o R_a$$

negd<sup>min</sup> speed when  $(E_b)_{\min}$

$$(E_b)_{\min} = I_o R_a$$

$$K_{\omega} \omega_{\min} = \frac{I_o R_a}{K_m} = \frac{300 \times 0.2}{1.2 \text{ Vs/rad}} = 50 \text{ rad/sec}$$

negd<sup>max</sup> speed when  $V_o = \text{max}^m$  i.e.  $V_o = \text{supply voltage} = V_s$   
" " " "  $(E_b)_{\max}$

$$(E_b)_{\max} = V_s + I_o R_a$$

$$= 400 + (300 \times 0.2)$$

$$\omega_{\max} = \frac{400 + (300 \times 0.2)}{1.2 \text{ Vs/rad}}$$

$$\omega_{\max} = 383.33 \text{ Rad/sec}$$

①  $E_b = V_o + I_o R_a$

$$K \cdot \omega = V_s(1-\alpha) + I_o R_a$$

$$\omega = \frac{400(1-0.5) + (300 \times 0.2)}{1.2 \text{ Vs/rad}}$$

$$\omega = 216.67 \text{ rad/sec}$$

Q The speed of a separately excited dc motor is controlled through a 1 $\phi$  H wave controlled converter from 230 volts mains the motor arm<sup>y</sup> resistance is 0.5 $\Omega$  and motor const<sup>n</sup> is  $K = 0.4$  Vs/rad For load torque of 20 Nm at 1500 rpm and for const<sup>n</sup> arm<sup>y</sup> current calc

- Firing angle delay of a conv<sup>r</sup>
- Rms value of thyristor current.
- glp power factor of the motor

soln 1 $\phi$  Half wave — means 1 pulse

1 $\phi$  Half controlled — means 2 pulse semiconv<sup>r</sup>

$$230 = E_b + I_o R_a$$

$$230 = 0.4 \times \omega + I_o \times 0.5 \Omega$$

$$T_L = 20 \text{ Nm} = \frac{P}{\omega} = \frac{V_o I_o}{\omega}$$

$$T_L = E_b \times I_o$$


$$E_b = 230 - I_o R_a$$


$$\begin{aligned} \omega &= \frac{230}{K} - \frac{I_o R_a}{K} \\ &= \frac{230}{0.4} - \frac{20 \cdot R_a}{K \omega \cdot K} \end{aligned}$$

$$T_L = 20 = E_b \times I_o$$


$$20 = 0.4 \times \frac{2\pi \cdot 1500}{60} \times I_o$$

$$P = T \omega$$

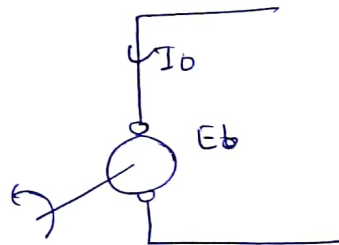

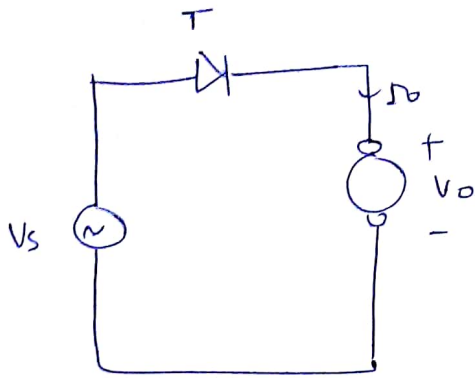

↓

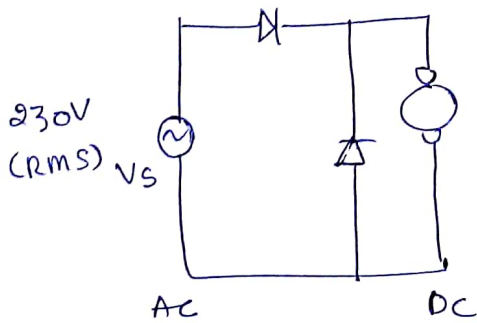

$$T_a = K I_o$$

$$20 = 0.4 I_o$$

$$I_o = \frac{20}{0.4} = 50 \text{ A}$$

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) = E_b + I_o R_o$$

$$\frac{230\sqrt{2}}{2\pi} (1 + \cos \alpha) = \frac{K \cdot 2\pi N}{60} + I_o R_o$$

$$= \frac{0.4 \times 2\pi (1500)}{60} + (50 \times 0.5)$$

$$\alpha = 45.84^\circ$$

$$(I_T)_{\text{RMS}} = I_o \left( \frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$= I_o \left( \frac{180 - \alpha}{360} \right)^{1/2}$$

$$= 50 \left( \frac{180 - 45.84}{360} \right)^{1/2}$$

$$= \cancel{45} \text{ A} = 30.52$$



using power balance eqn

$$P_{in} = P_o$$

$$V_{sr} \cdot I_{sr} \cdot PF = V_o I_o$$

$$PF = \frac{87.83 \times 50}{V_{sr} \times I_{sr}}$$

$$= \frac{230}{30.52}$$

$$PF = 0.625$$

$$V_o = \frac{2\sqrt{2} V_m}{2\pi} (1 + \cos \alpha)$$

$$V_o = 87.83 V$$

Find rectification efficiency

$$\text{Rectification efficiency} = \frac{P_{DC}}{P_{ac}} = \frac{V_o I_o}{V_{or} I_{or}}$$

$$V_{or} = \frac{V_m}{\sqrt{2.2\pi}} \left\{ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{1/2}$$

$\uparrow$   
 $45.84 \times \frac{\pi}{180}$   
 $0.499$